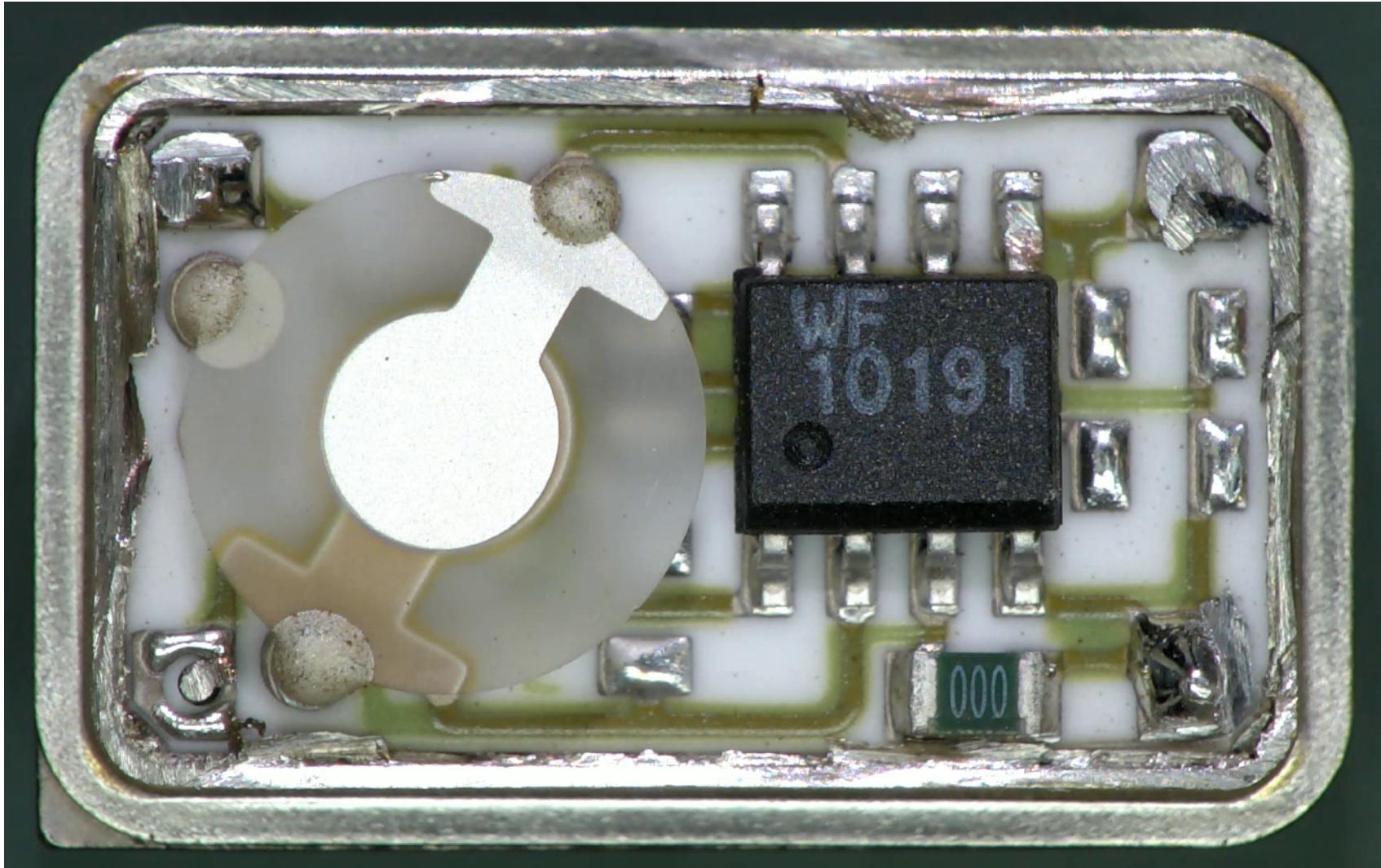


PHYS127AL Lecture 13


David Stuart, UC Santa Barbara, May 11, 2021

More oscillators



Review: Oscillator

We made an oscillator with an op-amp

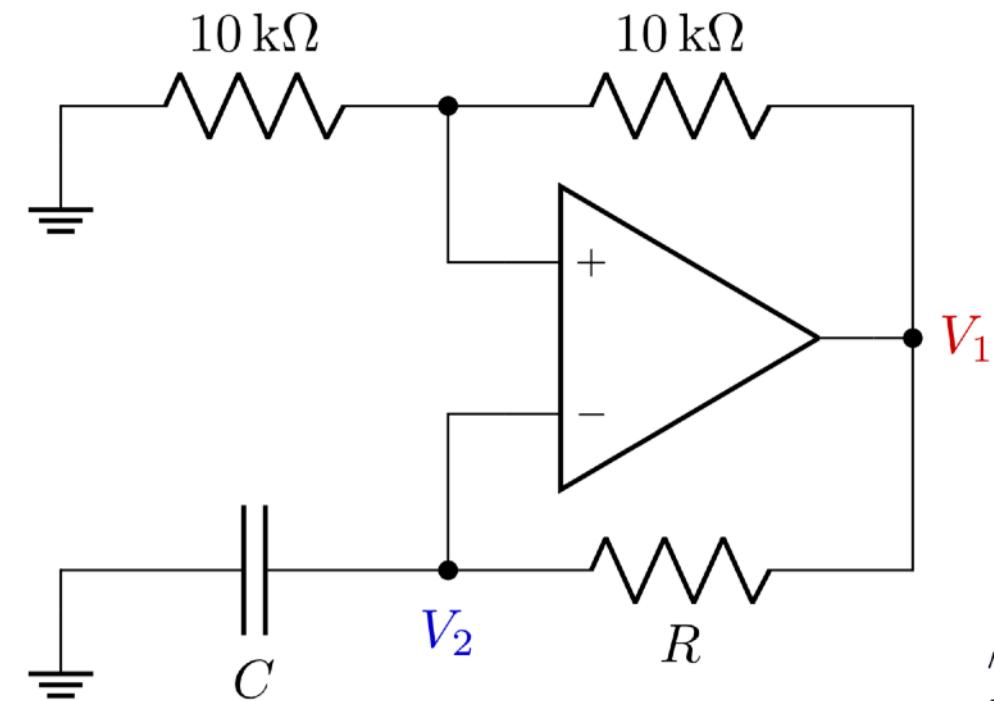

The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .


$$V_+ = V_1/2$$

$$V_2 = V_- = V_1 - I R$$

where $I = C \frac{dV_2}{dt}$


What is V_1 ?

$$T = RC \log 9 \approx 2.2 RC$$

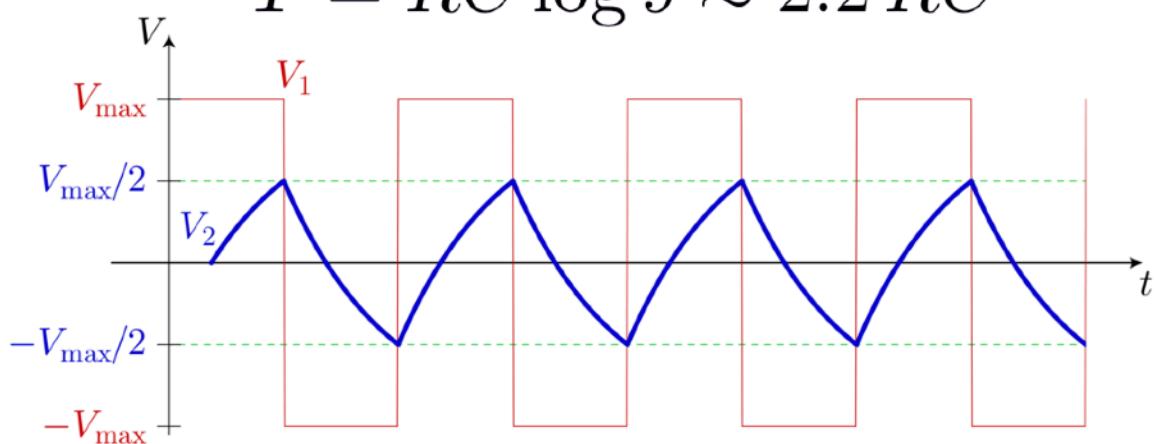


Review: 555 timer

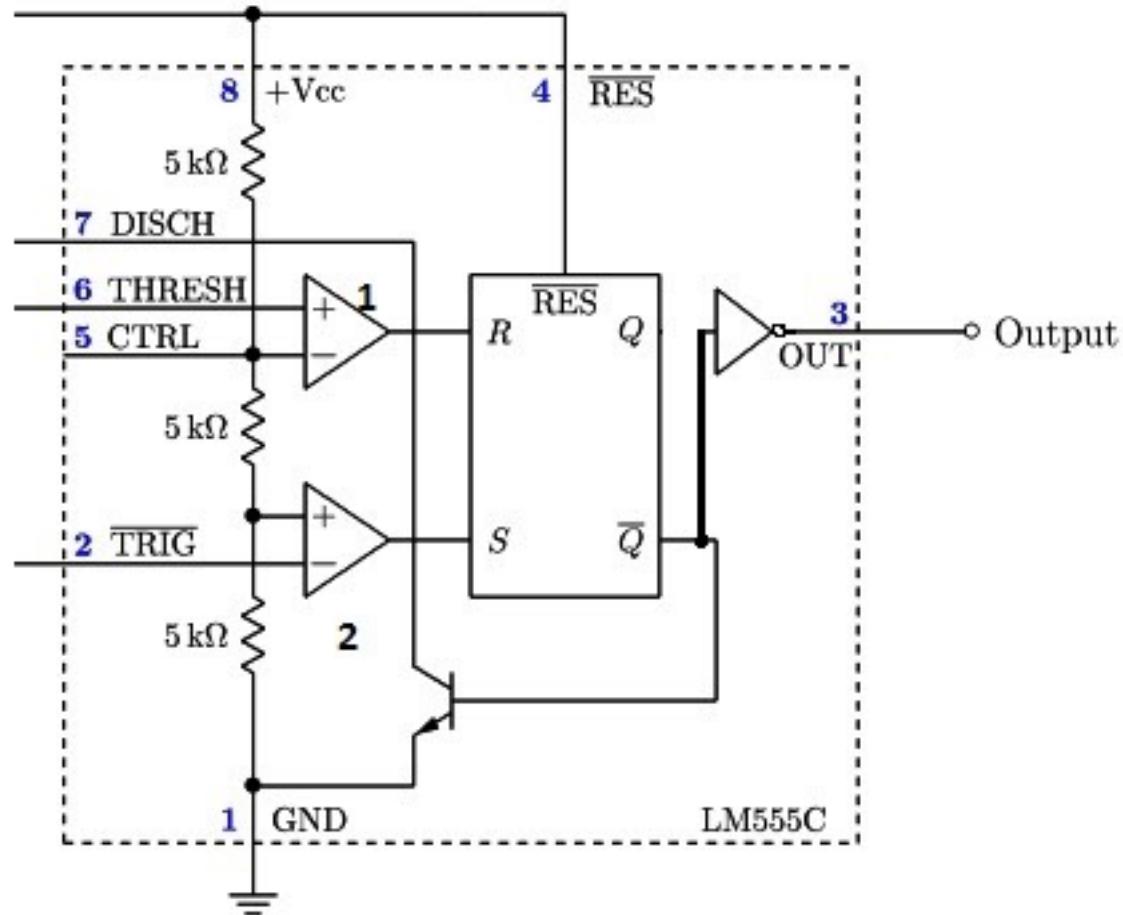Oscillators and other timing applications are so common, there is a timer chip



Review: 555 timer

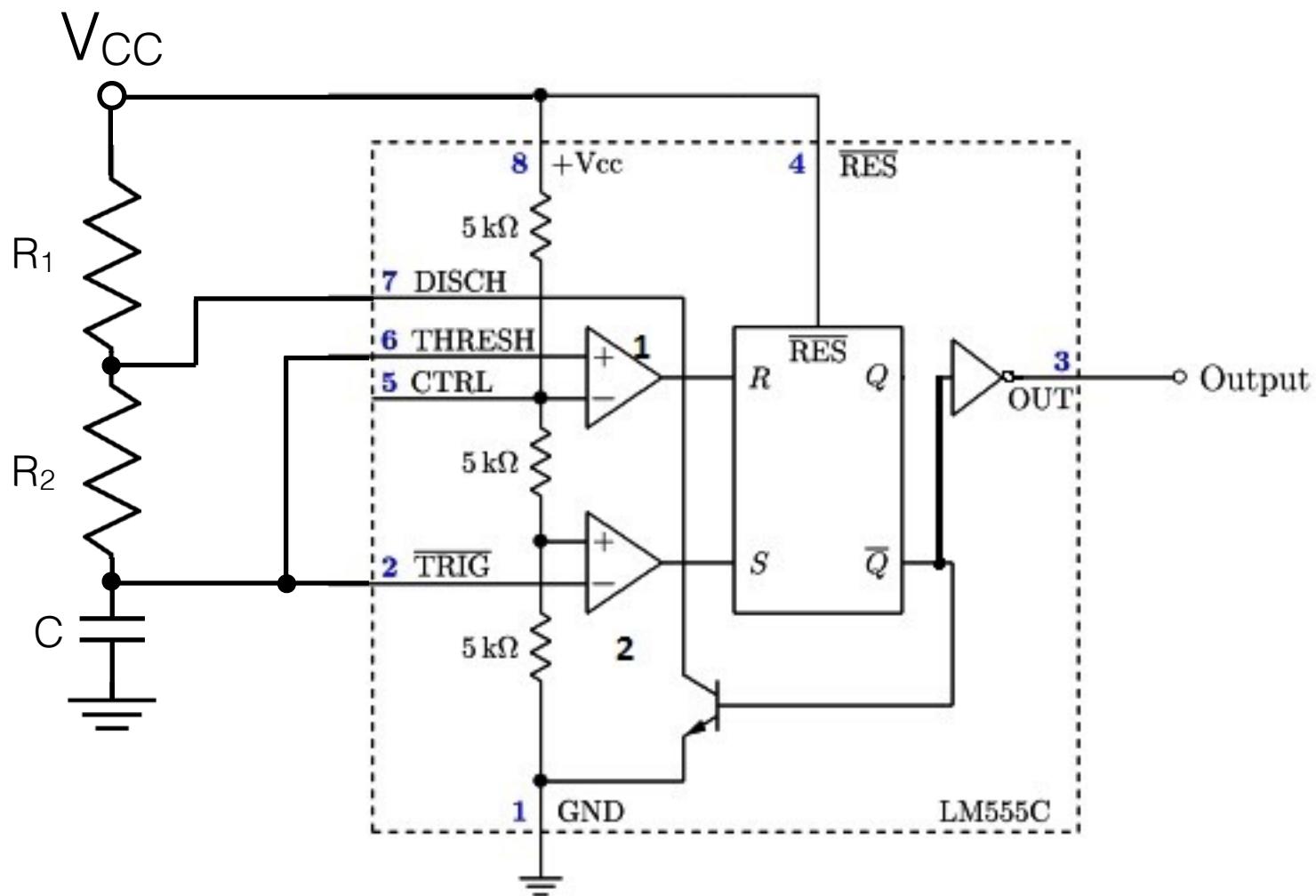
Oscillators and other timing applications are so common, there is a timer chip



This is the “astable” configuration. (Not stable in either configuration.)

Review: 555 timer



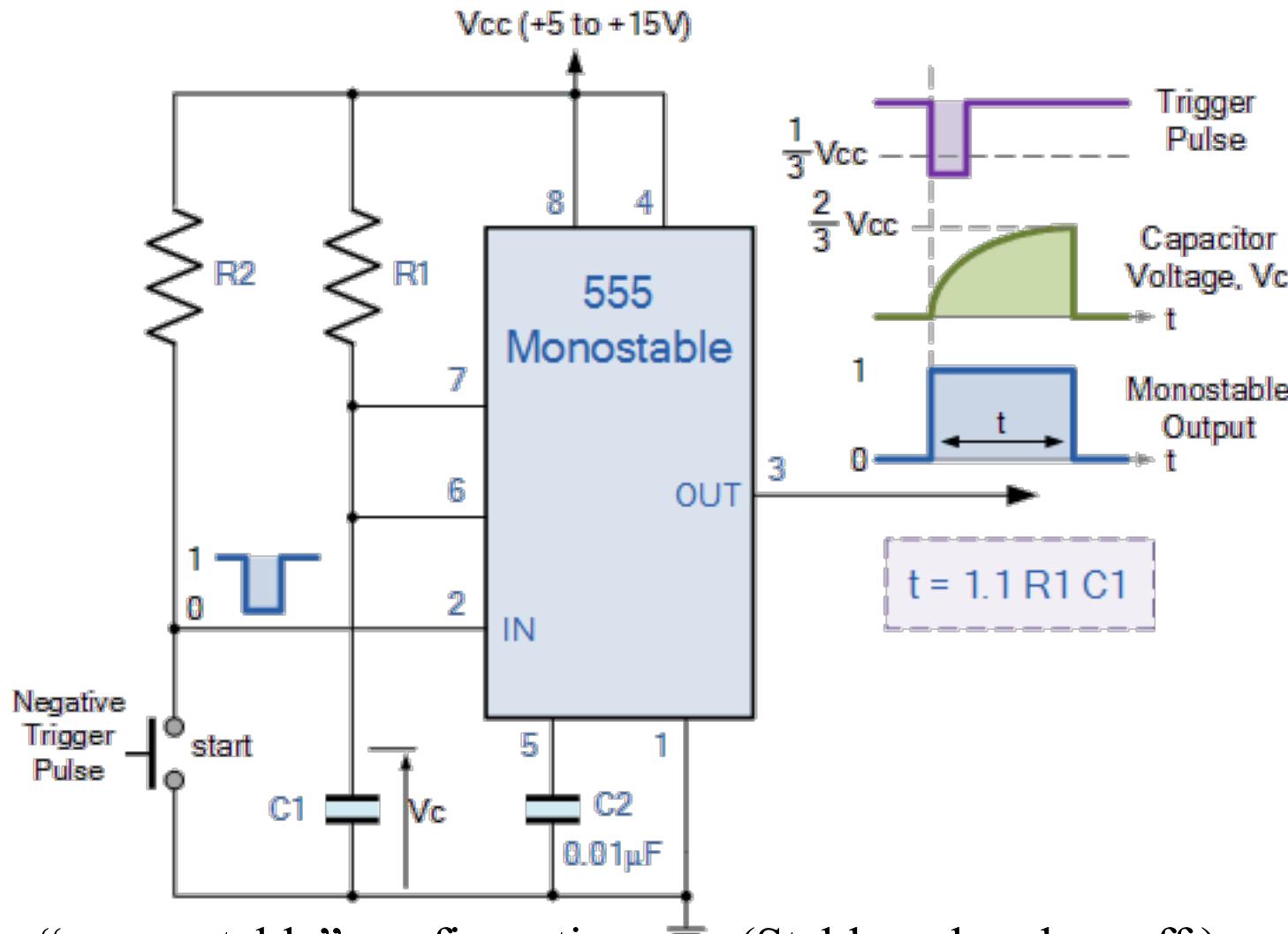
Oscillators and other timing applications are so common, there is a timer chip



This is the “mono-stable” configuration. (Stable only when off.)



Digital potentiometer

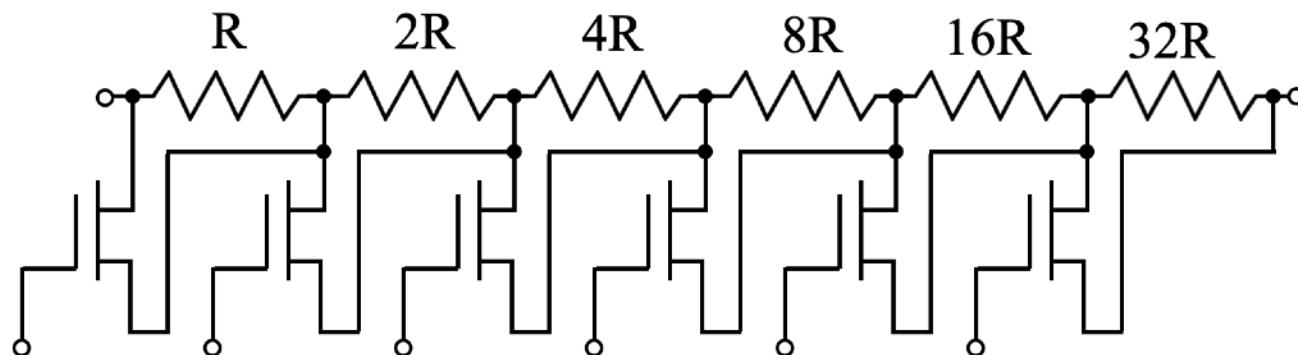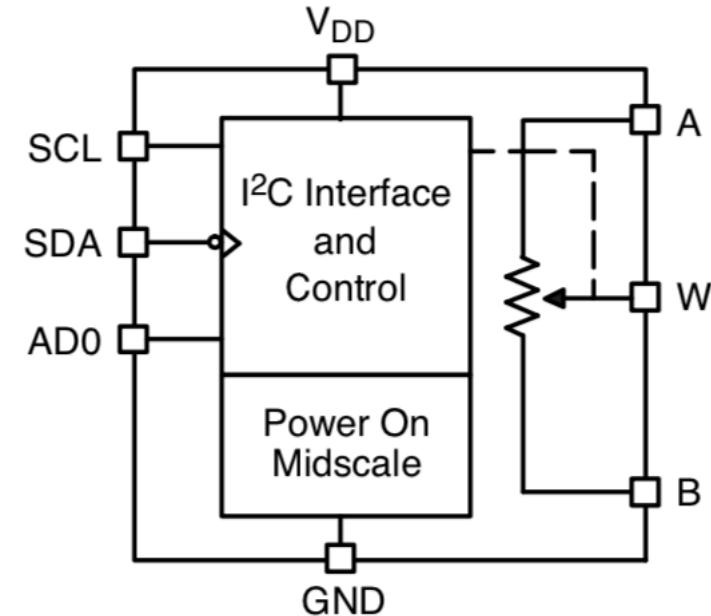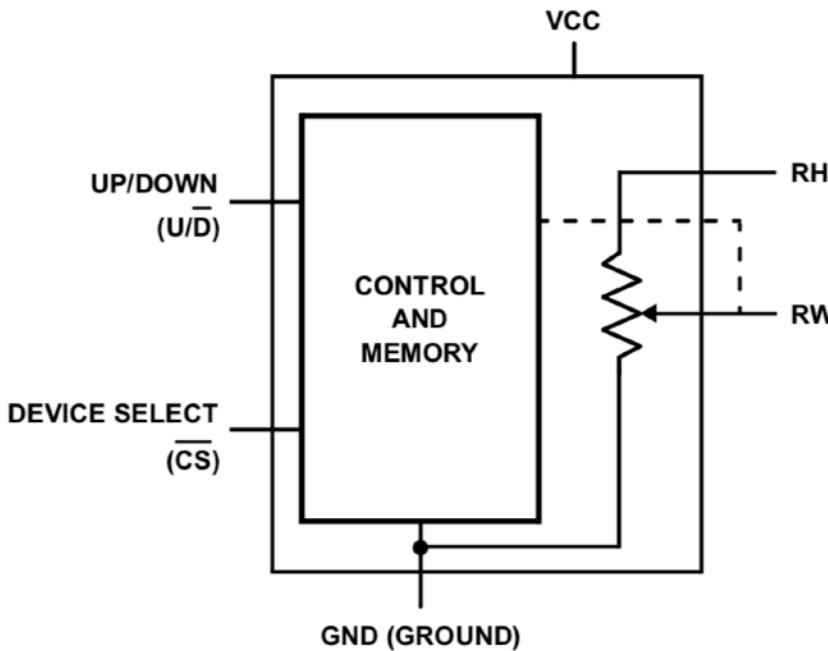We can adjust the frequency by changing the resistance with a potentiometer.
It is more common now to use a “digital potentiometer” (cheaper than trimpot).




Voltage controlled oscillator

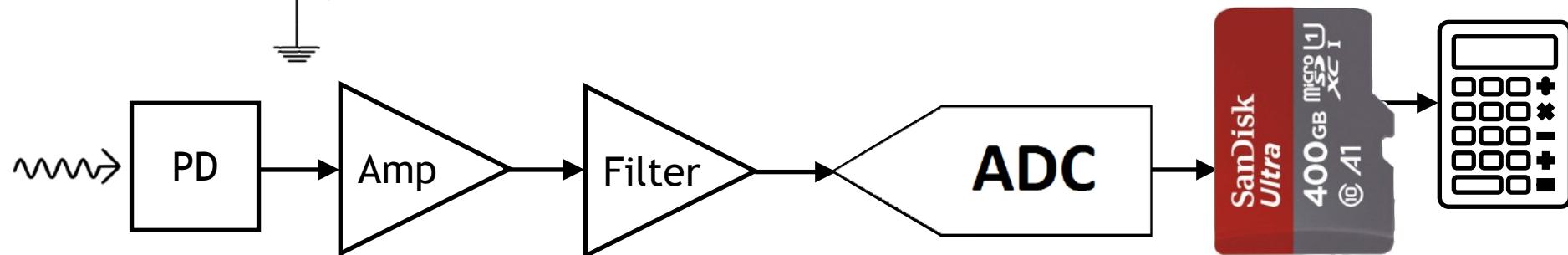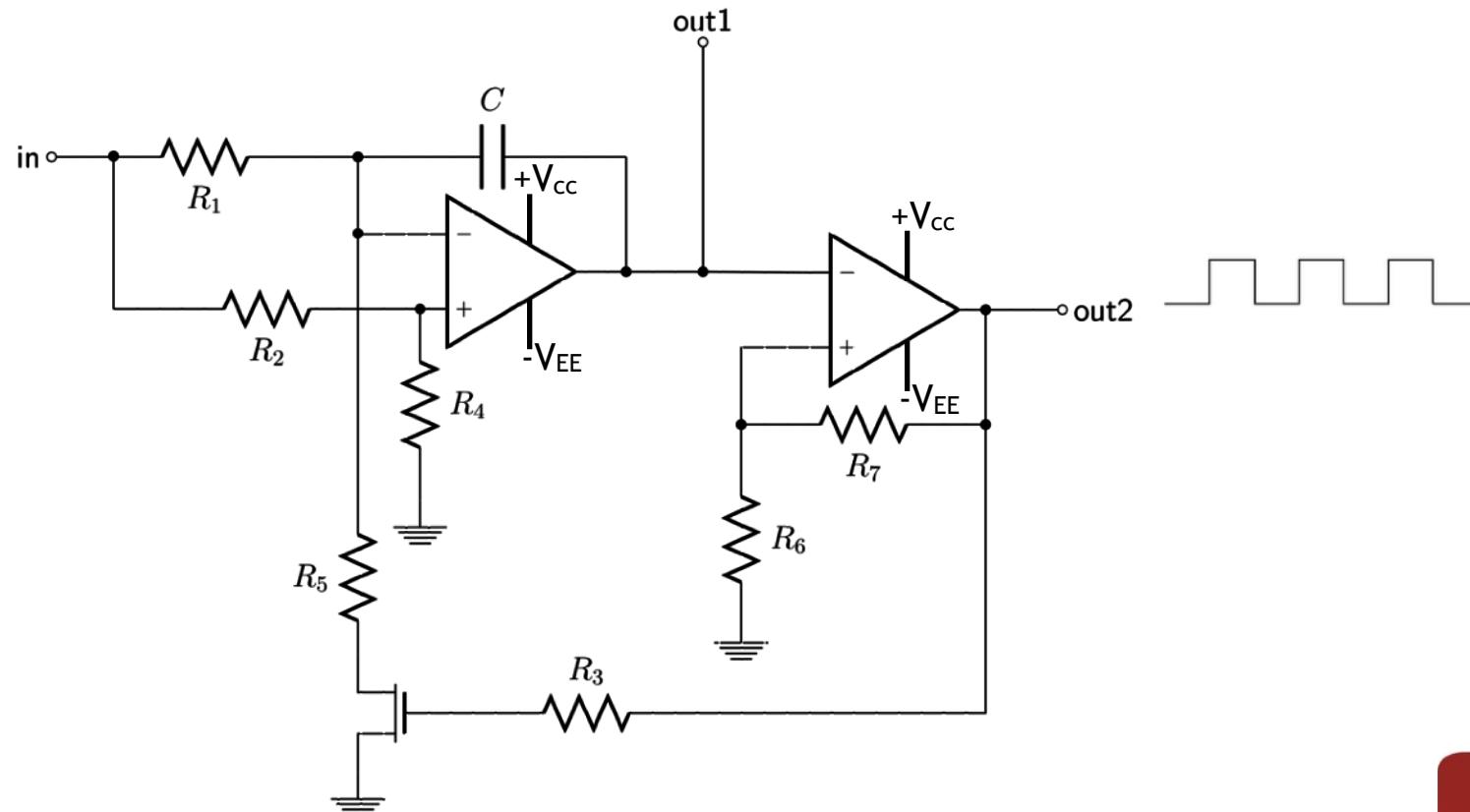It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Voltage controlled oscillator

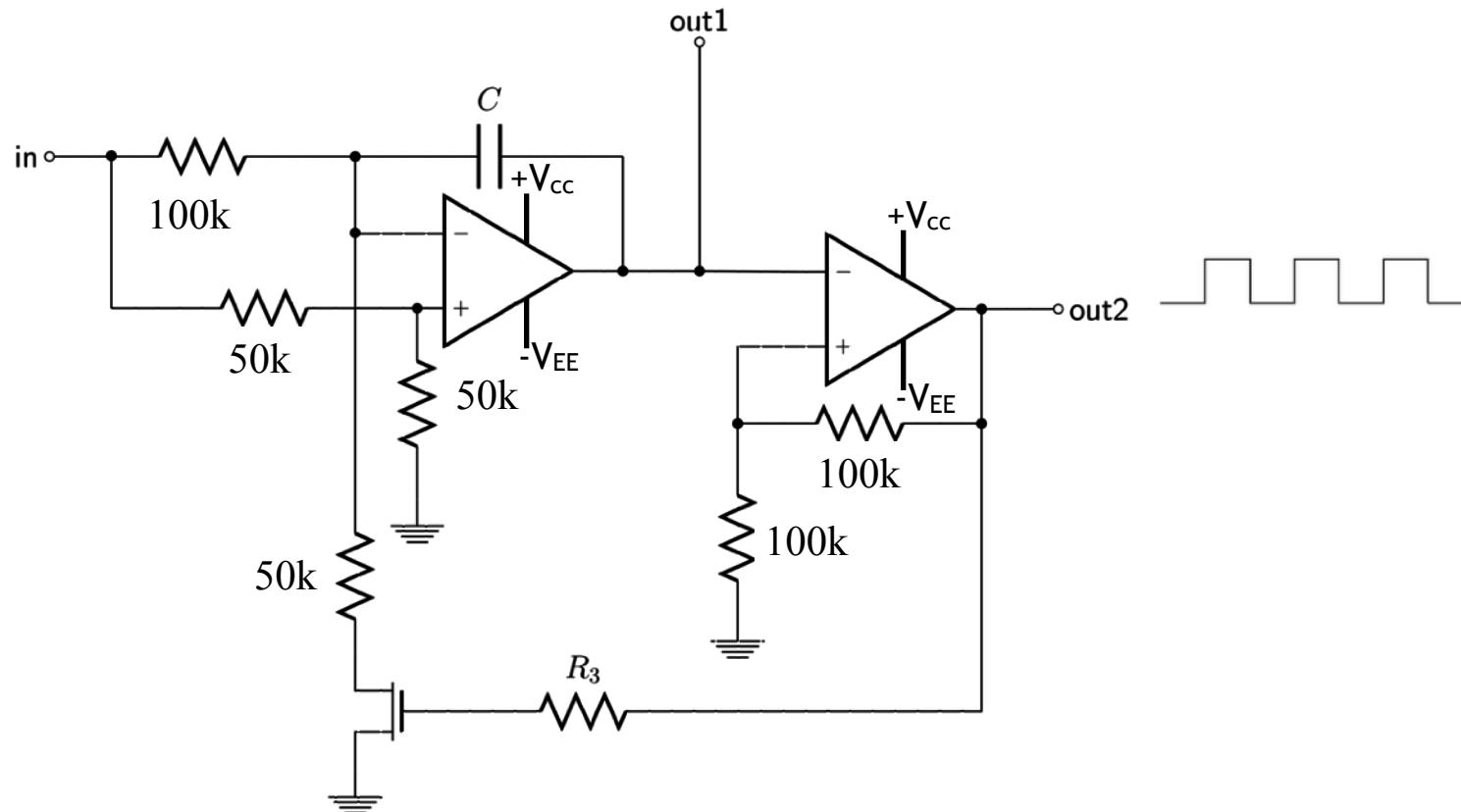
It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

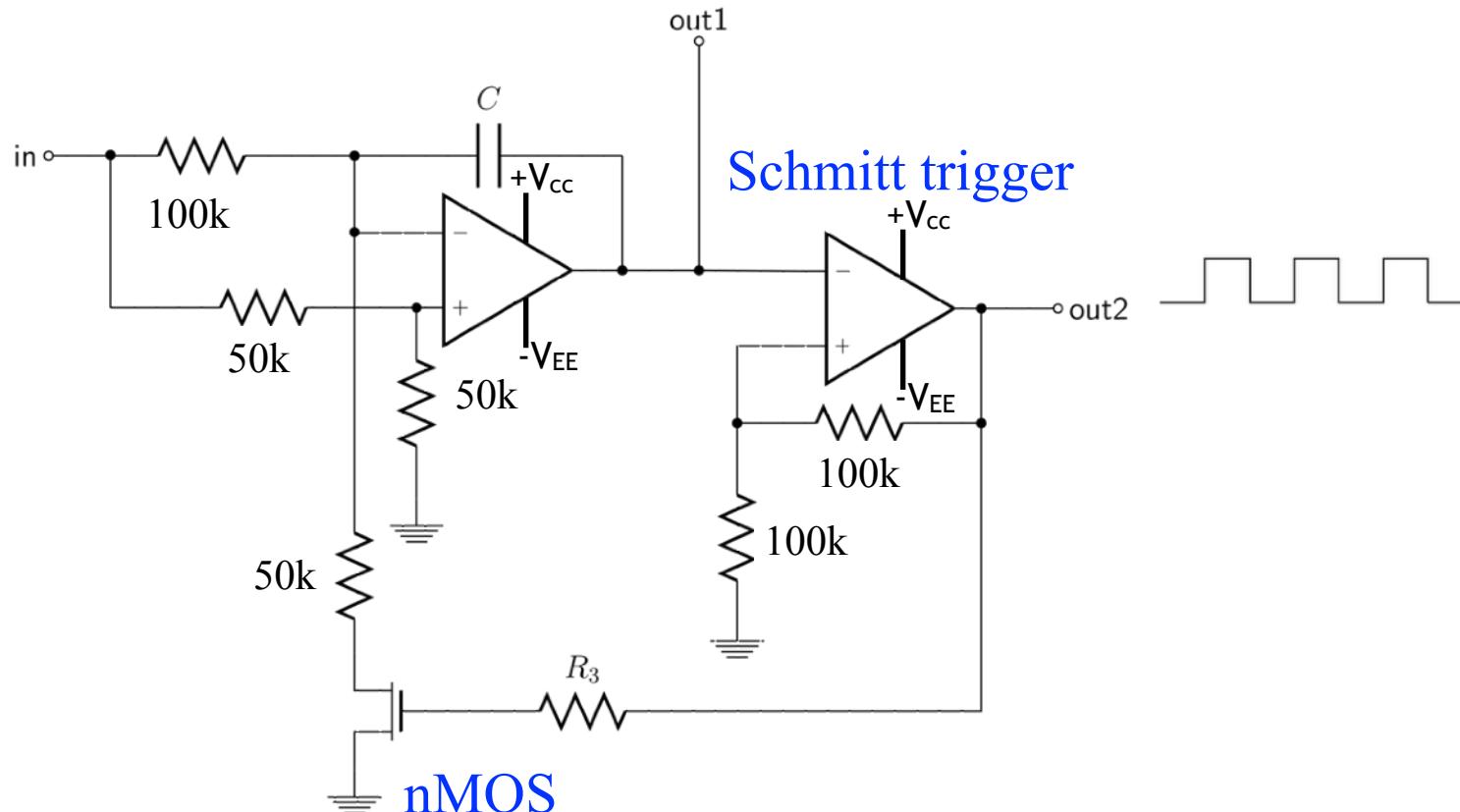Out2 is either high or low as output of comparator.



Out1 linearly ramps down until $\text{V}_{\text{EE}}/2$, then Out2 flips to V_{CC} .
Ramp rate proportional to V_{in} .


Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

Out2 is either high or low as output of comparator.

Integrator with

V_{in} control

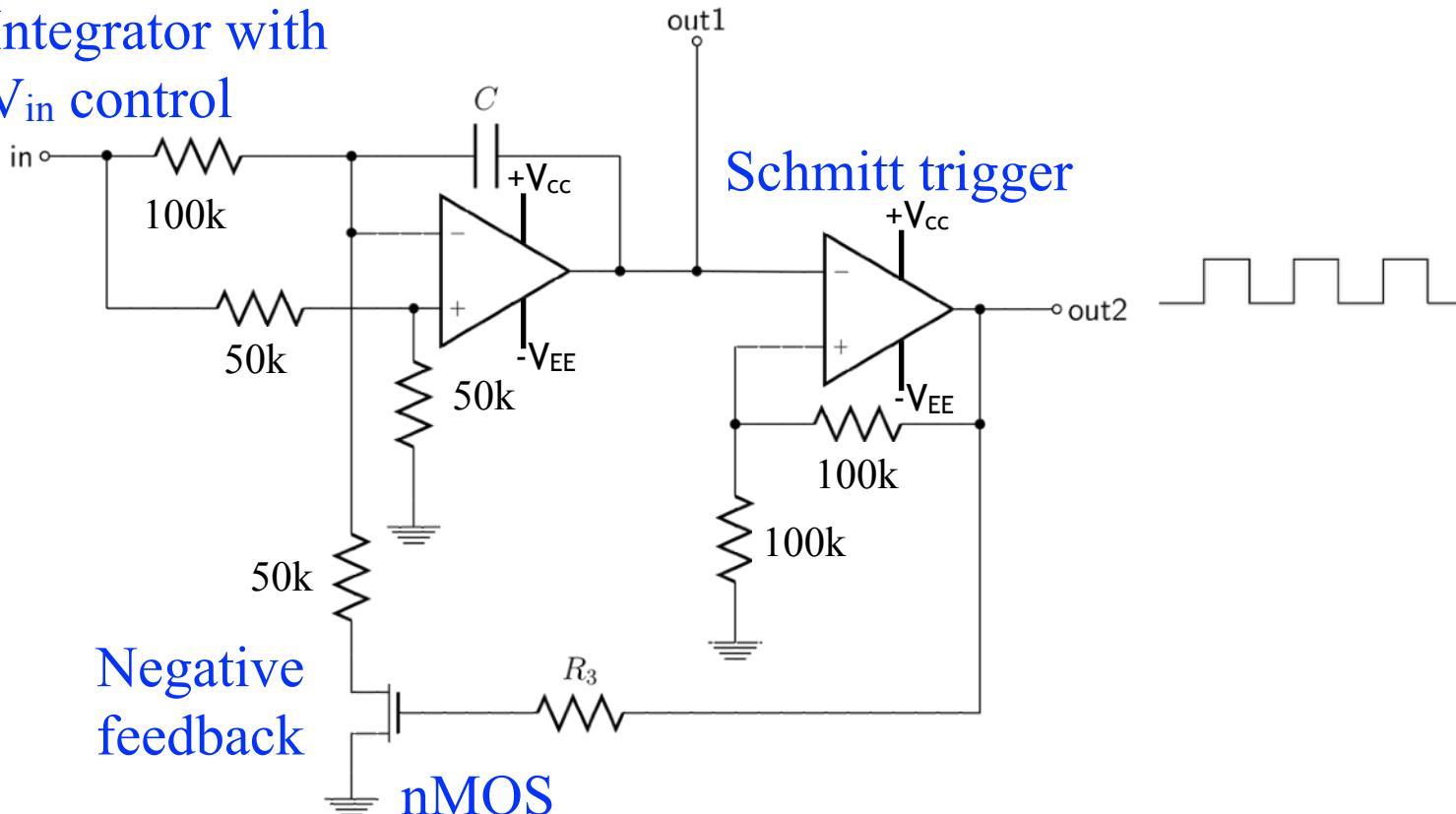


Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.


Out2 is either high or low as output of comparator.

Integrator with
 V_{in} control

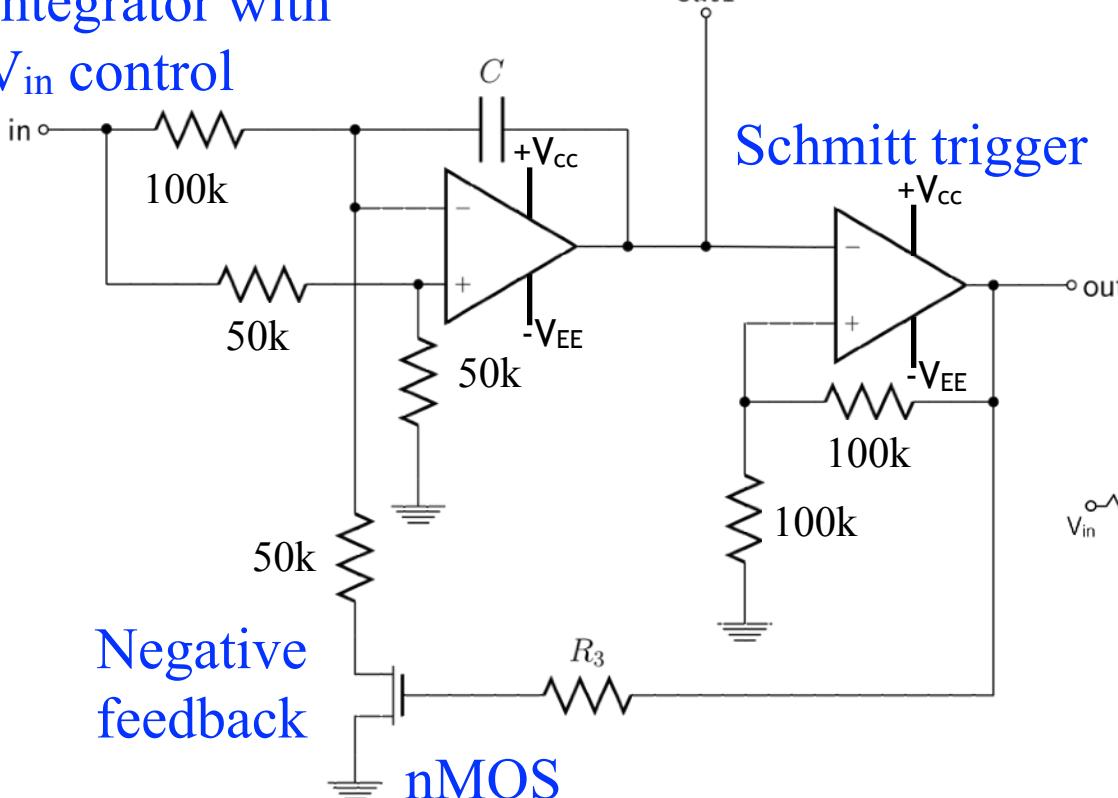

If Out1>0 & Out2=V_{EE},
then nMOS=off.

C charges as an integrator

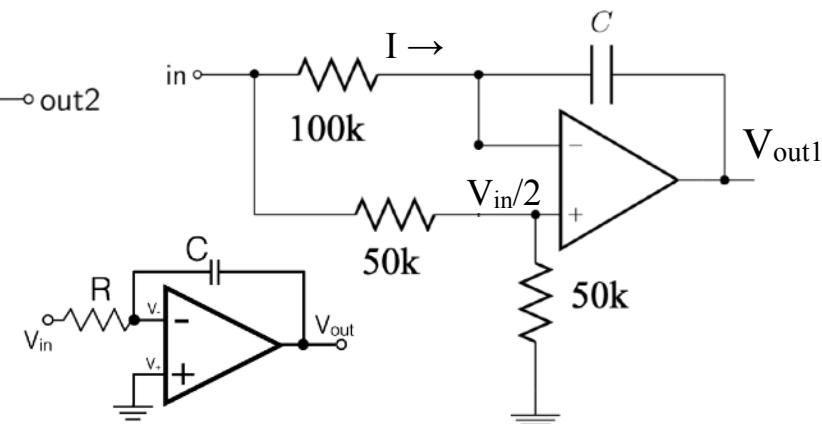

$$I = (V_{in} - V_{in}/2) / 100k = V_{in} / 200k$$

$$I = C \frac{dV}{dt} = V_{in} / 200k$$

$$C \frac{d(V_{in}/2 - V_{out1})}{dt} = V_{in} / 200k$$

$$C \frac{dV_{out1}}{dt} = -V_{in} / 200k$$


Out1 linearly ramps down until $V_{EE}/2$, then Out2 flips to V_{CC} .
Ramp rate proportional to V_{in} .

Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

Out2 is either high or low as output of comparator.

Integrator with
 V_{in} control

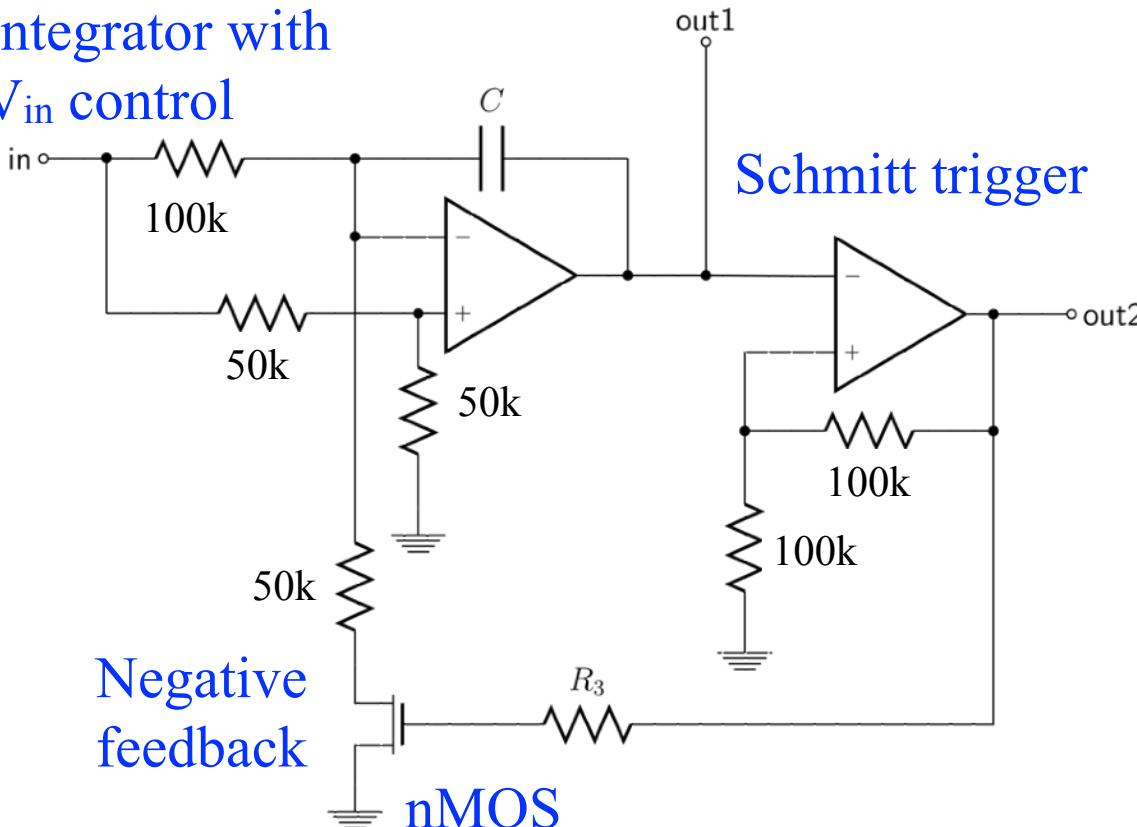


Negative
feedback

nMOS

Out1 linearly ramps up until $V_{CC}/2$, then Out2 flips to V_{EE} .
Ramp rate proportional to V_{in} .

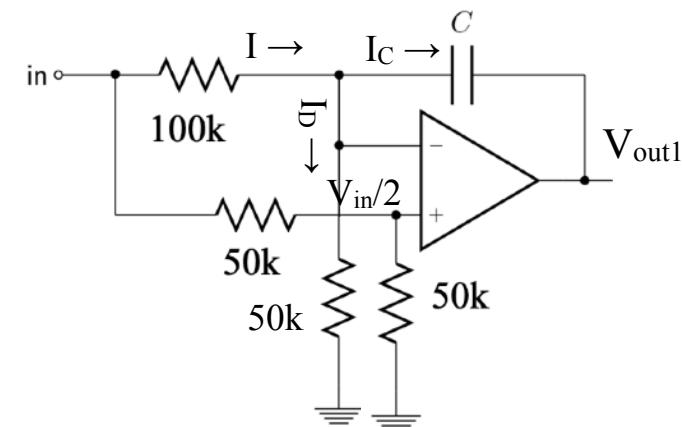If $Out1 < 0$ & $Out2 = V_{CC}$,
then nMOS=on.
C charges as an integrator



$$I = (V_{in} - V_{in}/2)/100k = V_{in}/200k$$

$$I_D = (V_{in}/2) / 50k = V_{in} / 100k$$

$$I_C = I - I_D = V_{in} (1/200k - 1/100k)$$


$$I_C = I - I_D = -V_{in}/200k$$

$$C \frac{d(V_{in}/2 - V_{out1})}{dt} = -V_{in} / 200k$$

$$C \frac{dV_{out1}}{dt} = V_{in} / 200k$$

Voltage controlled oscillator

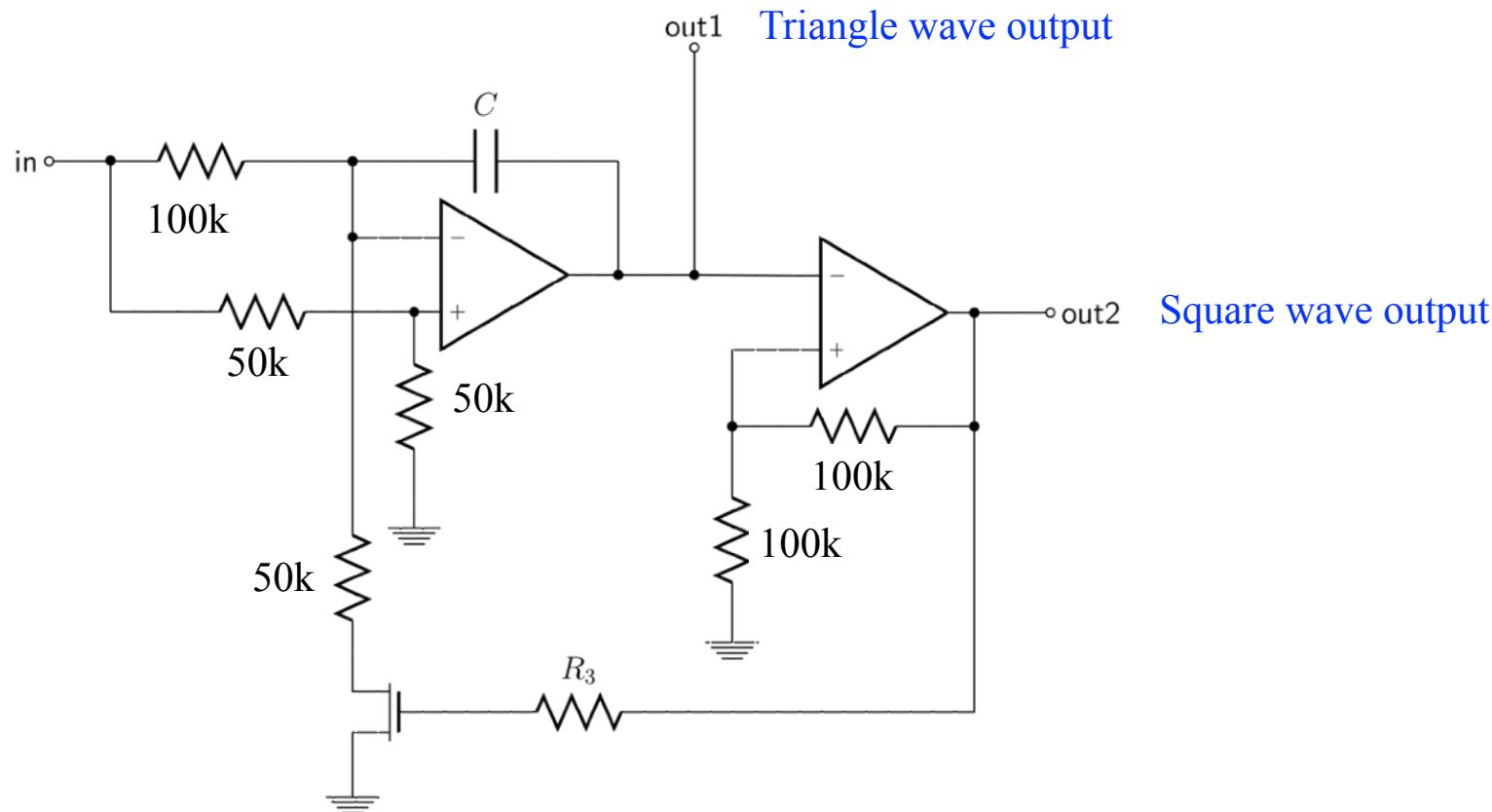
It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

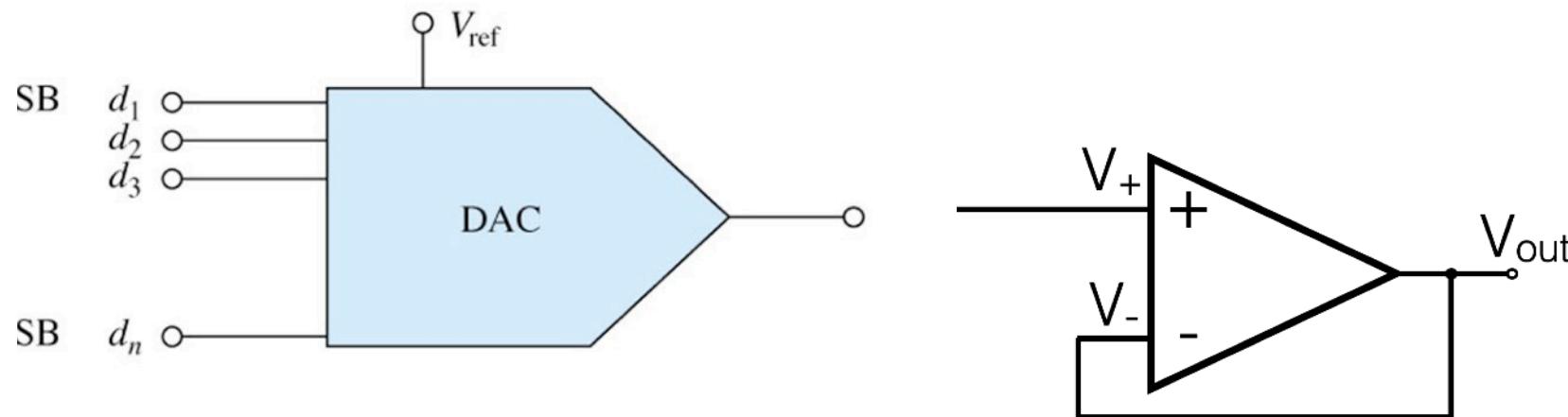
- 0). Use a computer to rapidly change the resistance in a digital potentiometer used in a voltage divider



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

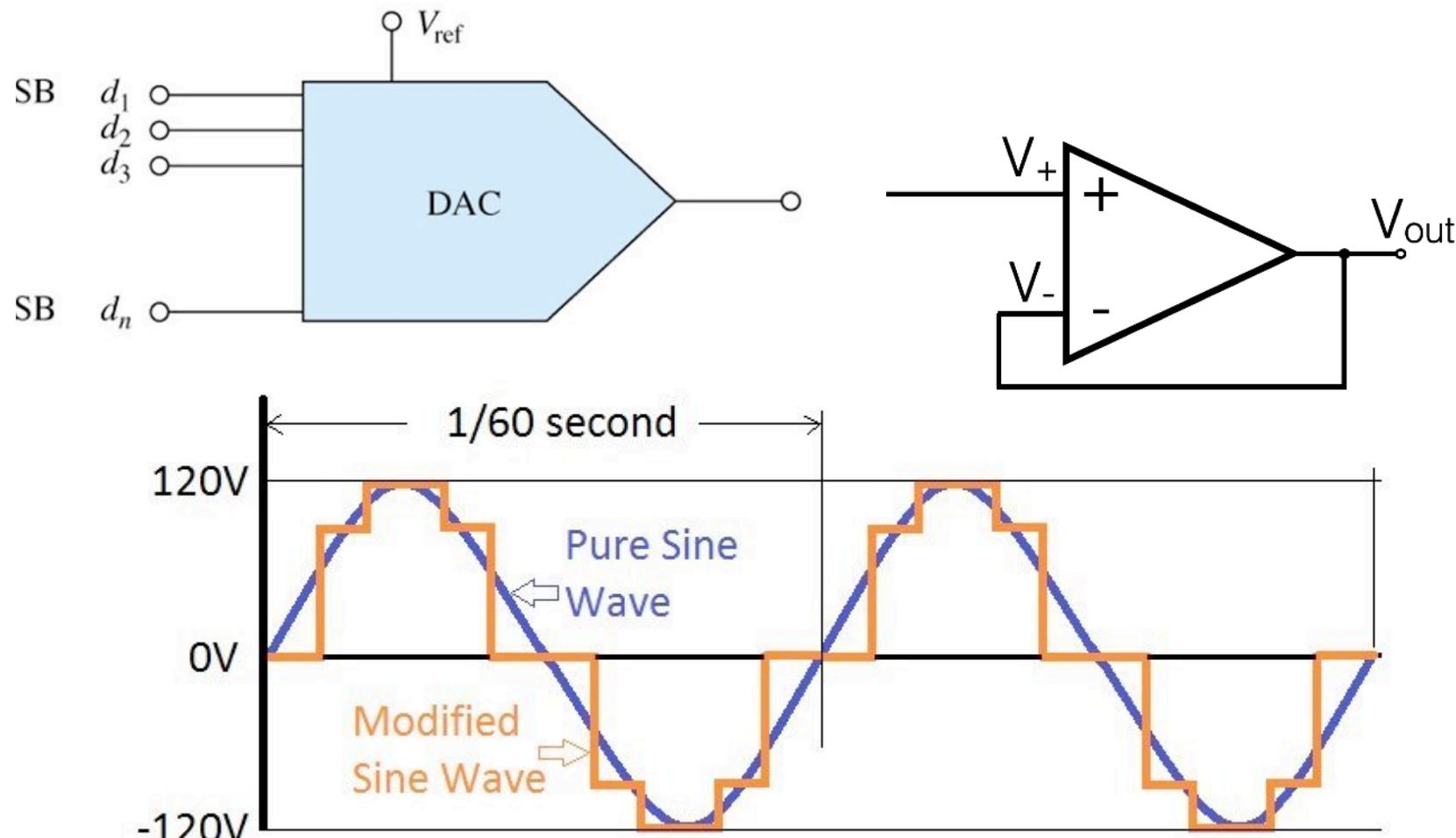- 0). Use a computer to rapidly change the resistance in a digital potentiometer used in a voltage divider



Sine wave oscillator



We could get a sine wave oscillator in a few ways:

- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance

Sine wave oscillator

We could get a sine wave oscillator in a few ways:


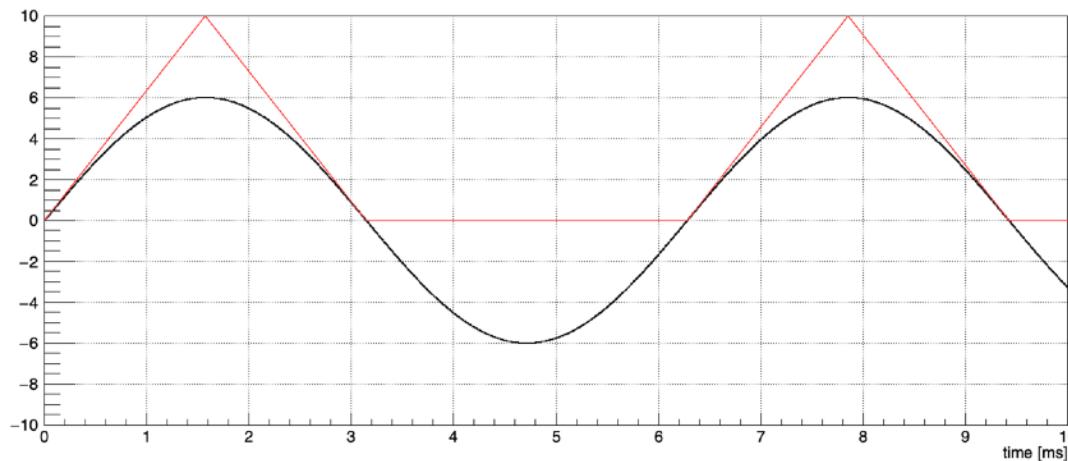
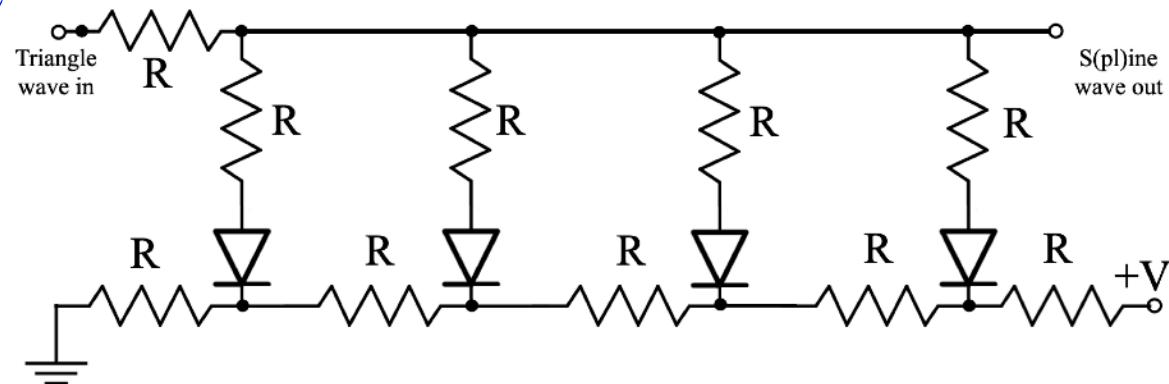
- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

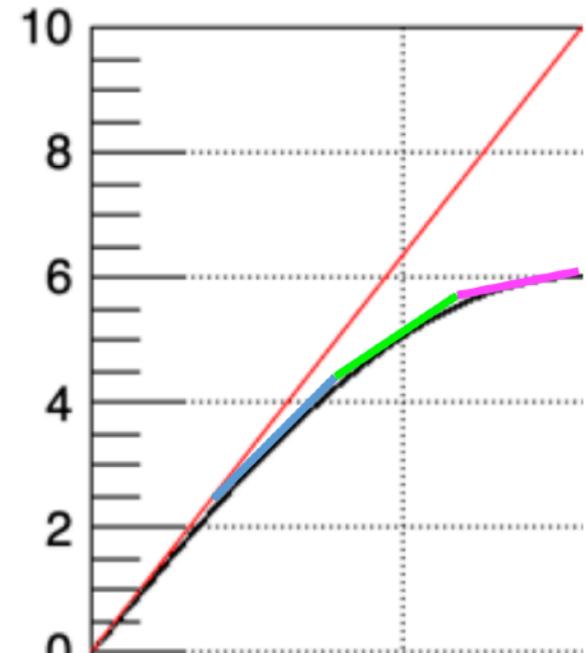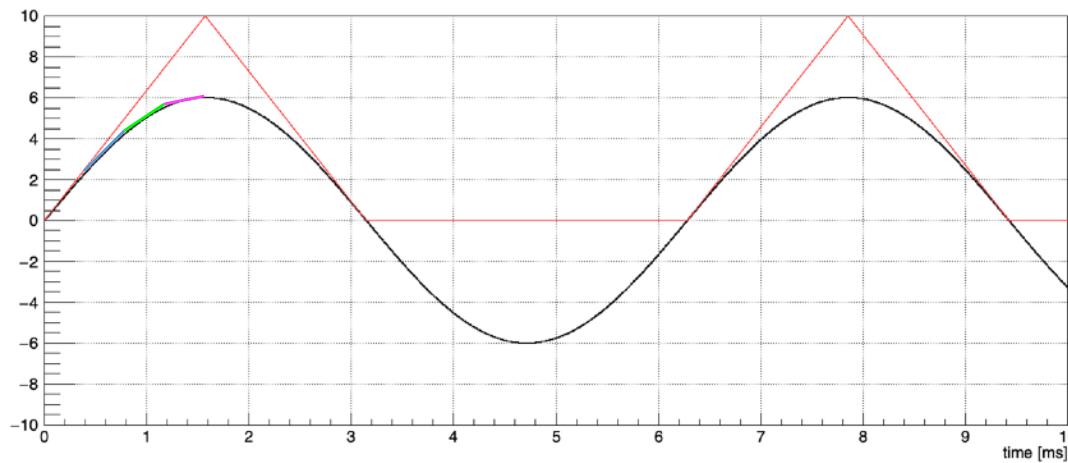
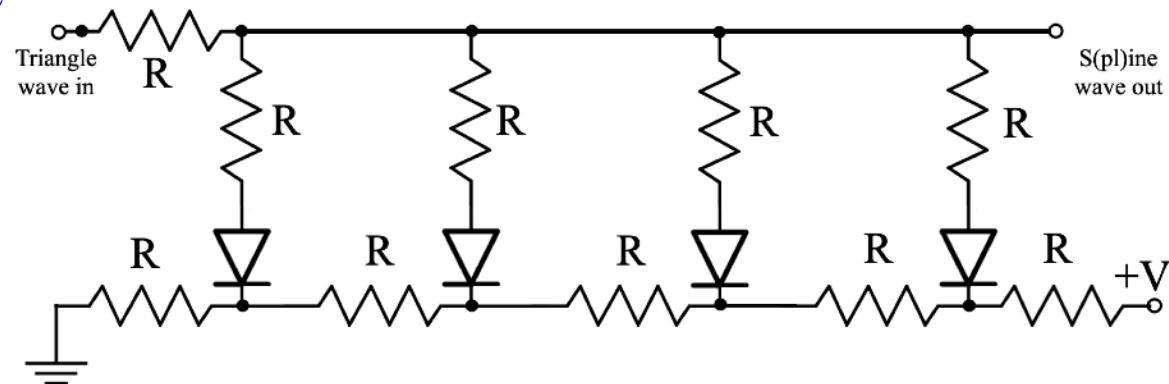
- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

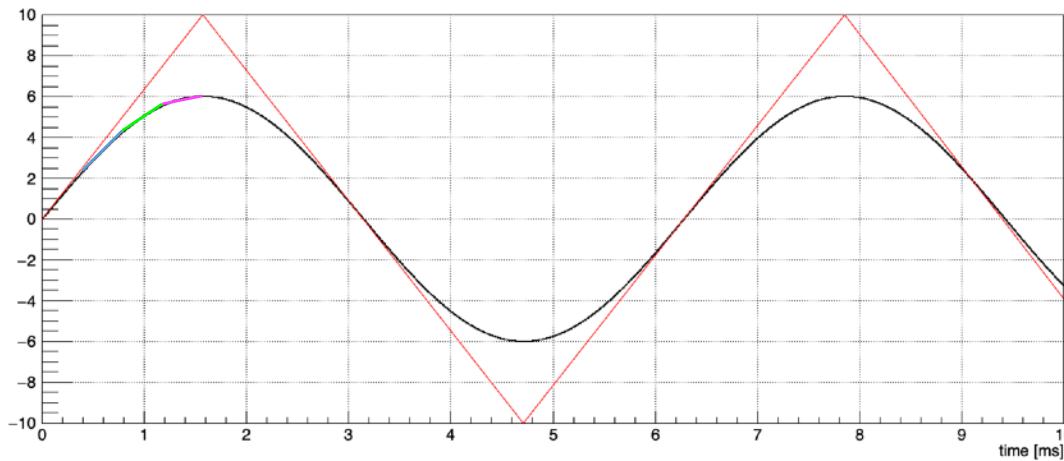
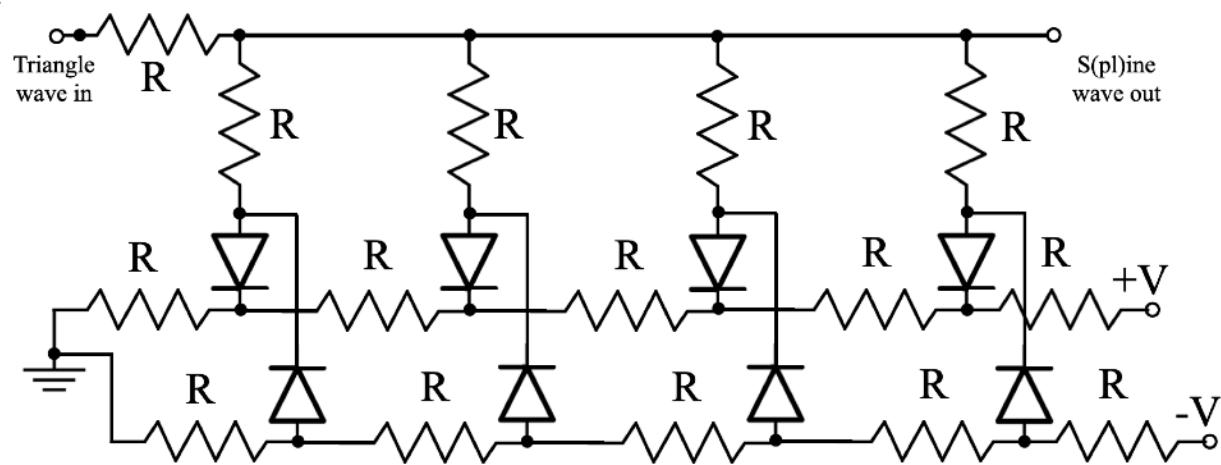
- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

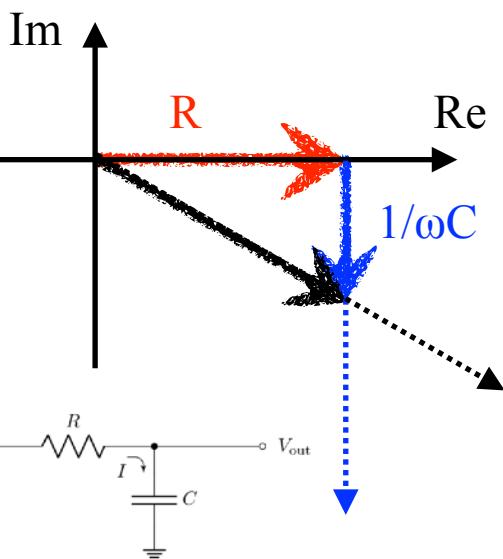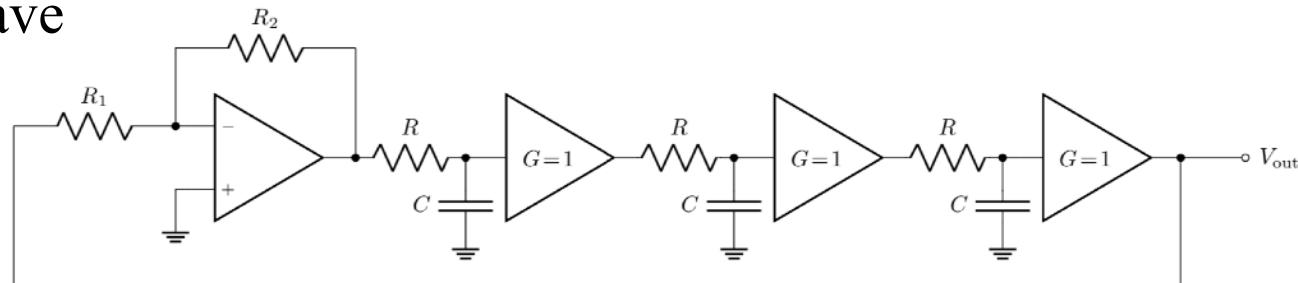- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance



Initially have an inverting amp, then RC filters that phase shift. At just the right frequency, $\omega = \frac{\sqrt{3}}{RC}$, they each have 60° phase shift.

So net effect is 180° so another inverter. Positive feedback at the resonant ω .


Lose a factor of $\frac{1}{\sqrt{1 + (\omega RC)^2}} = 1/2$ at each step.

So $R_2/R_1 = 8$ to get stable oscillation.

Sine wave from Wien bridge oscillator

We could get a sine wave oscillator in a few ways:

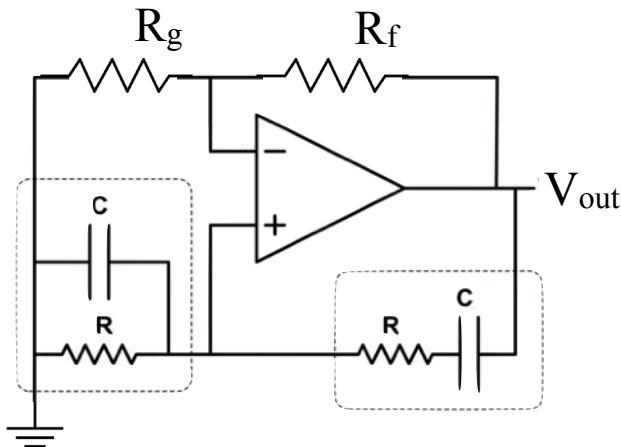- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance




The CR-RC are a hi&low pass filter.
At $\omega=1/RC$, phase shift at V_+ is 0°
so positive feedback, and $V_+ = V_{\text{out}}/3$.
If we could finely adjust $R_g = R_f/2$ to get the non-inverting amp gain of $G = 1+R_f/R_g = 3$, net gain=1.

Sine wave from Wien bridge oscillator

We could get a sine wave oscillator in a few ways:

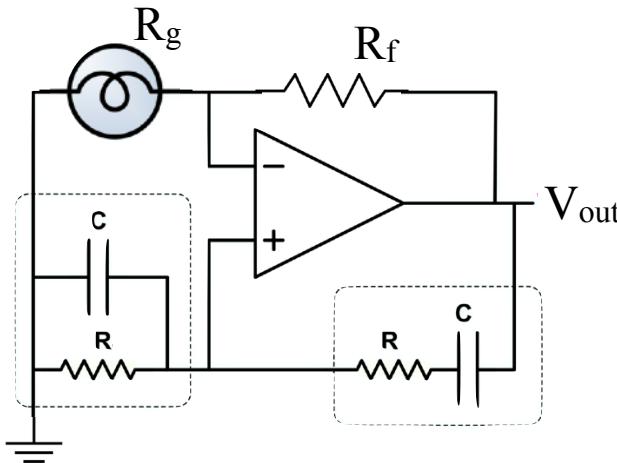- 1). Filter square wave with low-pass filter: $f(x) = \sin(x) + \sin(3x)/3 + \sin(5x)/5 + \dots$
- 2). Chop the triangle wave
- 3). Tune resonance



The CR-RC are a hi&low pass filter.

At $\omega=1/RC$, phase shift at V_+ is 0°

so positive feedback, and $V_+ = V_{out}/3$.

If we could finely adjust $R_g = R_f/2$ to get the non-inverting amp gain of $G = 1 + R_f/R_g = 3$, net gain=1.

Do this with thermal negative feedback using a lamp.
A lamp's resistance is low at low temperature and increases as its temperature increases.



If V_{out} gets too big, more current flows through R_g , which increases R_g , which decreases the gain and hence decreases V_{out} . Negative feedback.

If V_{out} gets too small, less current flows through R_g , which decreases R_g , which increases the gain and hence increases V_{out} . Negative feedback.

Equilibrium at just the right gain to oscillate at $\omega=1/RC$.

Piezo-buzzer

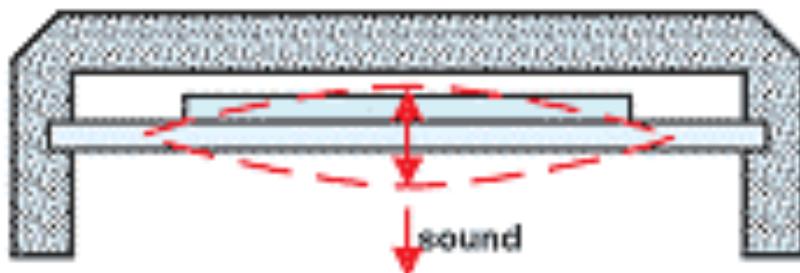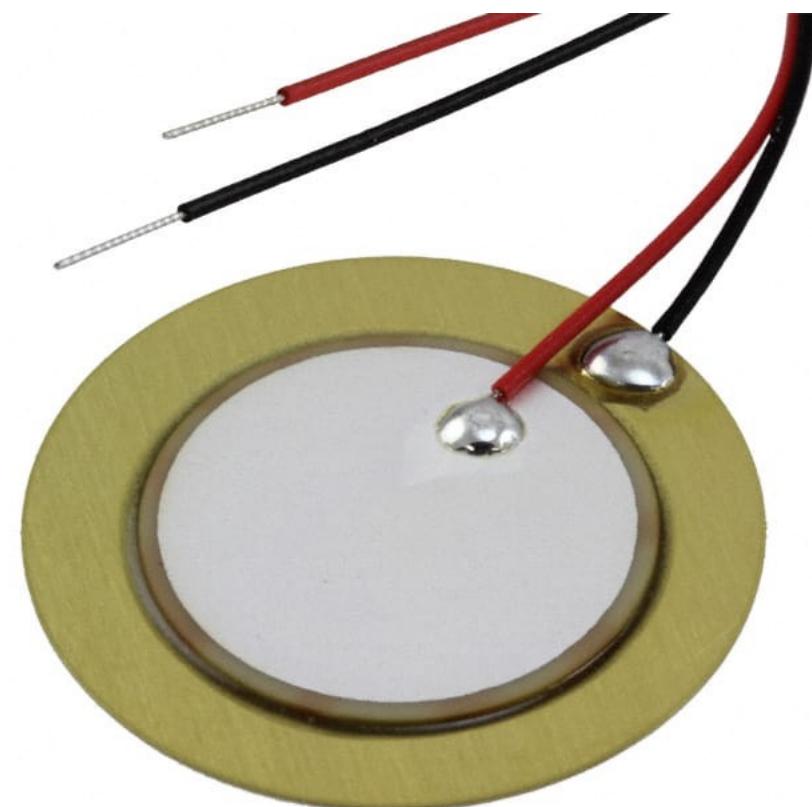The buzzer you will use in lab this week is not a speaker.
It is just a mechanical resonator, with thin ceramic and metal disks.
The ceramic deforms due to the electric field of an applied voltage.
Small ceramic deformations cause larger vibrations in the metal disk.



Quartz crystal oscillator

The resonant frequency depends on the size and tension.


To get very high resonant frequency, need a small & stiff material \Rightarrow quartz.



Quartz crystal oscillator

The resonant frequency depends on the size and tension.

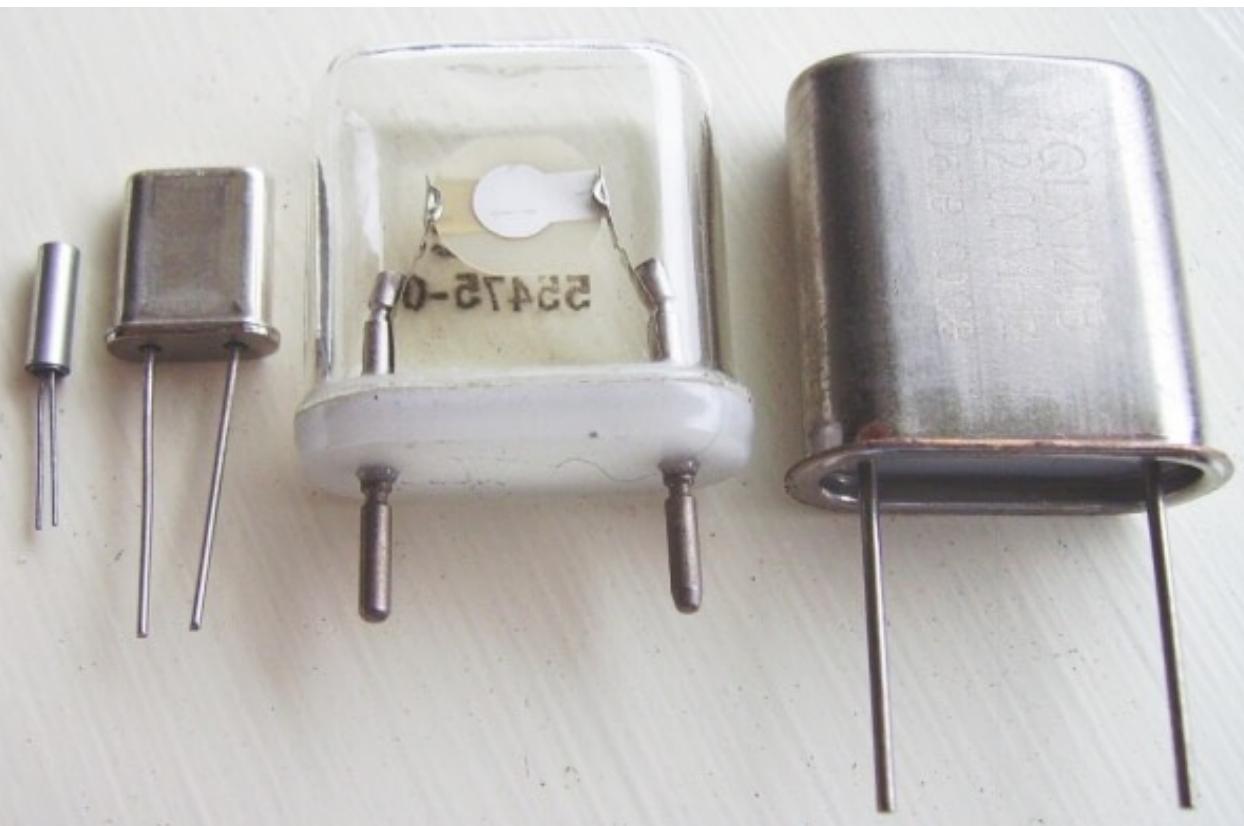
To get very high resonant frequency, need a small & stiff material \Rightarrow quartz.



Quartz crystal oscillator

The resonant frequency depends on the size and tension.

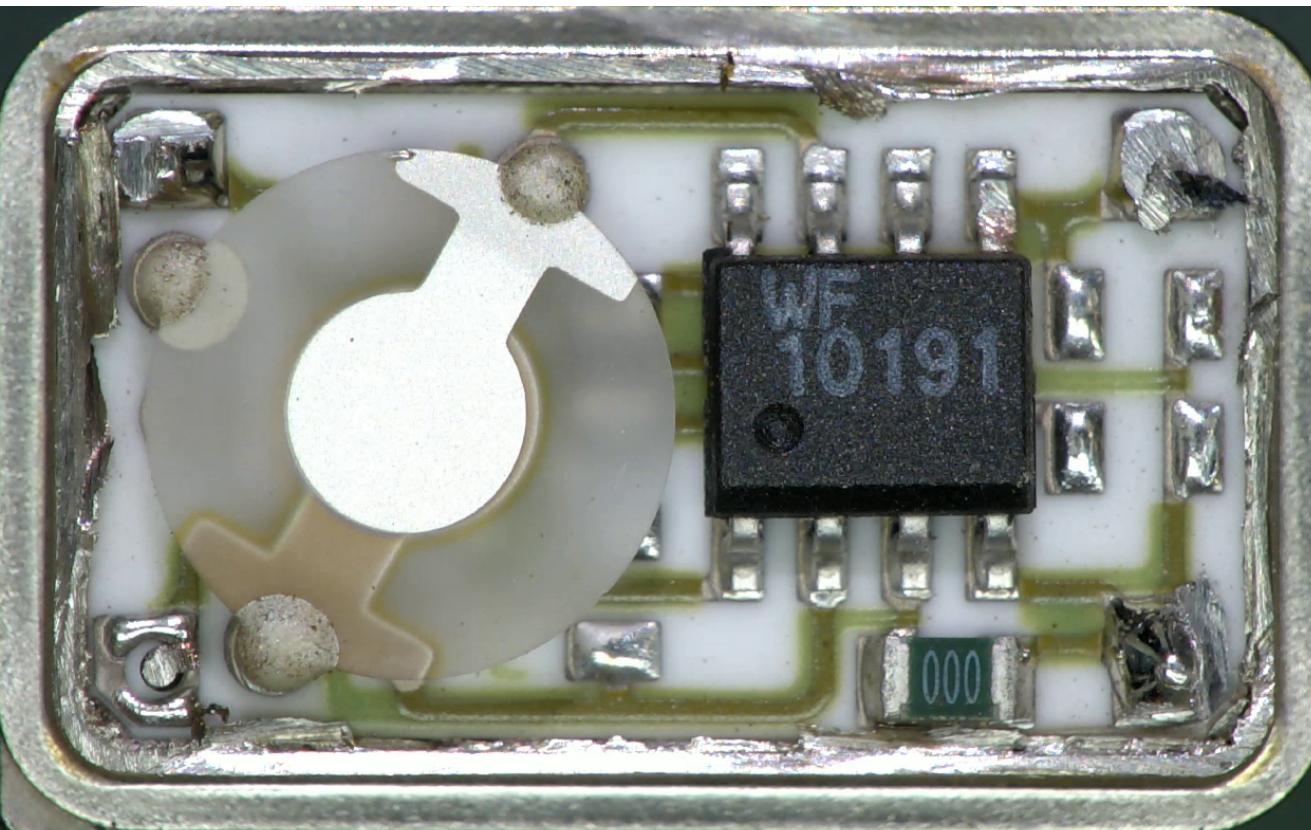To get very high resonant frequency, need a small & stiff material \Rightarrow quartz.




Can get high frequencies, with higher harmonics of resonance.

High Q oscillators so can get low drift. Temperature compensation helps.

Oscillator performance

A measure of oscillator performance is the frequency drift and phase jitter.


"Eye diagram":

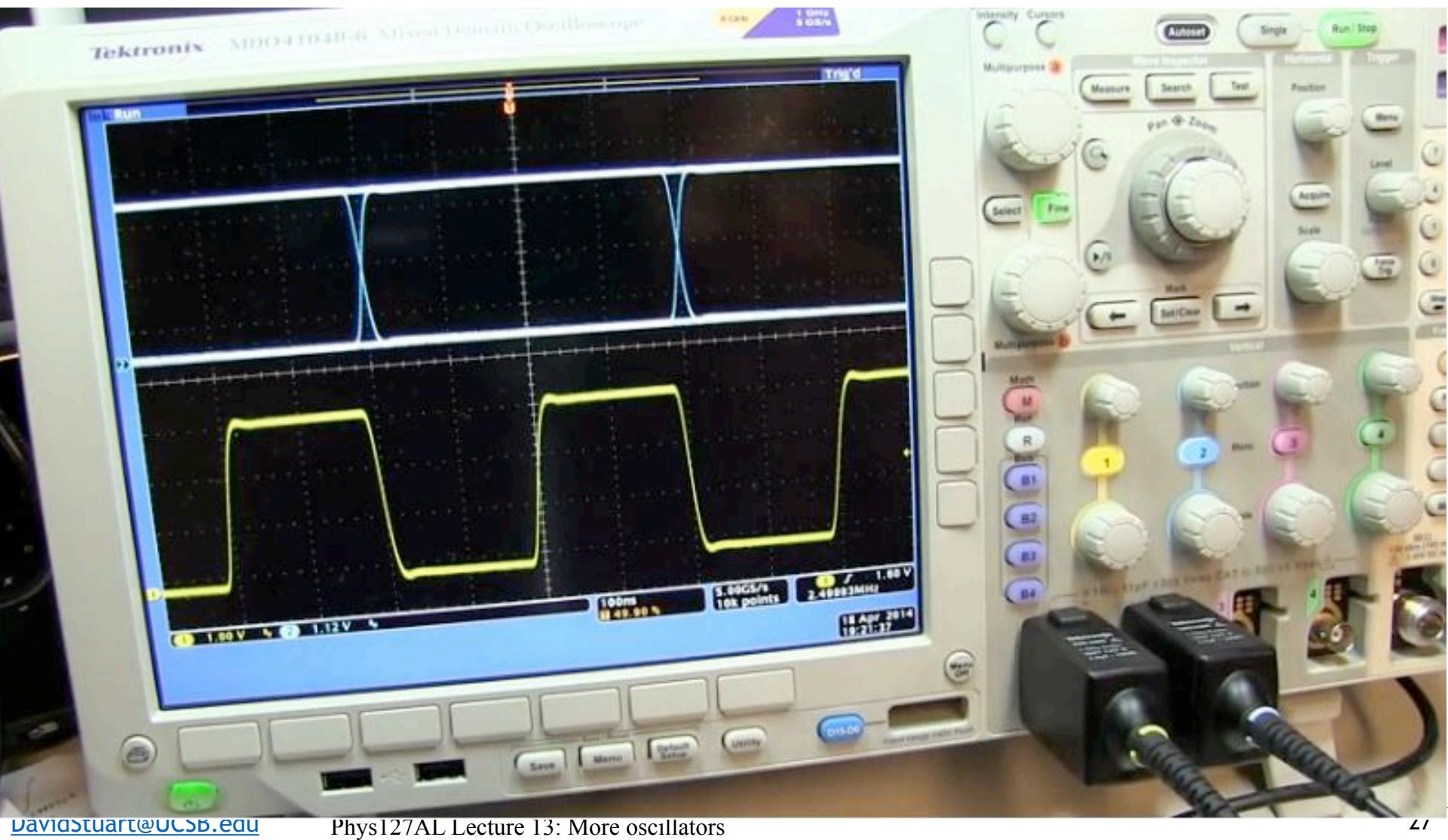

Oscillator performance

A measure of oscillator performance is the frequency drift and phase jitter.


"Eye diagram":

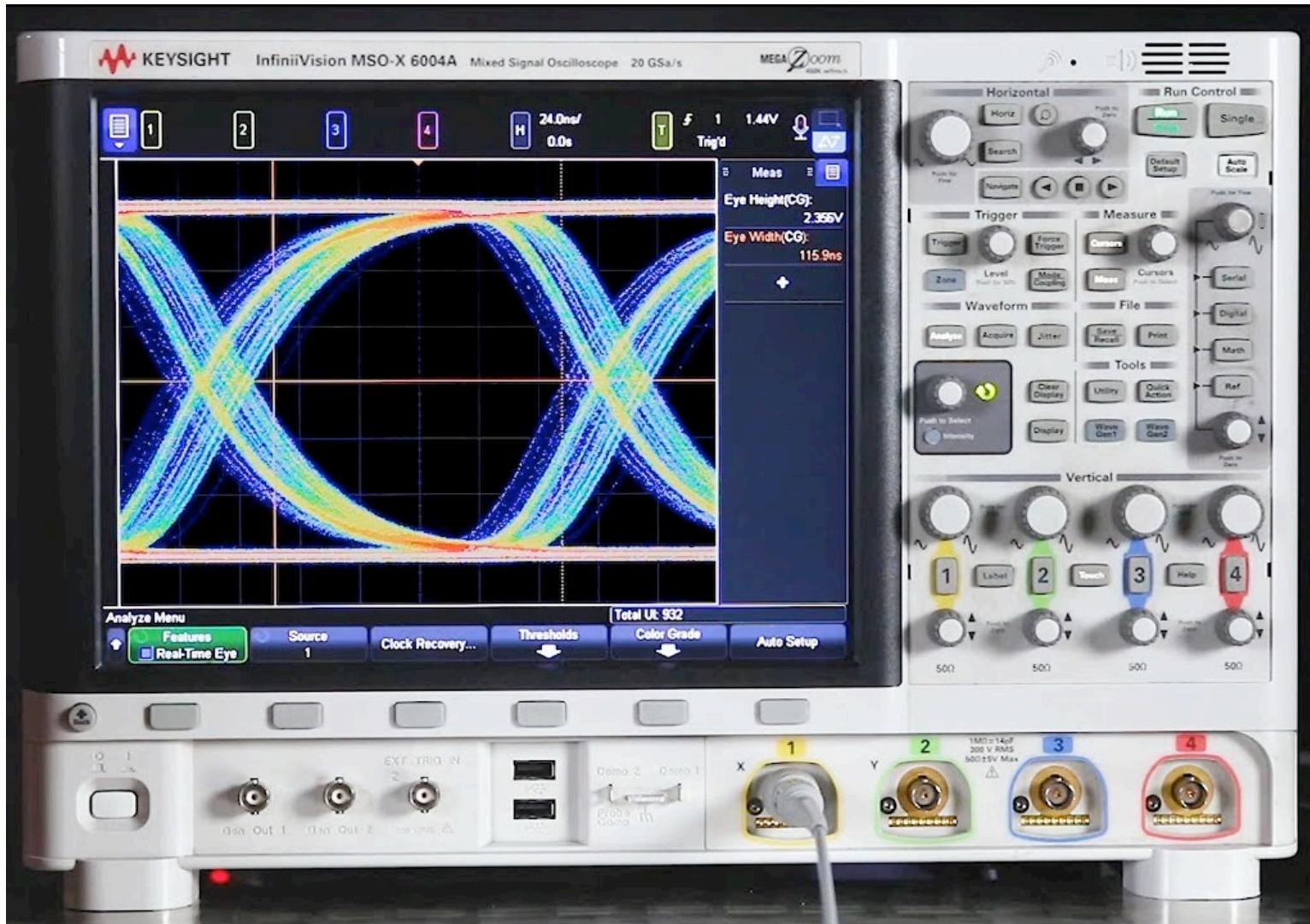

Oscillator performance


A measure of oscillator performance is the frequency drift and phase jitter.

"Eye diagram":


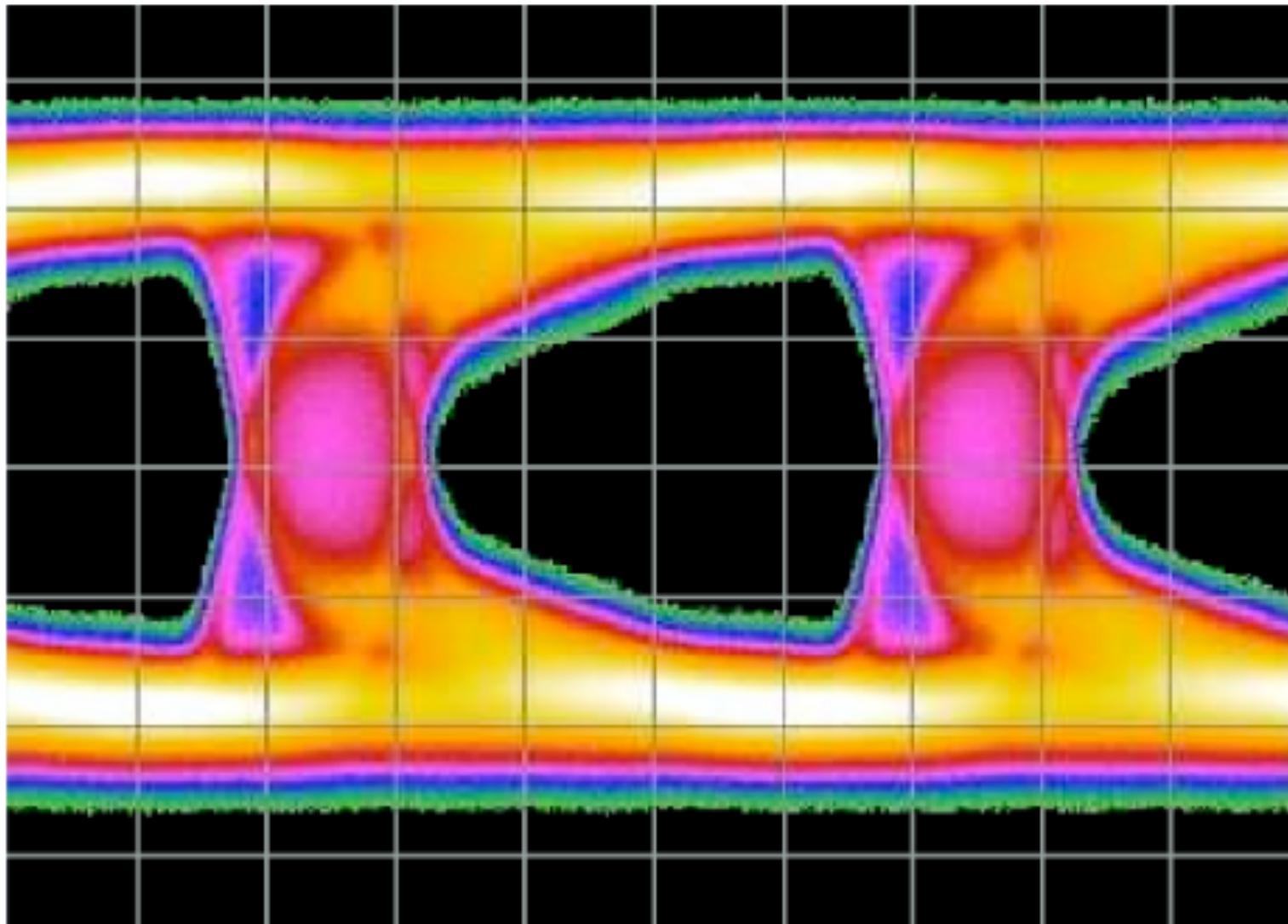


Open collector comparator

Recall that comparator ICs differ from a simple op-amp wired as a comparator.

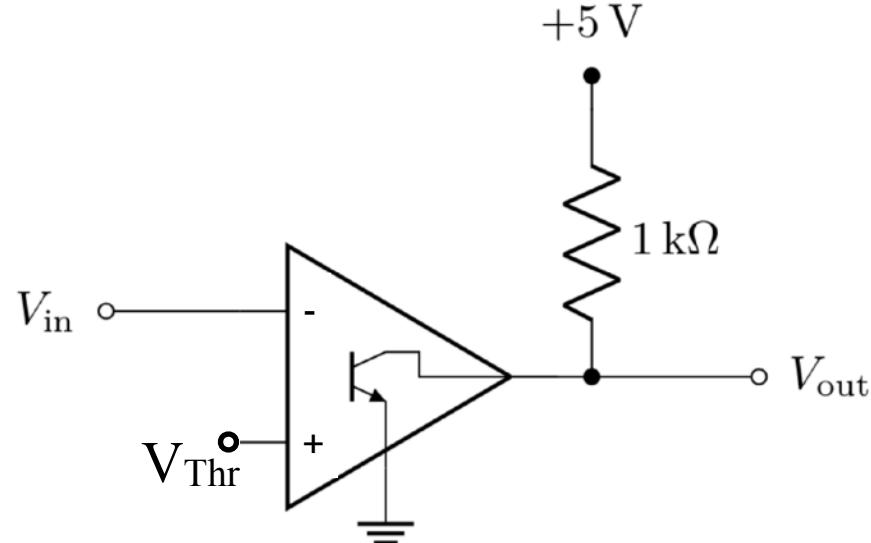

LM311

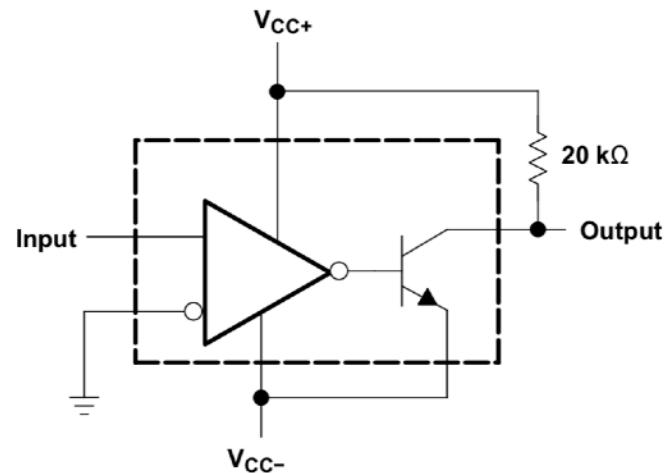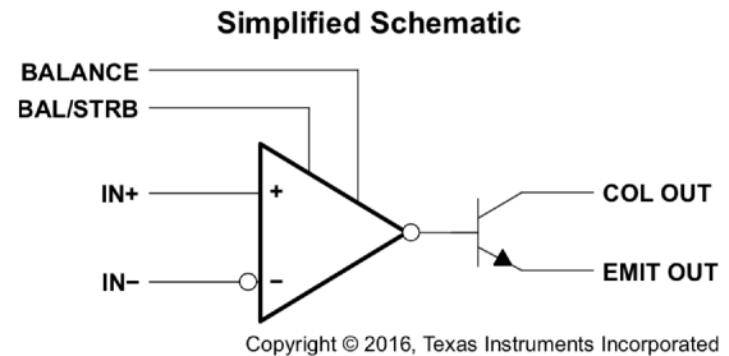


Copyright © 2016, Texas Instruments Incorporated

Figure 13. Zero-Crossing Detector


Differential amplifier

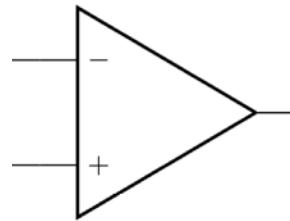The op-amp is a huge gain differential amplifier. We can get controlled differential amplification with negative feedback using...



Differential amplifier

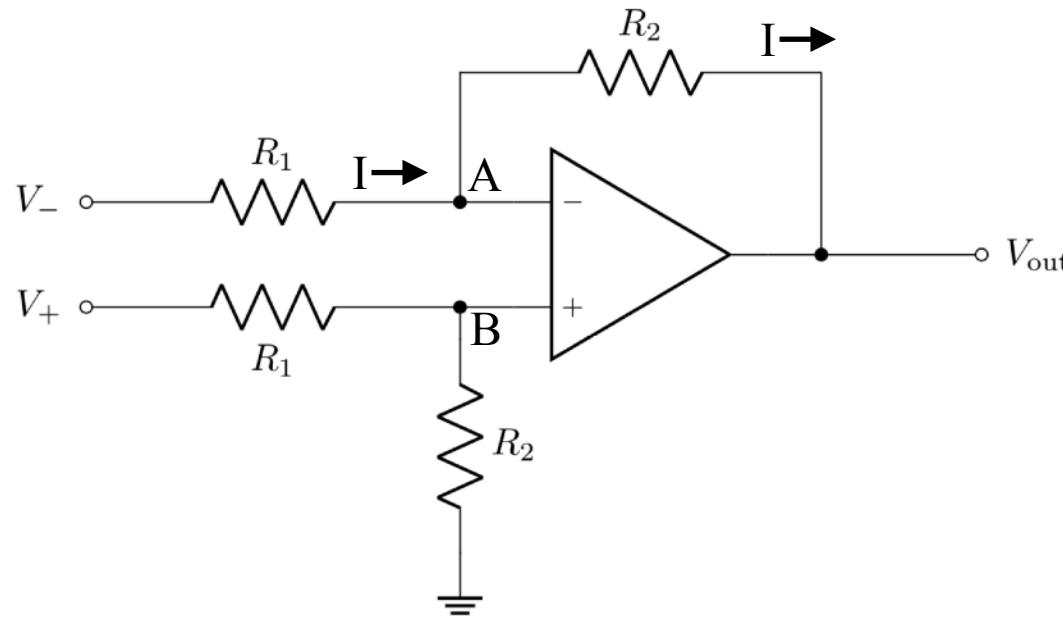The op-amp is a huge gain differential amplifier. We can get controlled differential amplification with negative feedback using this circuit.



$$V_B = V_+ R_2 / (R_1 + R_2) = V_A$$

$$I = (V_- - V_A) / R_1$$


$$V_{out} = V_A - I R_2$$

$$\begin{aligned} V_{out} &= V_+ R_2 / (R_1 + R_2) - (V_- - V_A) R_2 / R_1 \\ &= R_2 [V_+ / (R_1 + R_2) - V_- / R_1 + V_+ R_2 / R_1 (R_1 + R_2)] \\ &= R_2 [V_+ (1 + R_2 / R_1) / (R_1 + R_2) - V_- / R_1] \\ &= R_2 [V_+ (R_1 / R_1 + R_2 / R_1) / (R_1 + R_2) - V_- / R_1] \\ &= R_2 [V_+ / R_1 - V_- / R_1] \\ &= (V_+ - V_-) R_2 / R_1 \end{aligned}$$

An optimal, general purpose differential amplifier

Ideally, we would “buffer” the inputs and precisely match the resistors.



Worth making this a standard IC.

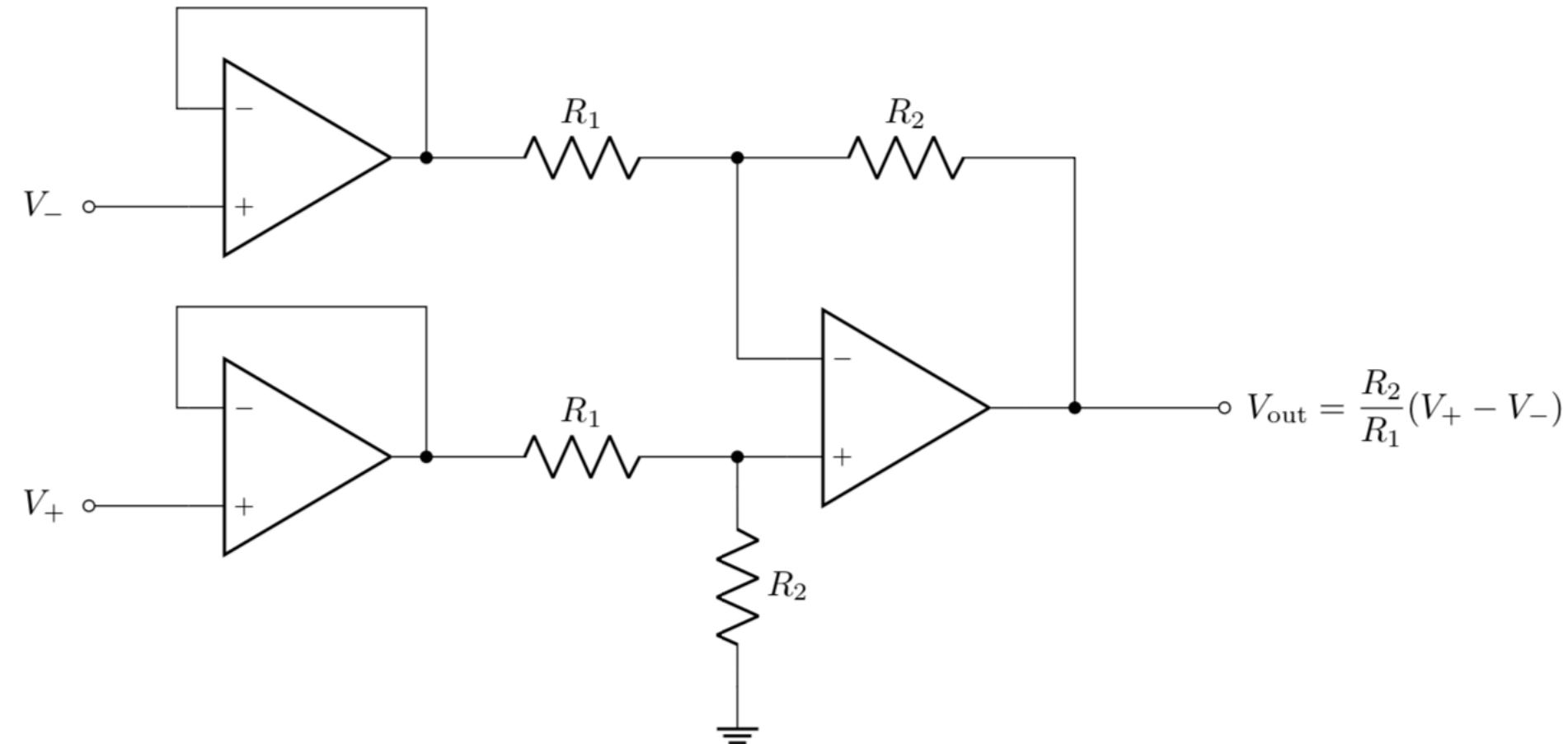

An optimal, general purpose differential amplifier

Ideally, we would “buffer” the inputs and precisely match the resistors.

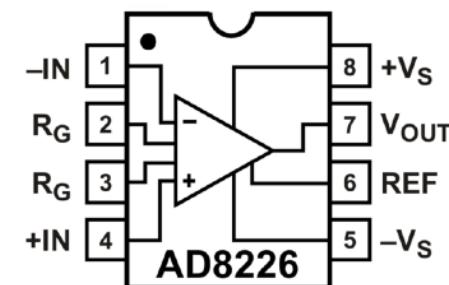
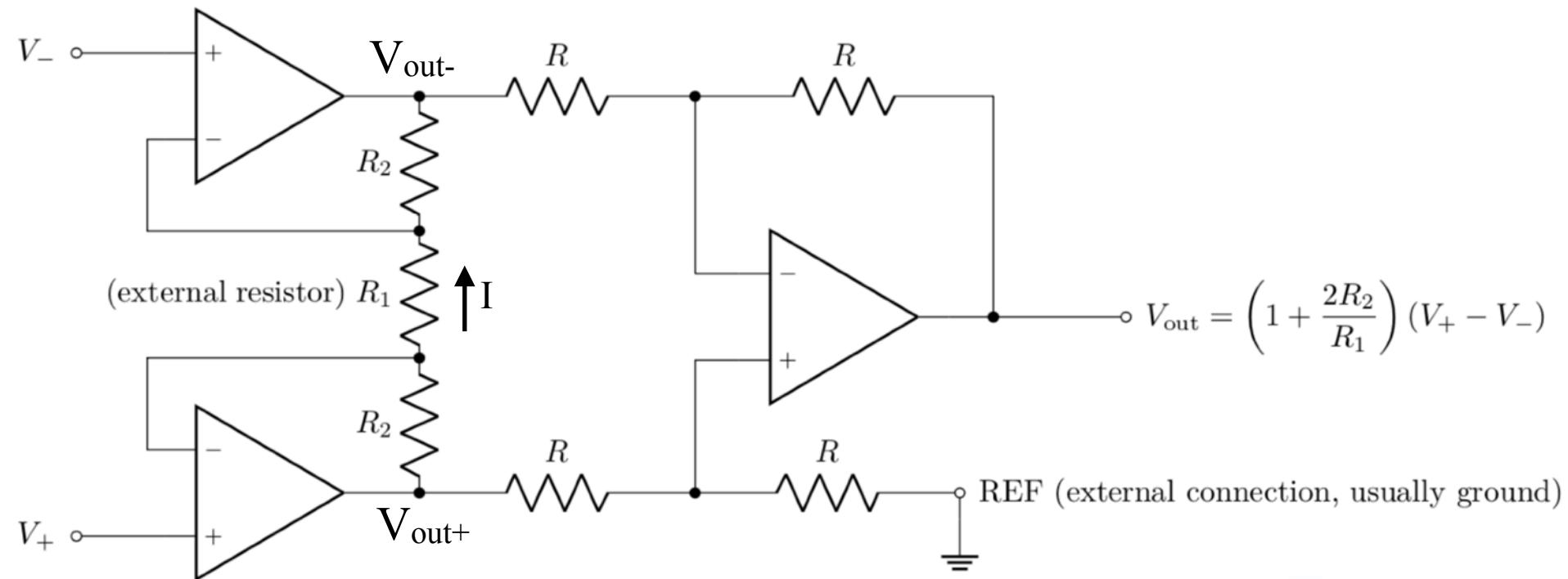
Worth making this a standard IC. Called an “instrumentation amp”.



An optimal, general purpose differential amplifier

Ideally, we would “buffer” the inputs and precisely match the resistors.

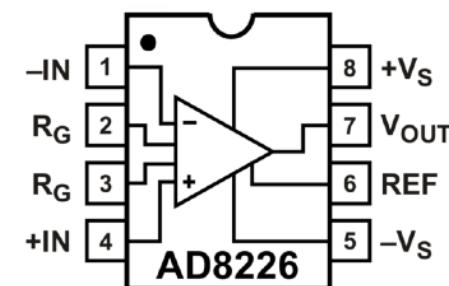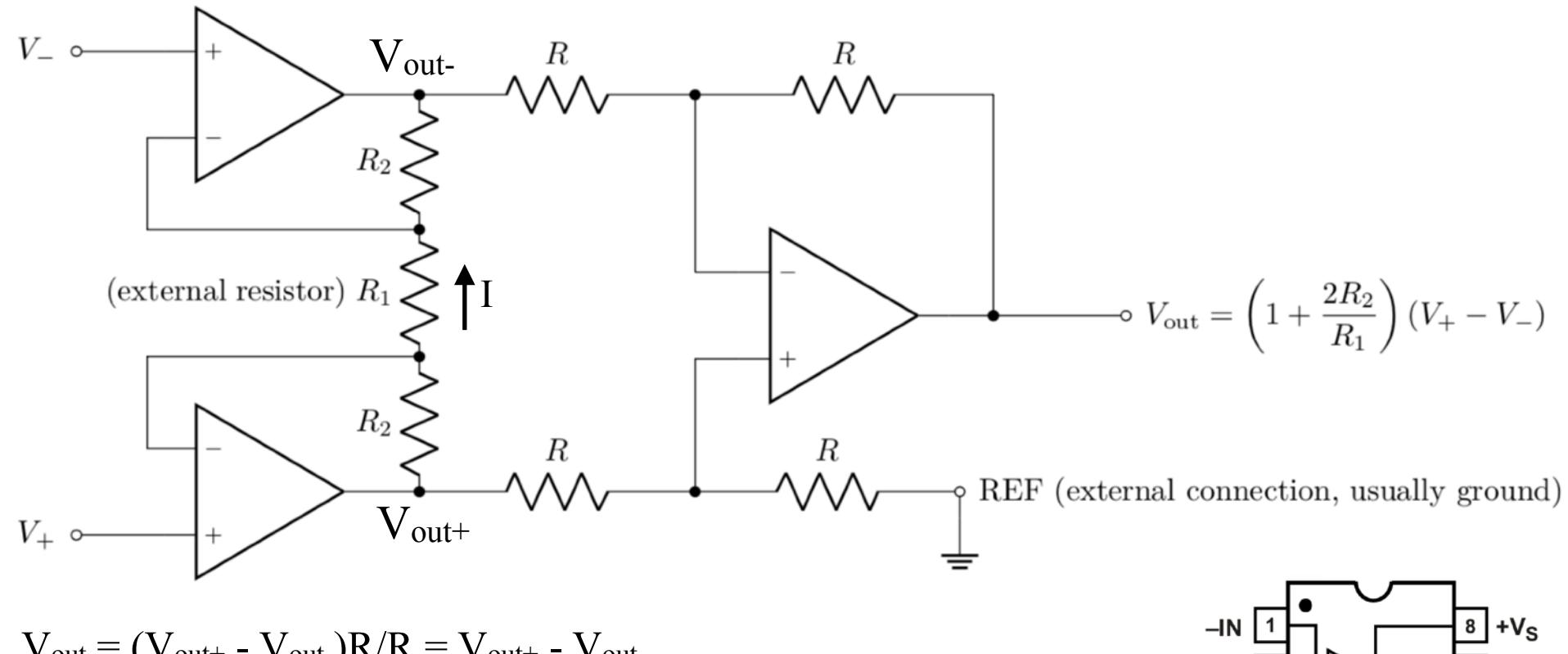
Worth making this a standard IC. Called an “instrumentation amp”.



An optimal, general purpose differential amplifier

Ideally, we would “buffer” the inputs and precisely match the resistors.

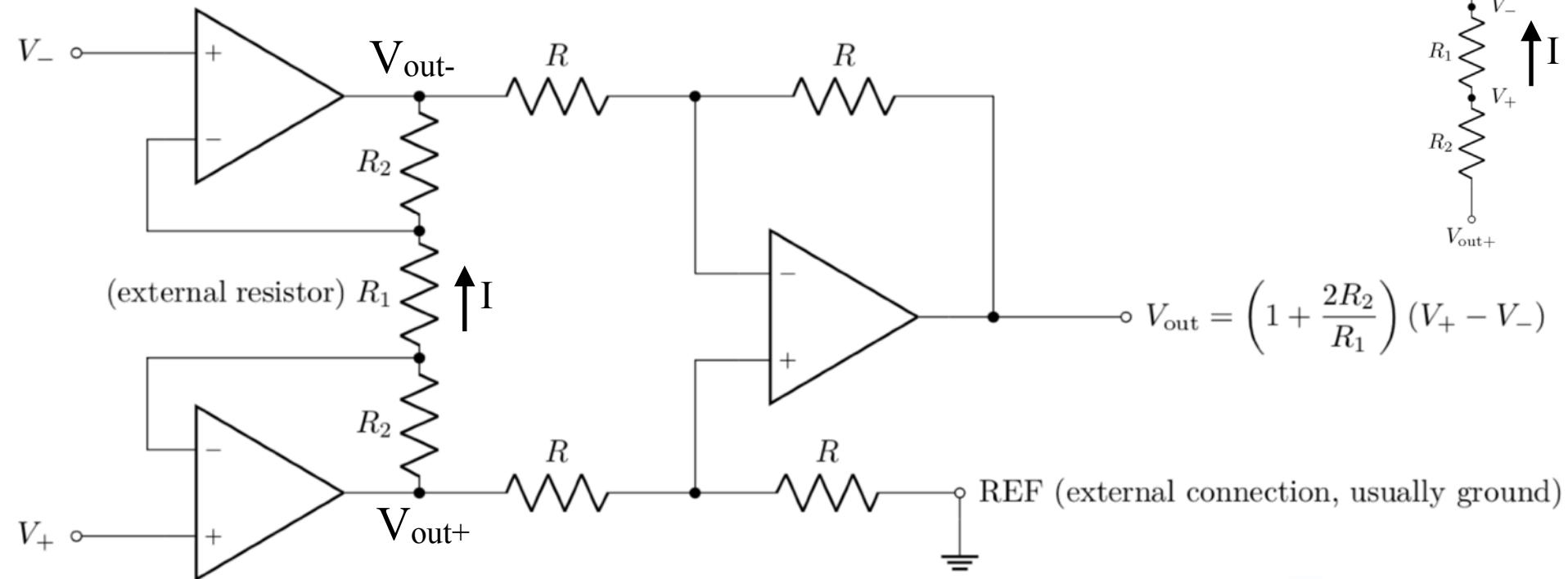Worth making this a standard IC. Called an “instrumentation amp”.




$$V_{out} = (V_{out+} - V_{out-})R/R = V_{out+} - V_{out-}$$

$$I = (V_+ - V_-)/R_1$$


$$V_{out+} = V_+ + I R_2 \quad \text{and} \quad V_{out-} = V_- - I R_2$$
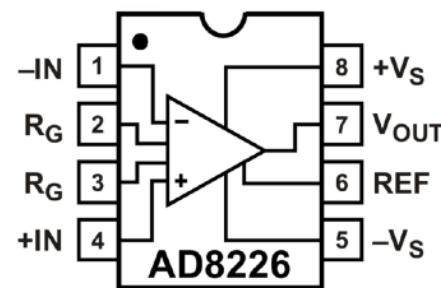
$$V_{out} = \left(1 + \frac{2R_2}{R_1}\right)(V_+ - V_-)$$



Mobility

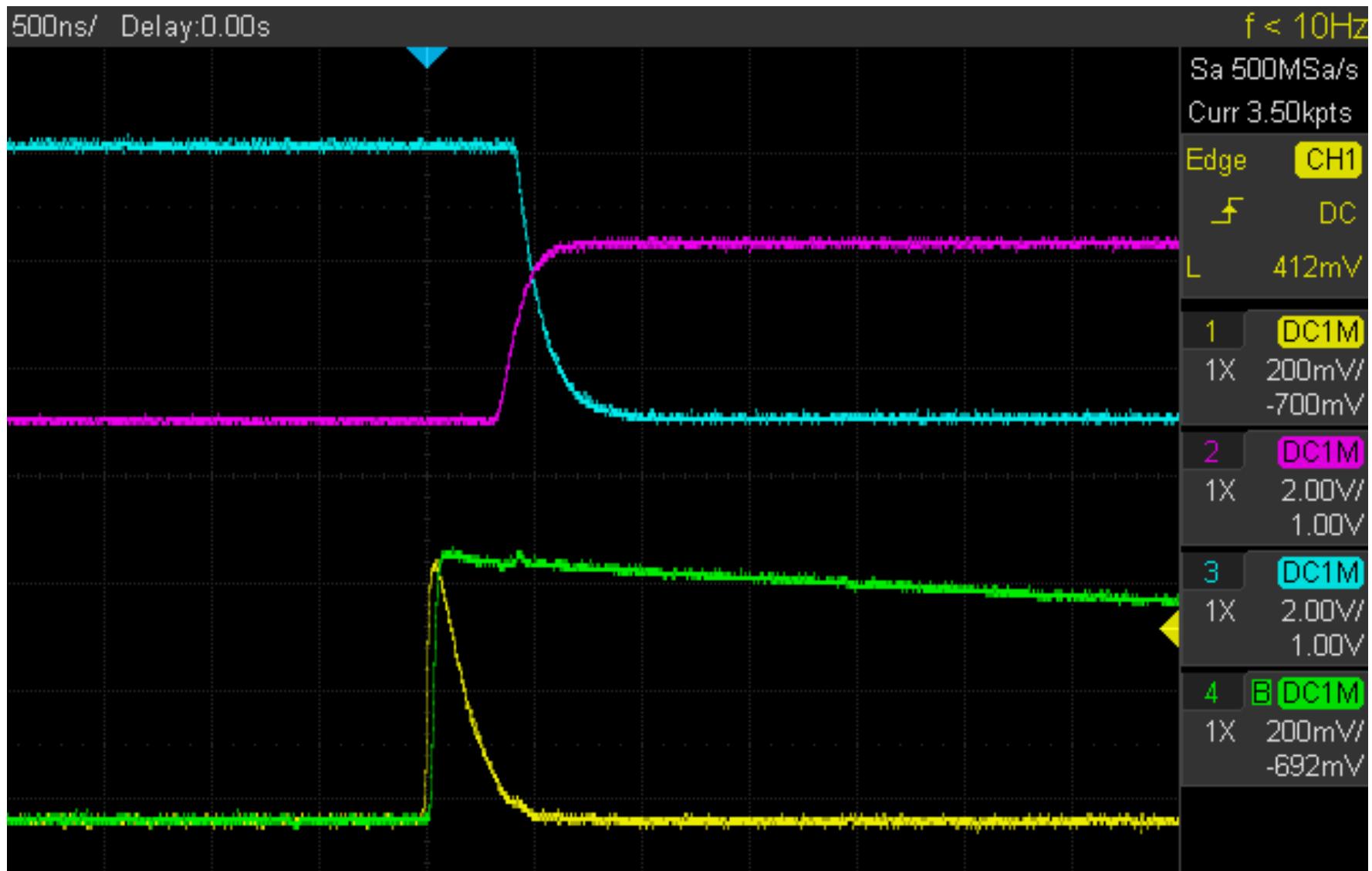The speed of charge carriers is determined by "mobility"



Mobility

The speed of charge carriers is determined by "mobility", μ

