

# PHYS127AL Lecture 14


David Stuart, UC Santa Barbara

AM Radio


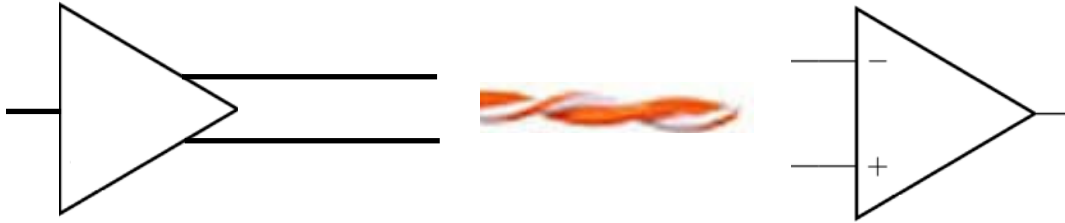
# Frequency encoding


We saw how to send signals over long cables with LVDS.



Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.
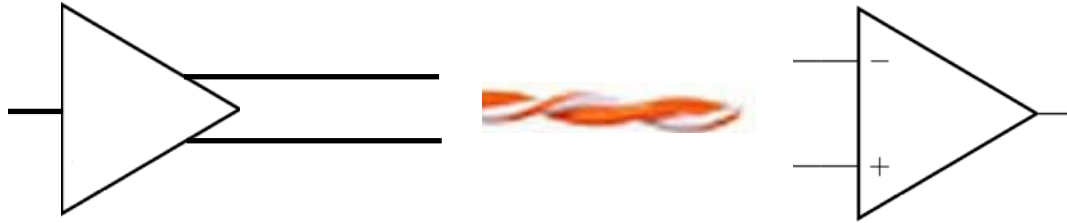
# Frequency encoding

We saw how to send signals over long cables with LVDS.




Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.

We’ll see other noise suppression techniques later.

Frequency encoding is today’s method.
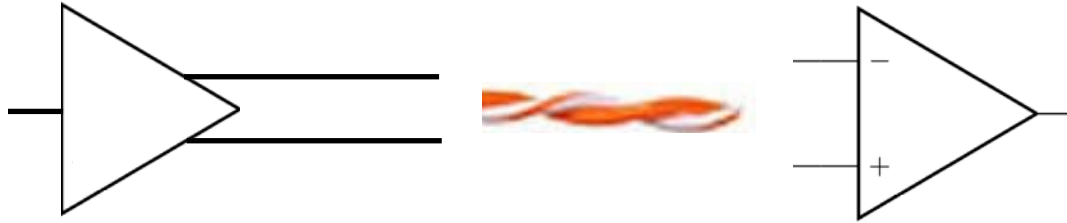
# Frequency encoding



We saw how to send signals over long cables with LVDS.



Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.


We’ll see other noise suppression techniques later.

Frequency encoding is today’s method.

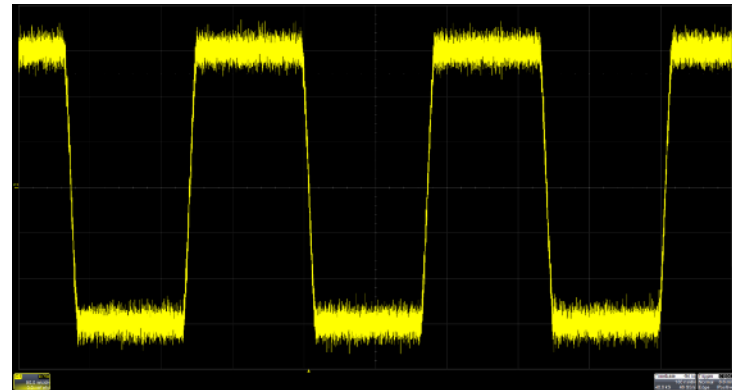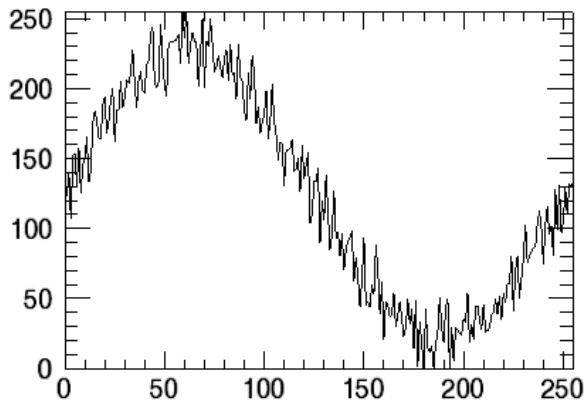
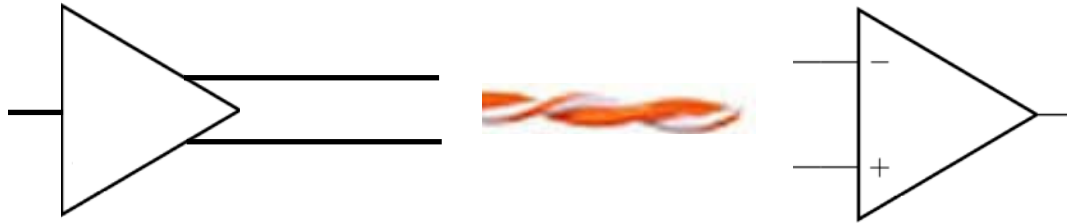
# Frequency encoding

We saw how to send signals over long cables with LVDS.



Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.

We’ll see other noise suppression techniques later.


Frequency encoding is today’s method.



This illustrates the power of encoding a voltage in a frequency with the VCO.
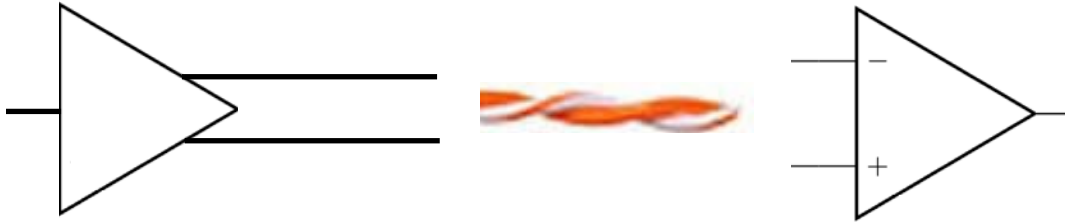
# Frequency encoding

We saw how to send signals over long cables with LVDS.




Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.

We’ll see other noise suppression techniques later.


Frequency encoding is today’s method.

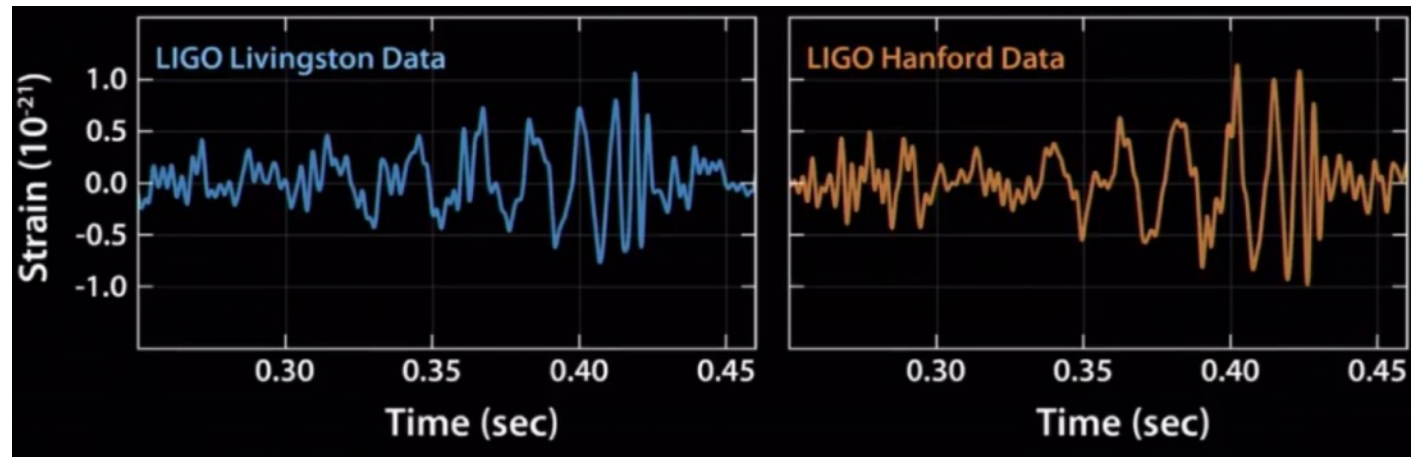Here is a more physics oriented example with recent relevance.


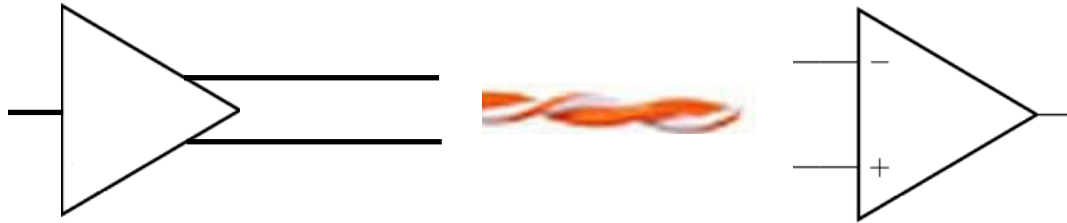
# Frequency encoding

We saw how to send signals over long cables with LVDS.




Encoding signal in a specific configuration allowed us to separate the signal information from other spurious (background or “noise”) sources because of the separate differential vs common mode encoding.

We’ll see other noise suppression techniques later.



Frequency encoding is today’s method.

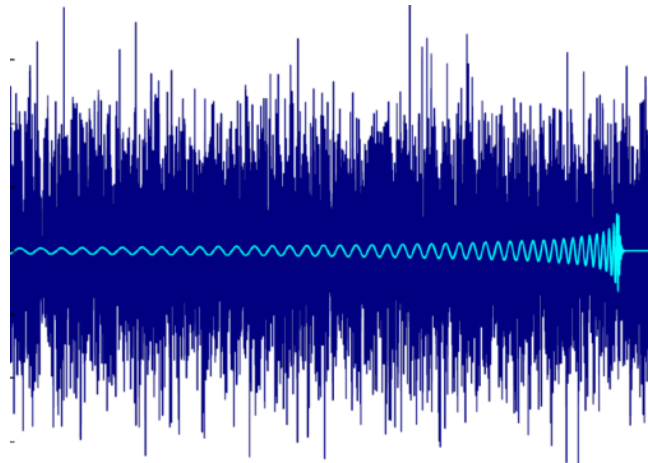Here is a more physics oriented example with recent relevance.


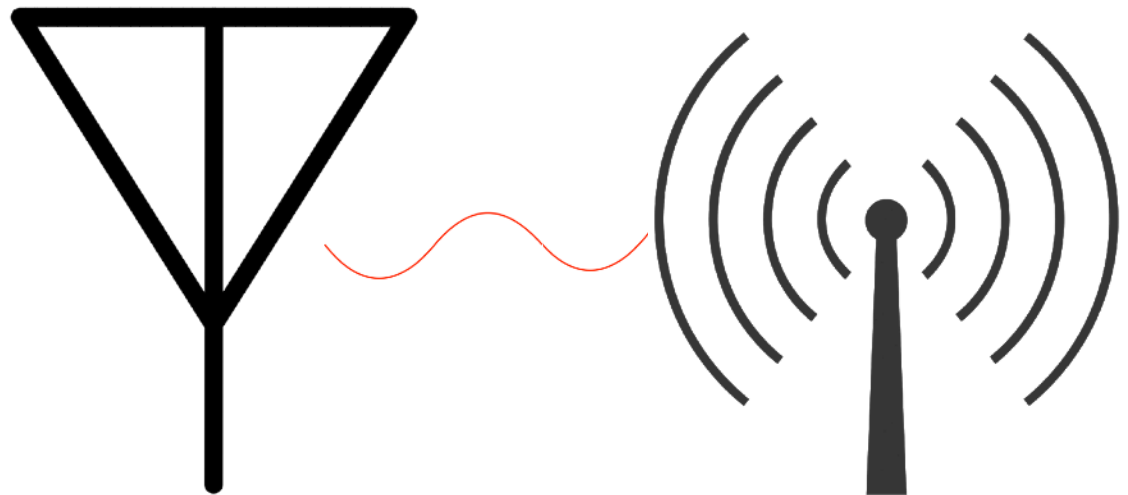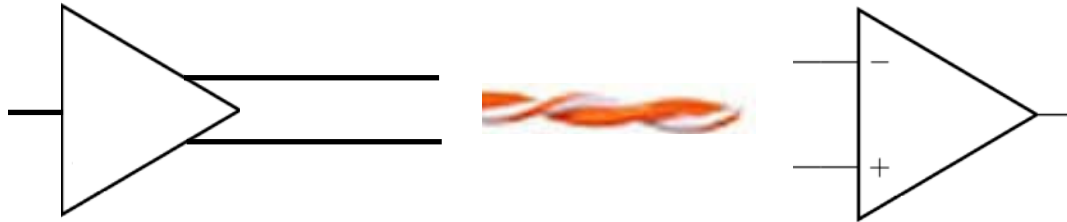
# AM (amplitude modulation) radio




AM radio encodes information within a narrow frequency band (range).  
It can operate over wires or wireless.





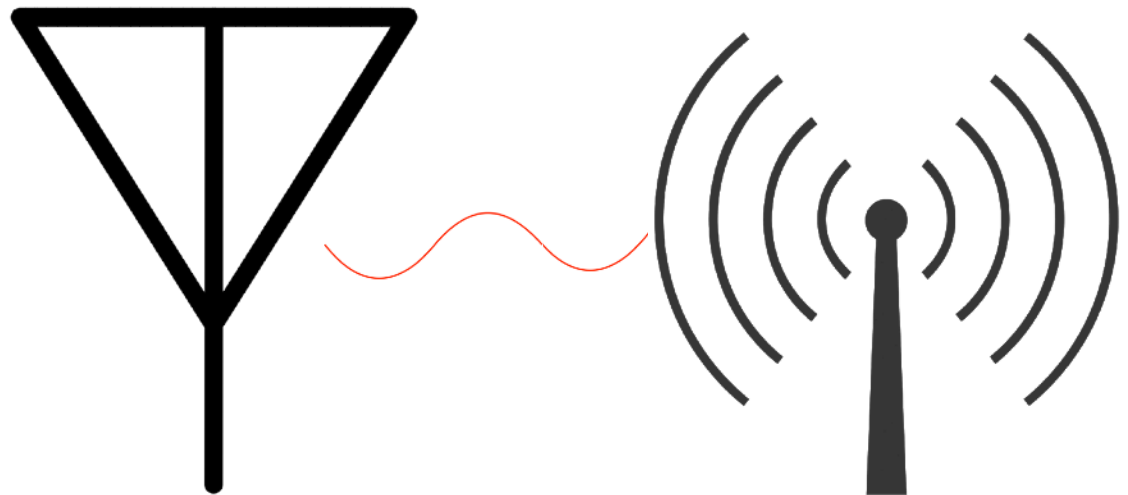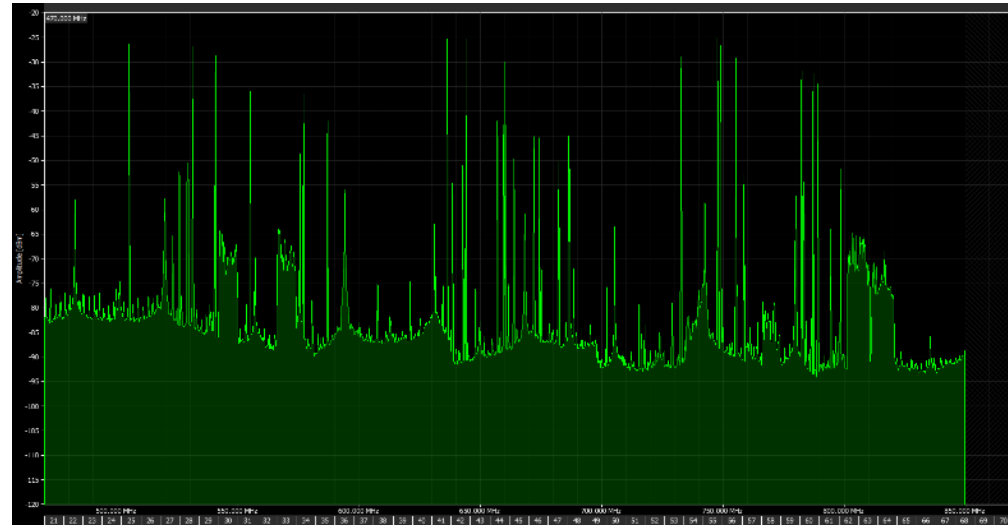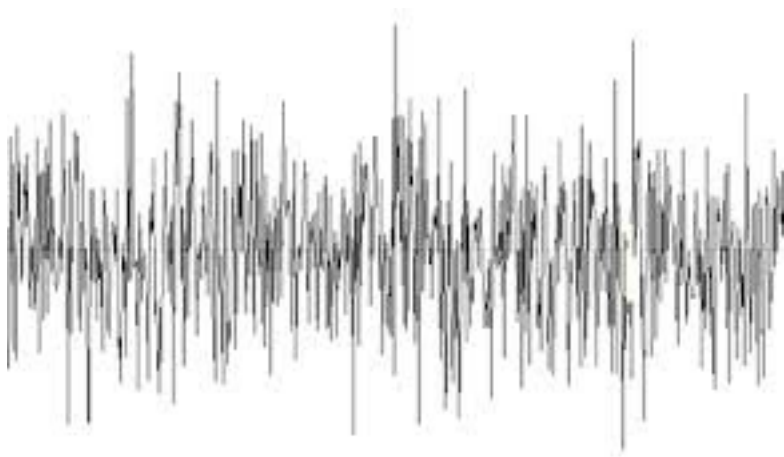
# AM (amplitude modulation) radio

AM radio encodes information within a narrow frequency band (range).  
It can operate over wires or wireless.


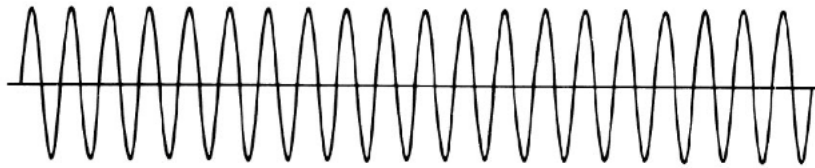
# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.



Carrier,  $\cos(2\pi f t)$

Message,  $m(t)$




Input binary sequence



ASK Modulated output wave

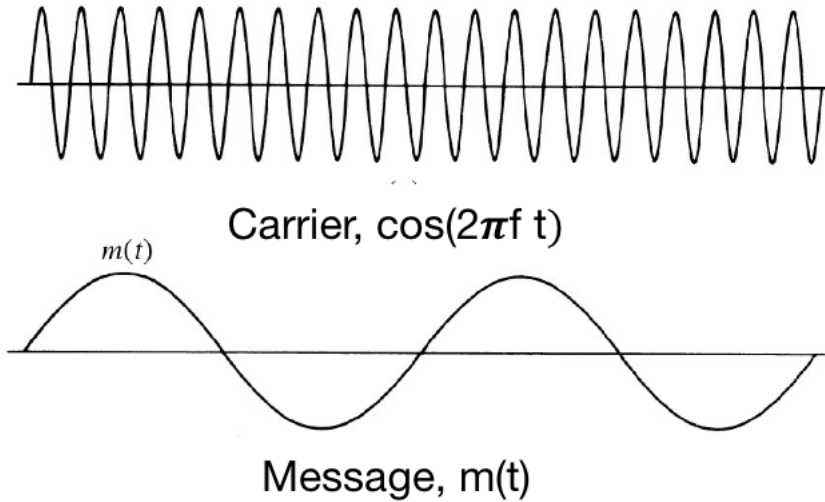
# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.



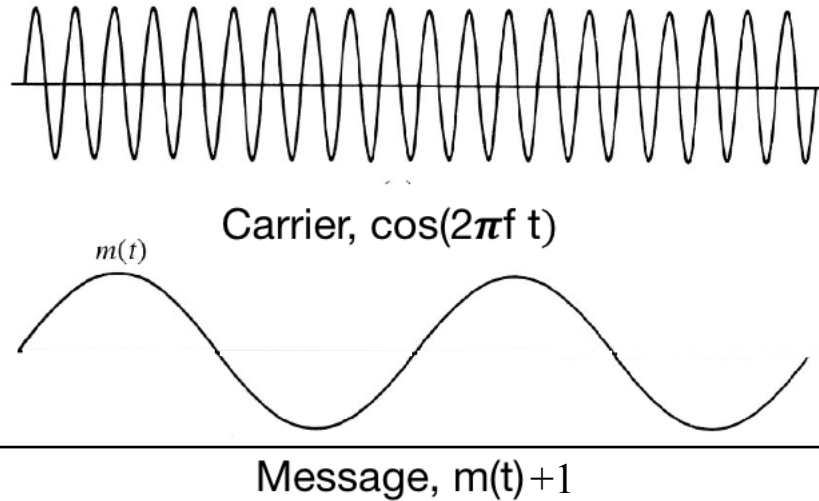
# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.


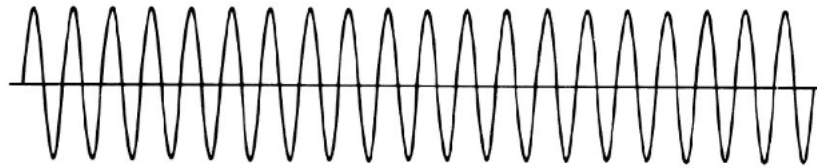
# AM (amplitude modulation) radio


Modulate—vary the amplitude of—a carrier signal.



Carrier,  $\cos(2\pi f t)$




Message,  $m(t)+1$

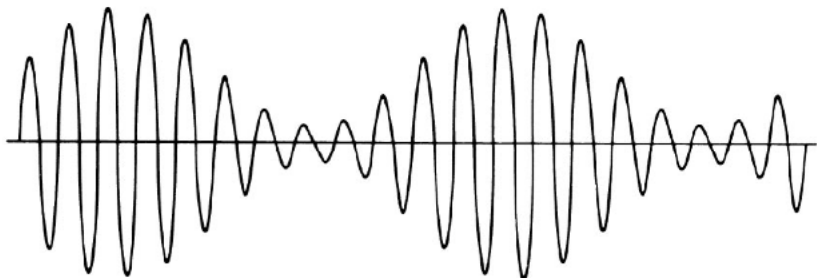

AM Signal,  $(m(t)+1)\cos(2\pi f t)$
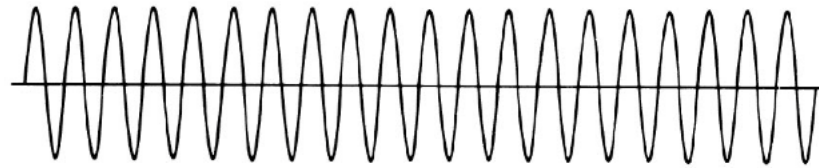
# AM (amplitude modulation) radio


Modulate—vary the amplitude of—a carrier signal.





Carrier,  $\cos(2\pi f t)$



Message,  $m(t)+1$

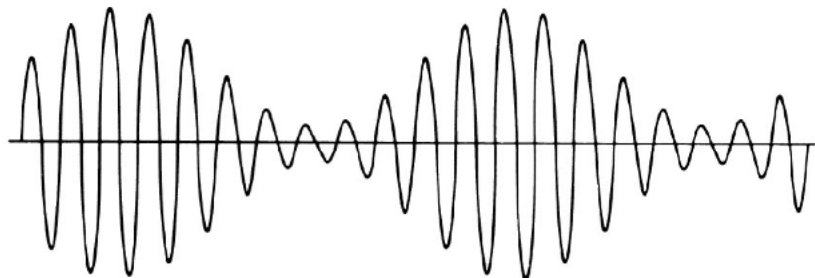


AM Signal,  $(m(t)+1)\cos(2\pi f t)$

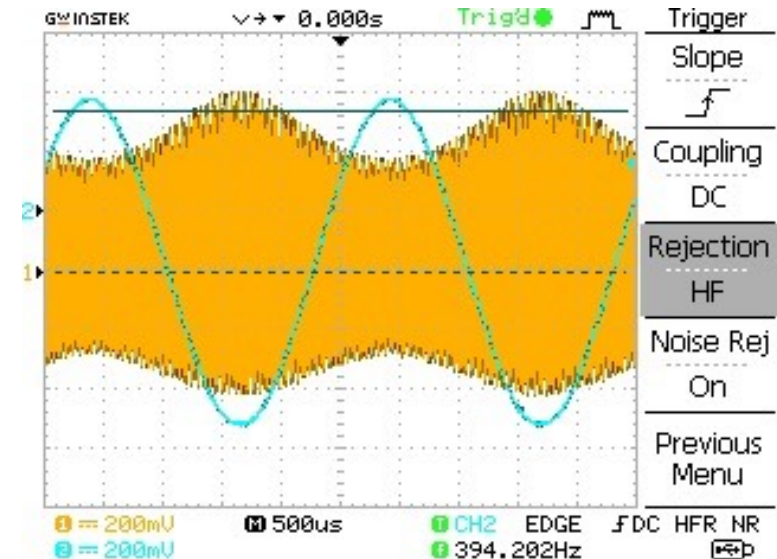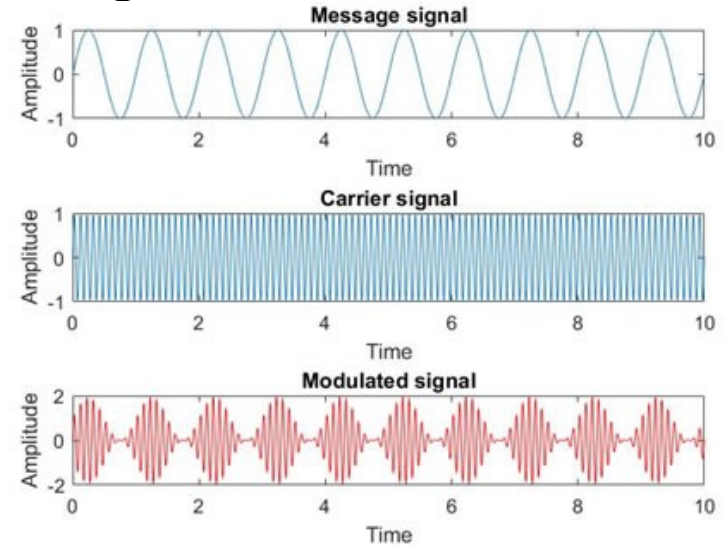

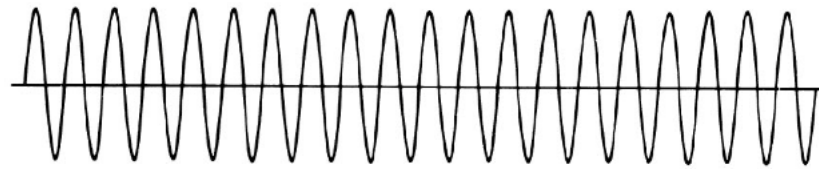
# AM (amplitude modulation) radio


Modulate—vary the amplitude of—a carrier signal.



Carrier,  $\cos(2\pi f t)$


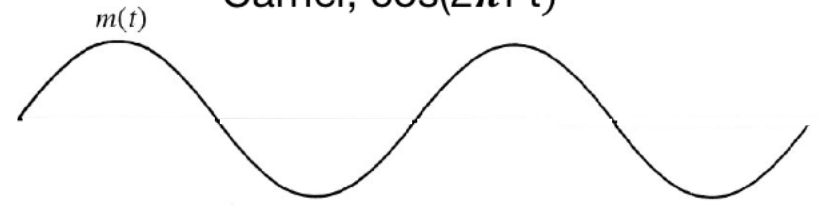


Message,  $m(t)+1$

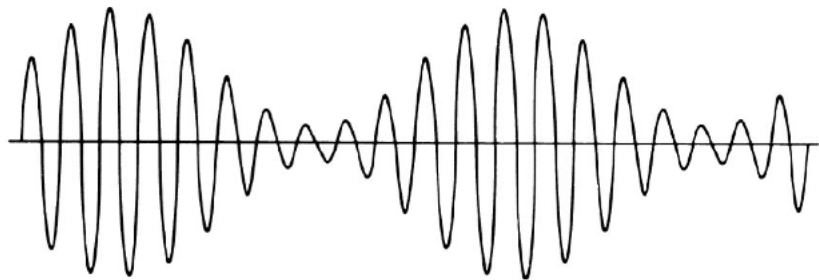


AM Signal,  $(m(t)+1)\cos(2\pi f t)$

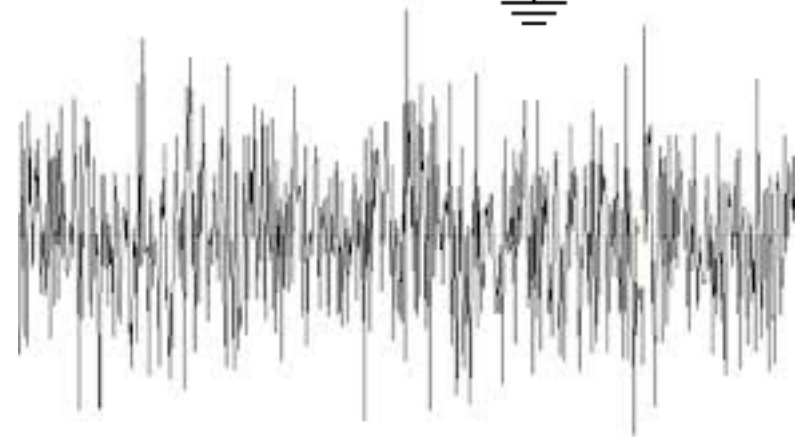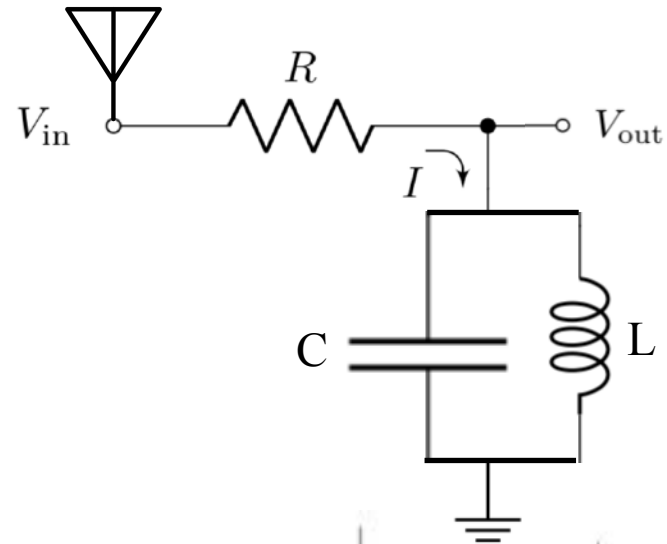We can select only the “station” of interest with a band-pass filter.



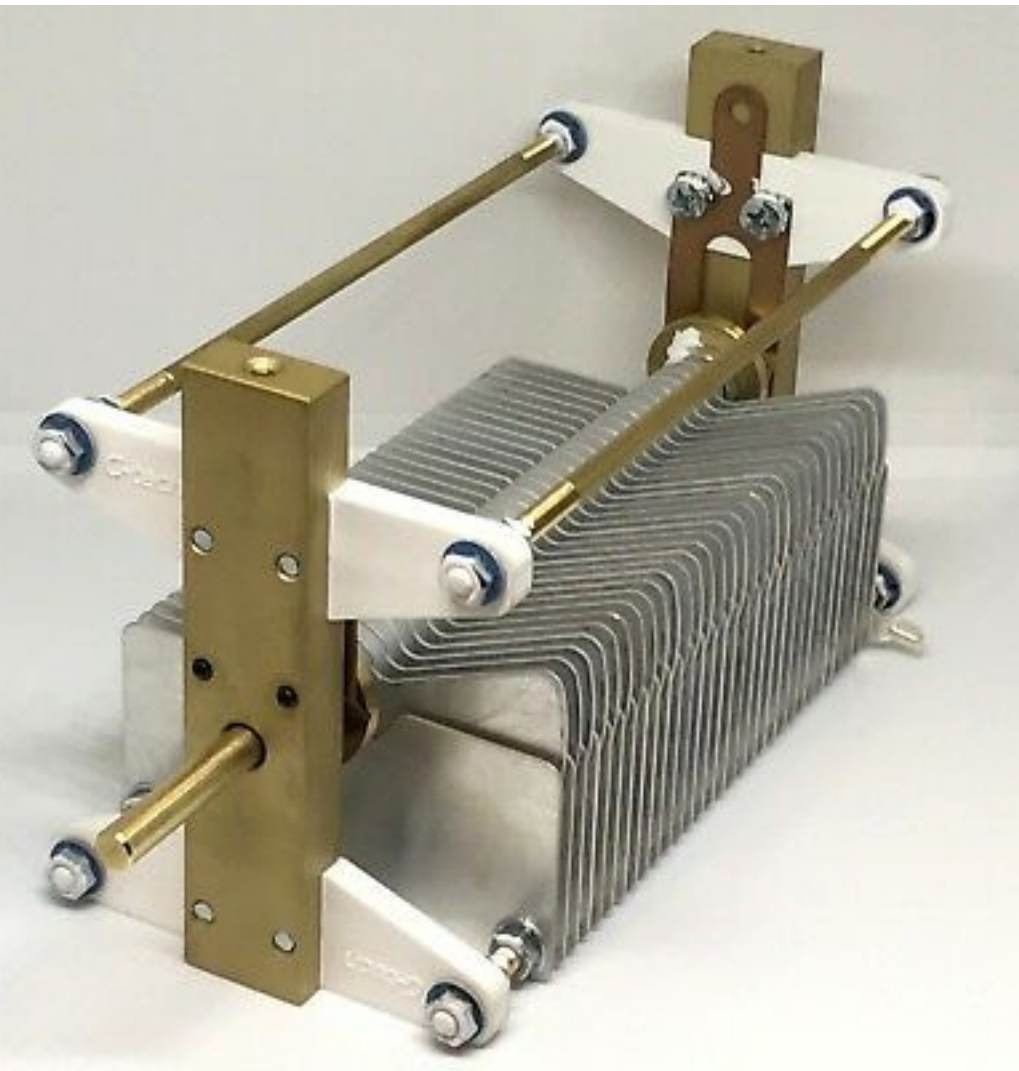
# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.



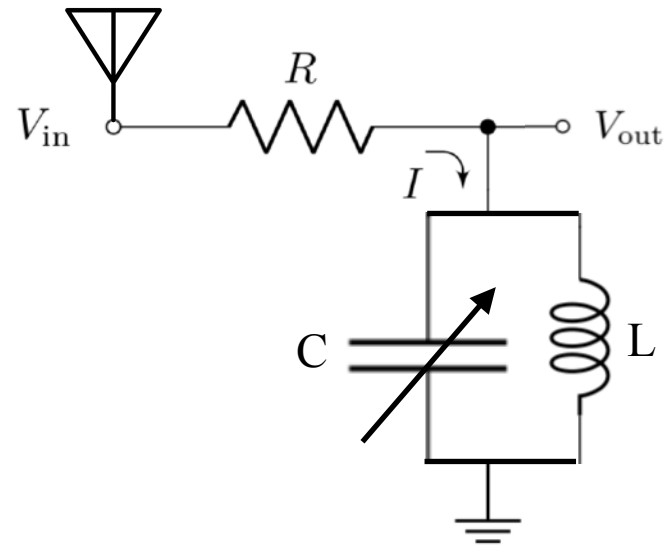We can select only the “station” of interest with a band-pass filter.



$$\omega_0 = 1/\sqrt{LC}$$




# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.

We can select only the “station” of interest with a band-pass filter.

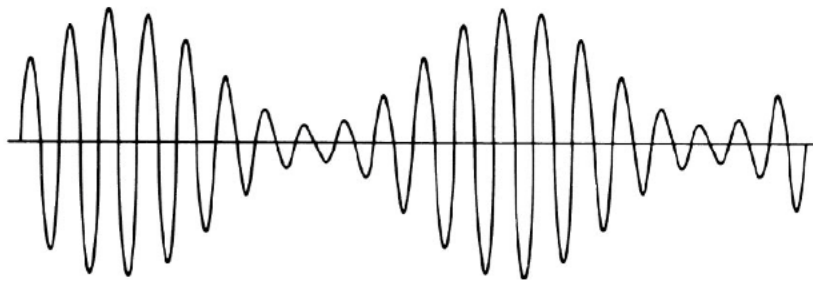The low frequency message can still get through the band-pass.



AM Signal,  $(m(t)+1)\cos(2\pi f t)$

# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.

We can select only the “station” of interest with a band-pass filter.


The low frequency message can still get through the band-pass.

$$\begin{aligned}r(t) &= [A_s \cos(\omega_s t) + 1] \cos(\omega_c t) \\ &= \cos(\omega_c t) + A_s \cos(\omega_c t) \cos(\omega_s t)\end{aligned}$$

Use trig identity:  $\cos(A) \cos(B) = \frac{1}{2}[\cos(A+B) + \cos(A-B)]$

$$r(t) = \cos(\omega_c t) + \frac{1}{2}A_s \cos[(\omega_c + \omega_s)t] + \frac{1}{2}A_s \cos[(\omega_c - \omega_s)t]$$

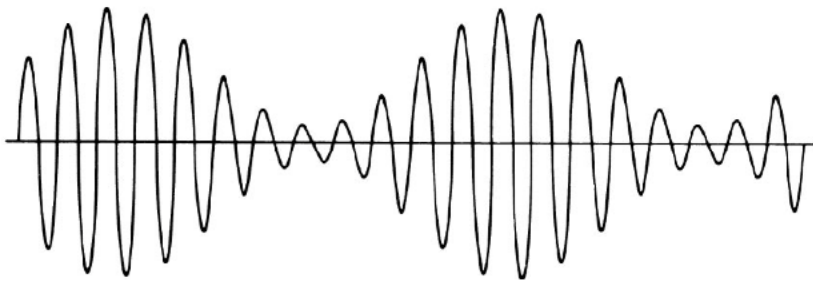Signal is just above and below the carrier frequency.



AM Signal,  $(m(t)+1)\cos(2\pi f t)$

# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.

We can select only the “station” of interest with a band-pass filter.


The low frequency message can still get through the band-pass.

$$\begin{aligned}r(t) &= [A_s \cos(\omega_s t) + 1] \cos(\omega_c t) \\ &= \cos(\omega_c t) + A_s \cos(\omega_c t) \cos(\omega_s t)\end{aligned}$$


Use trig identity:  $\cos(A) \cos(B) = \frac{1}{2}[\cos(A+B) + \cos(A-B)]$

$$r(t) = \cos(\omega_c t) + \frac{1}{2}A_s \cos[(\omega_c + \omega_s)t] + \frac{1}{2}A_s \cos[(\omega_c - \omega_s)t]$$

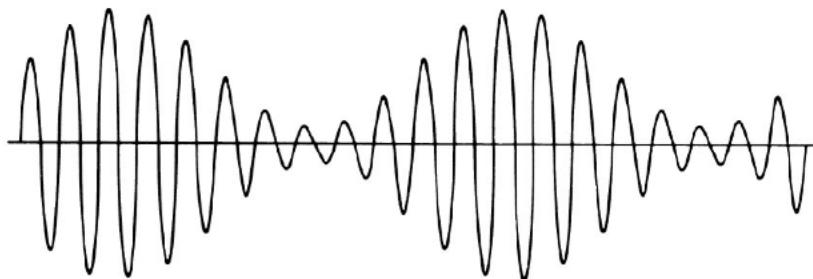Signal is just above and below the carrier frequency.



AM Signal,  $(m(t)+1)\cos(2\pi f t)$

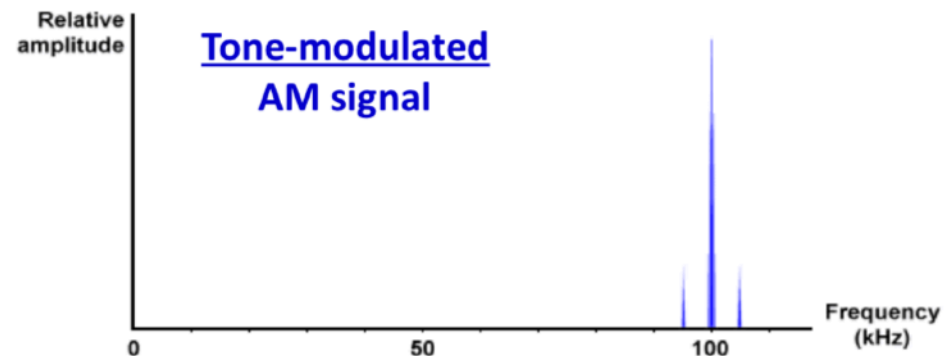

# AM (amplitude modulation) radio

Modulate—vary the amplitude of—a carrier signal.

We can select only the “station” of interest with a band-pass filter.


The low frequency message can still get through the band-pass.

$$\begin{aligned}r(t) &= [A_s \cos(\omega_s t) + 1] \cos(\omega_c t) \\ &= \cos(\omega_c t) + A_s \cos(\omega_c t) \cos(\omega_s t)\end{aligned}$$


Use trig identity:  $\cos(A) \cos(B) = \frac{1}{2}[\cos(A+B) + \cos(A-B)]$

$$r(t) = \cos(\omega_c t) + \frac{1}{2}A_s \cos[(\omega_c + \omega_s)t] + \frac{1}{2}A_s \cos[(\omega_c - \omega_s)t]$$

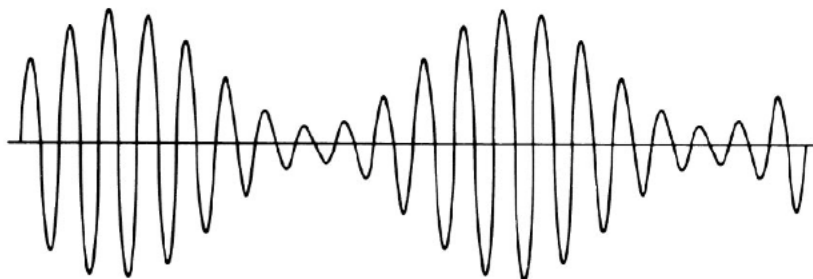Signal is just above and below the carrier frequency.




AM Signal,  $(m(t)+1)\cos(2\pi f t)$

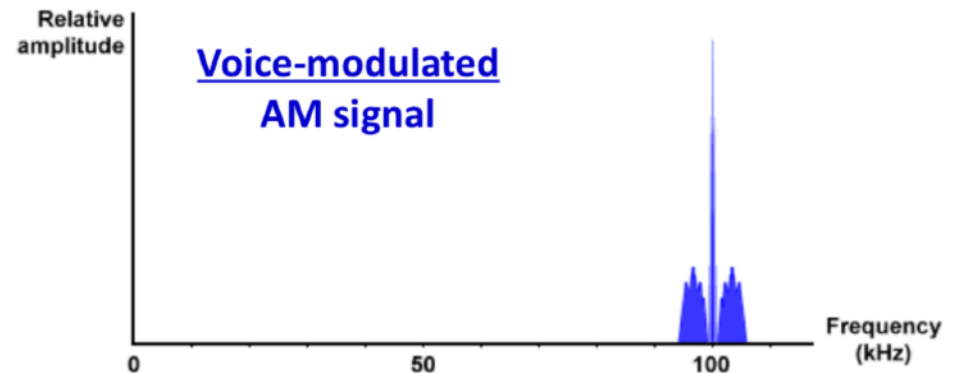

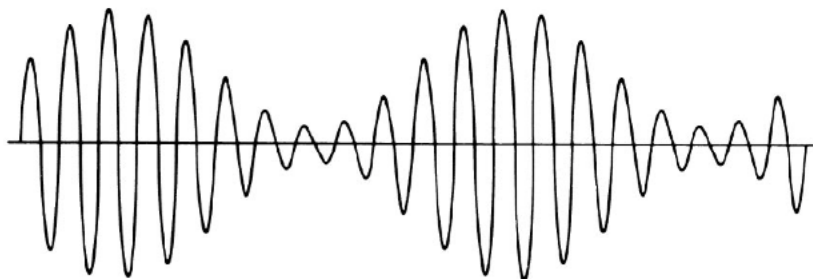
# AM (amplitude modulation) radio

Signal is just above and below the carrier frequency, in the “side bands”.

FCC regulates AM radio stations to be max signal frequency of 5 kHz and spaces them by 10 kHz.  $f_c$  ranges from 540 kHz - 1600 kHz.



AM Signal,  $(m(t)+1)\cos(2\pi f t)$

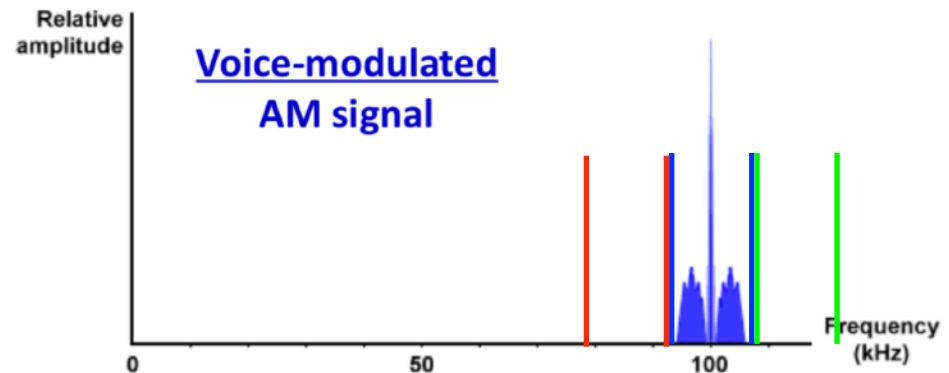

# AM (amplitude modulation) radio


Signal is just above and below the carrier frequency, in the “side bands”.

FCC regulates AM radio stations to be max signal frequency of 5 kHz and spaces them by 10 kHz.  $f_c$  ranges from 540 kHz - 1600 kHz.


FM ranges from 88 - 108 MHz with 200 kHz wide bands

WiFi operates in channels at  $\sim$  5 GHz or 2.4 GHz. (802.11a - 802.11n) with channel widths about 20 MHz and 5 MHz wide. (AKA *bandwidth*).

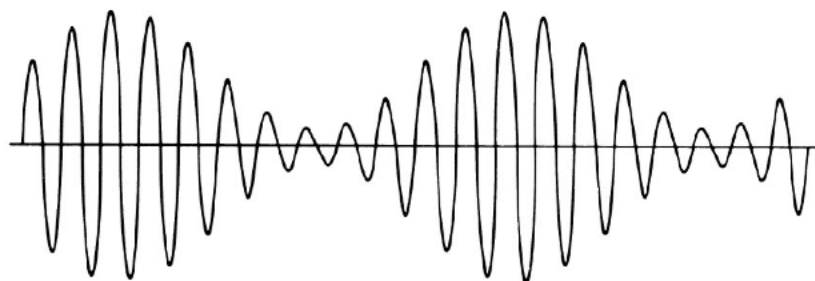4G is around 2 GHz; 5G has many bands from 24 GHz to 47 GHz.





AM Signal,  $(m(t)+1)\cos(2\pi f t)$

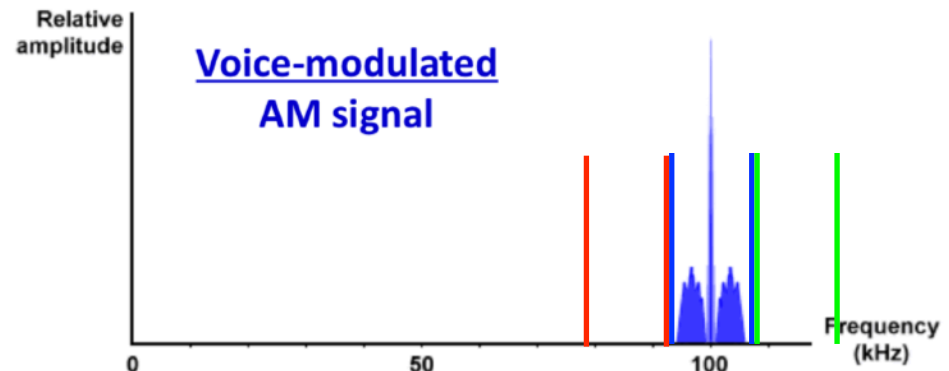

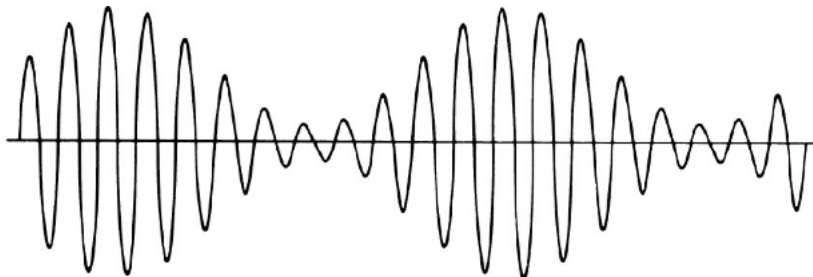
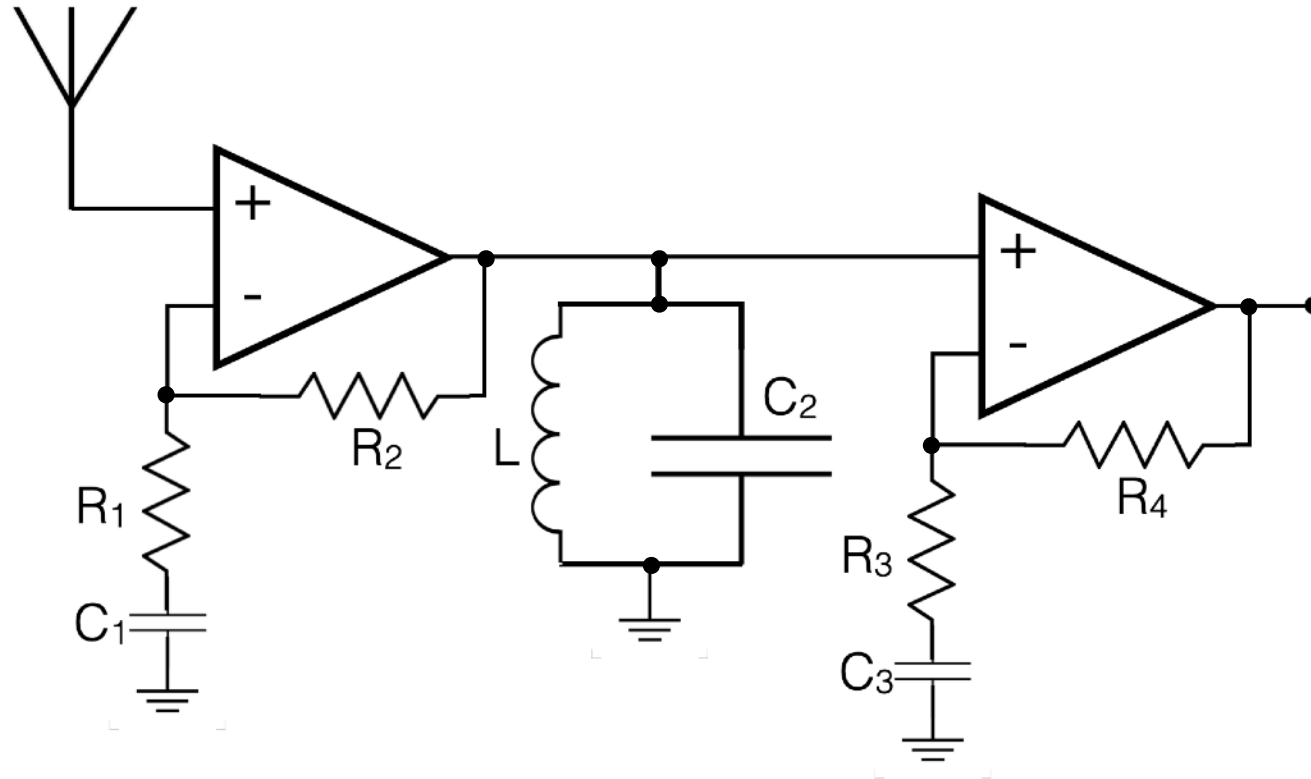
# AM radio circuit

Amplify; not for volume but for impedance.


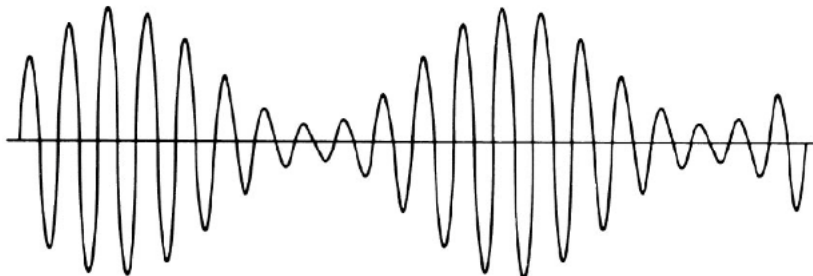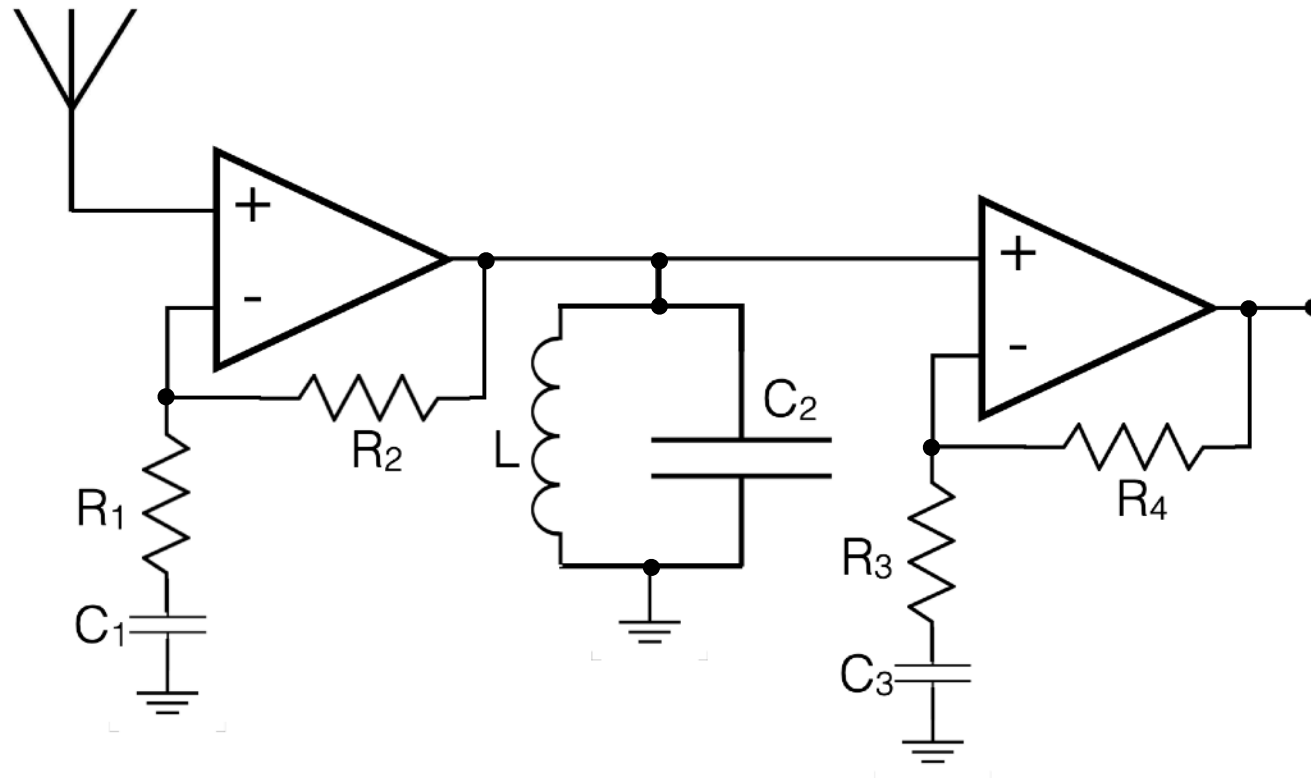
# AM radio circuit

Amplify; not for volume but for impedance.





Then we need to extract the low frequency signal from the high frequency carrier and side bands.


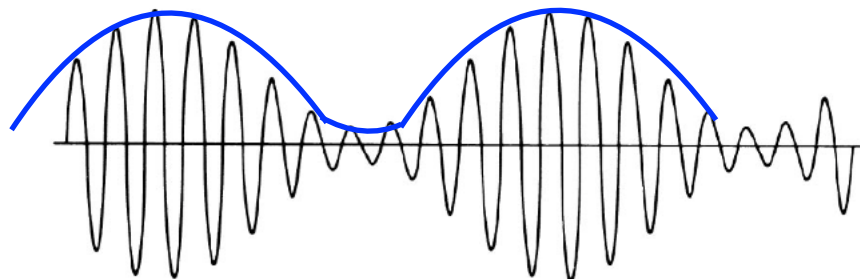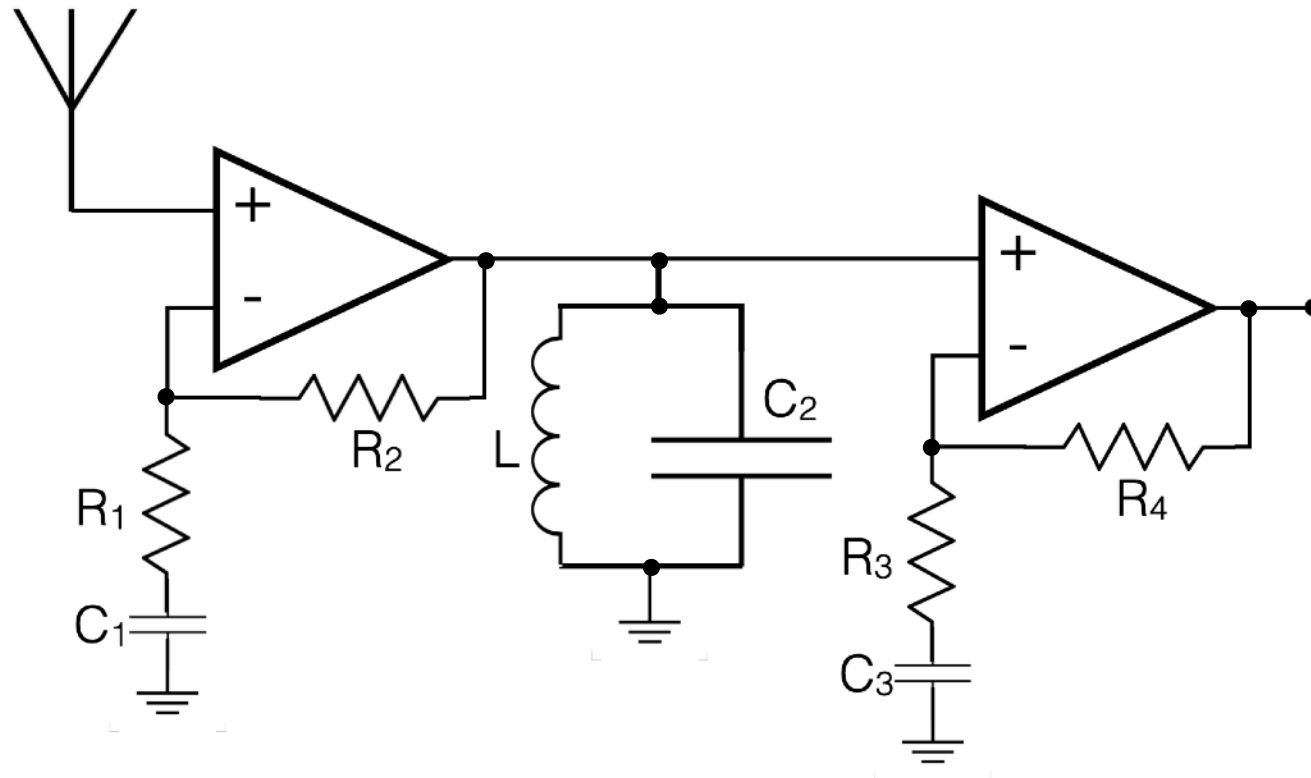
# AM radio circuit


Amplify; not for volume but for impedance.



Then we need to extract the low frequency signal from the high frequency carrier and side bands. That is in the **envelope**.
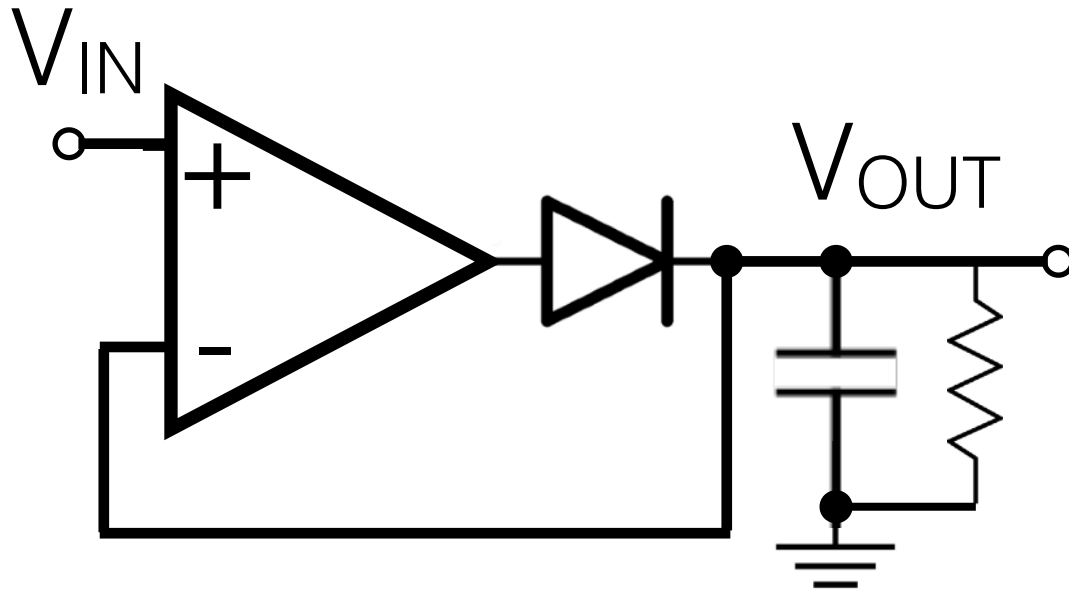
# AM radio circuit: extracting the envelope



Extract the envelope with a “leaky peak detector”



Choose RC to match the frequency of the signal, not the carrier.


$$f_s = 10 \text{ kHz}$$
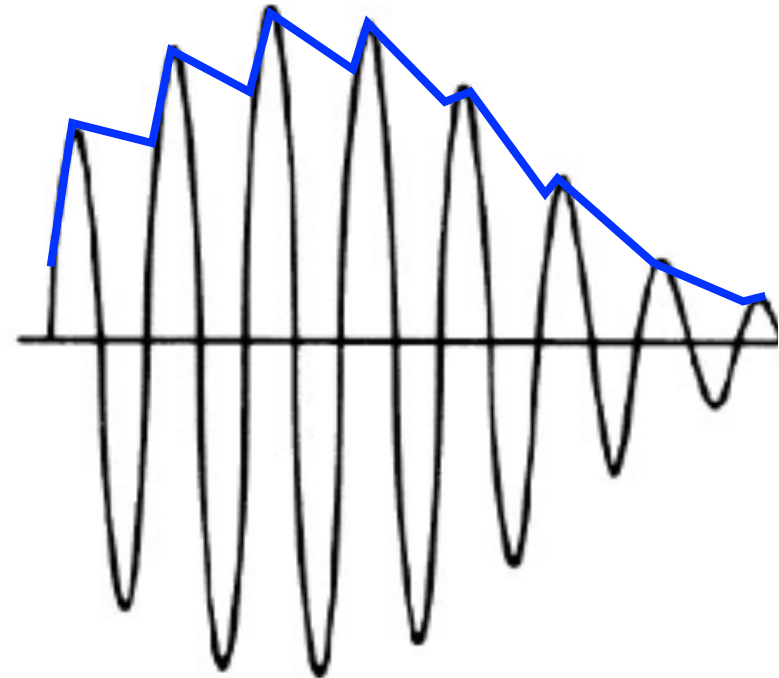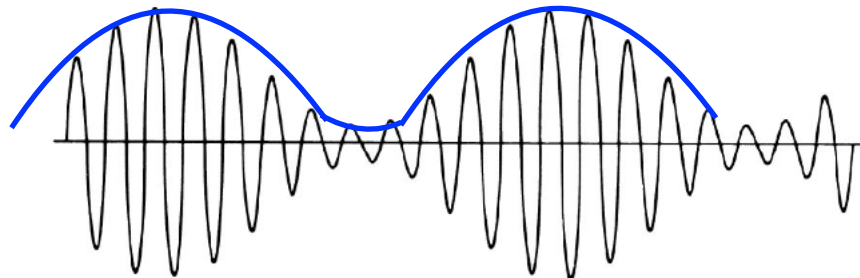
$$RC = (1\text{k}\Omega)(100\text{nF}) = 100\mu\text{s}.$$





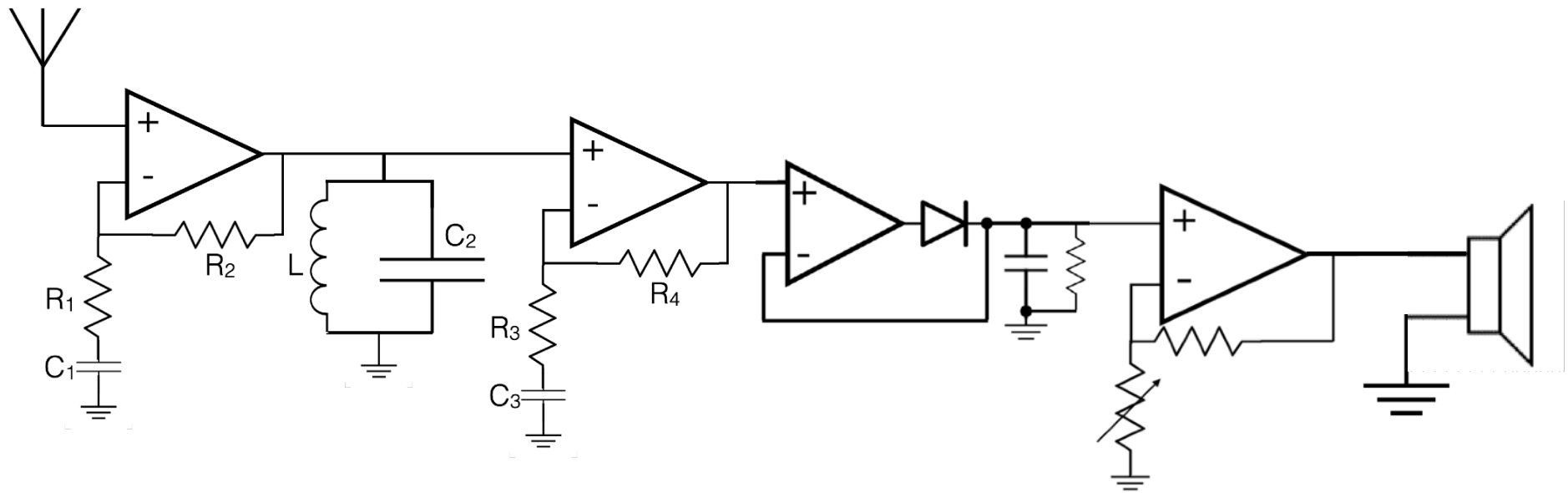
# AM radio circuit: extracting the envelope

Now we have a signal, e.g., music, that we can amplify and drive a speaker.



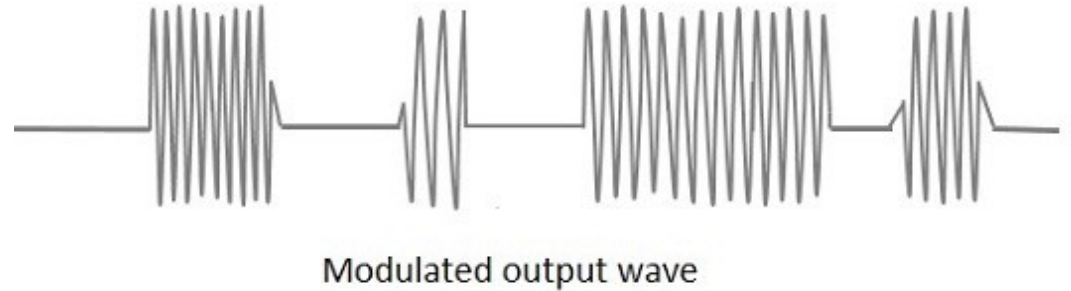
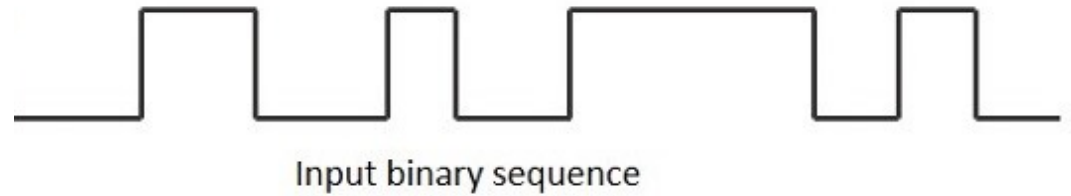
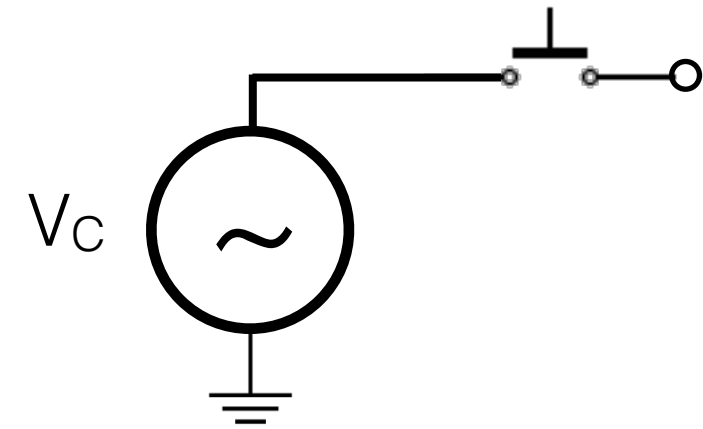
# AM radio modulating circuit

To modulate the signal onto the carrier, you could use a simple switch, like morse code.



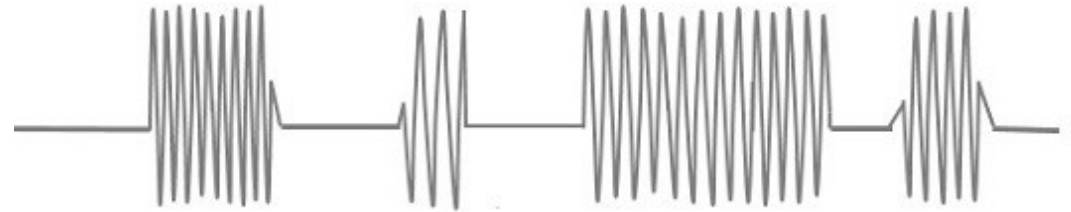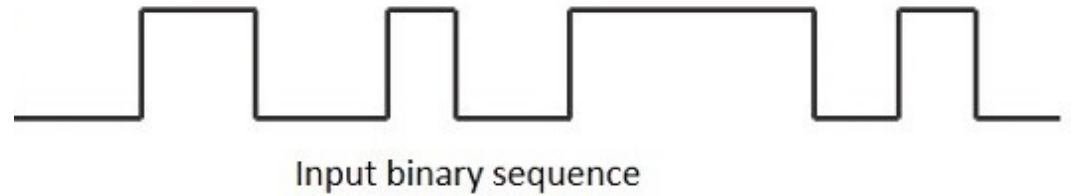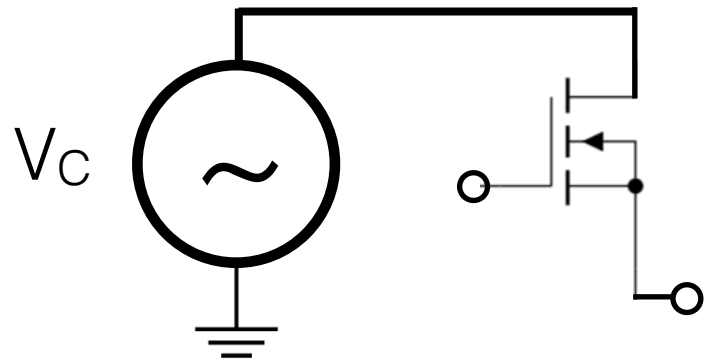
# AM radio modulating circuit

To modulate the signal onto the carrier, you could use a MOSFET switch.



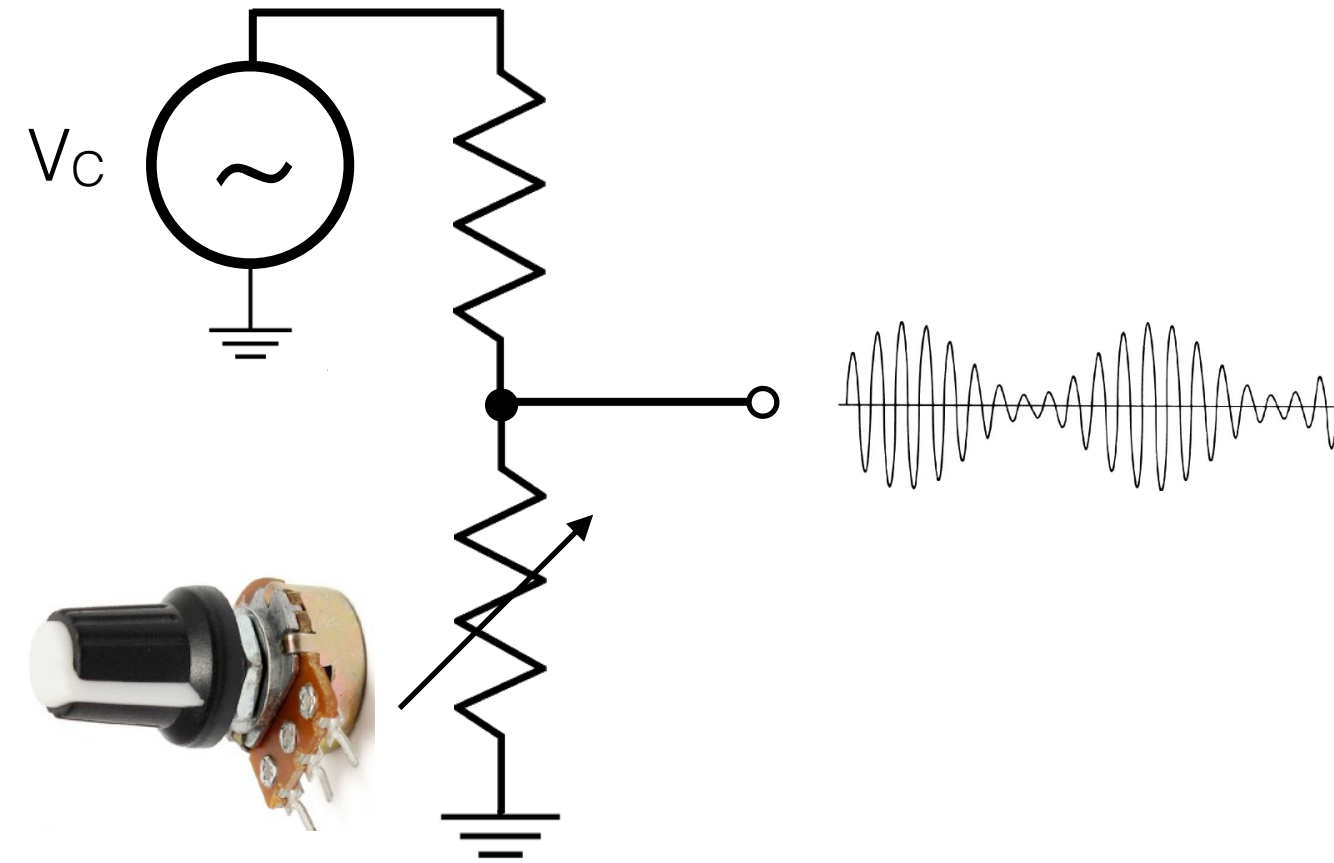
# AM radio modulating circuit

To modulate the signal onto the carrier, you could use a variable resistance voltage divider.




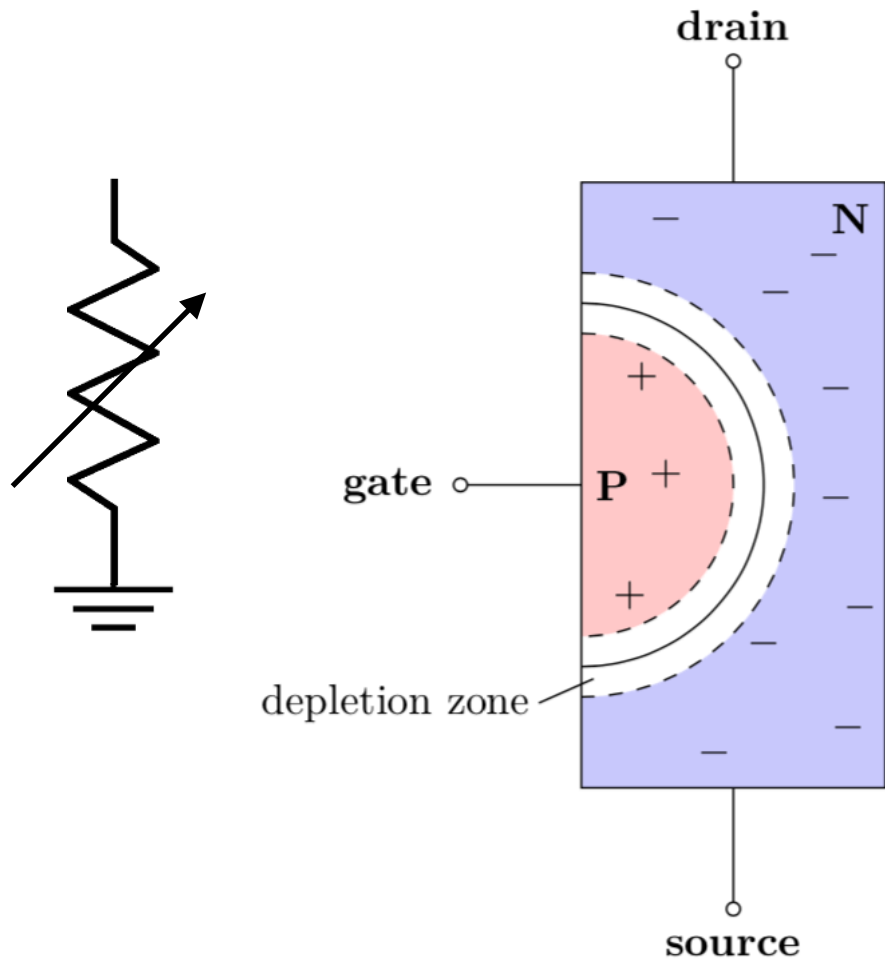
# AM radio modulating circuit

To modulate the signal onto the carrier, you could use a variable resistance voltage divider. We want a voltage-controlled variable resistance.



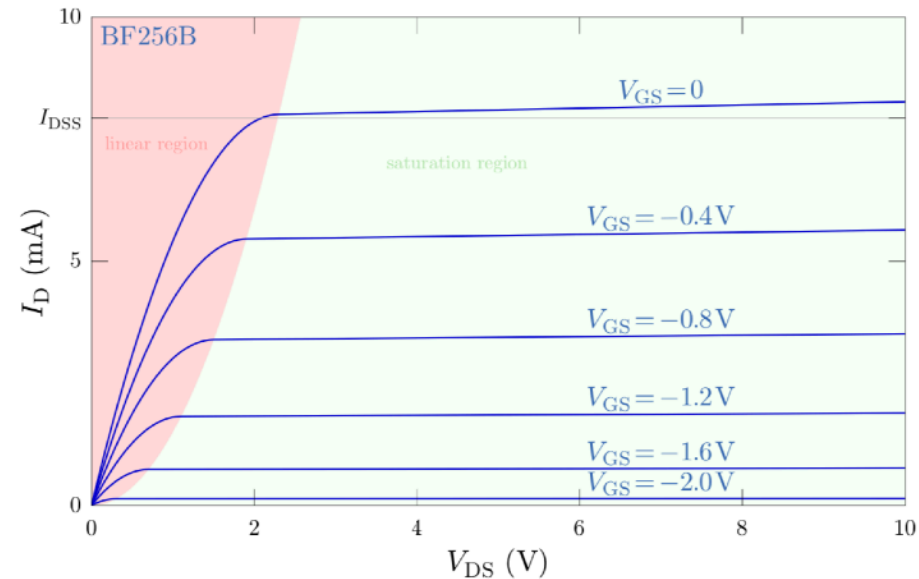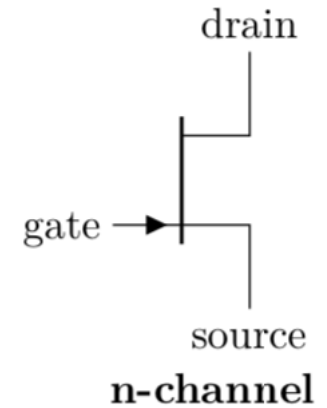
$$R = \frac{1}{2k(V_{GS} - V_{\Theta})}$$


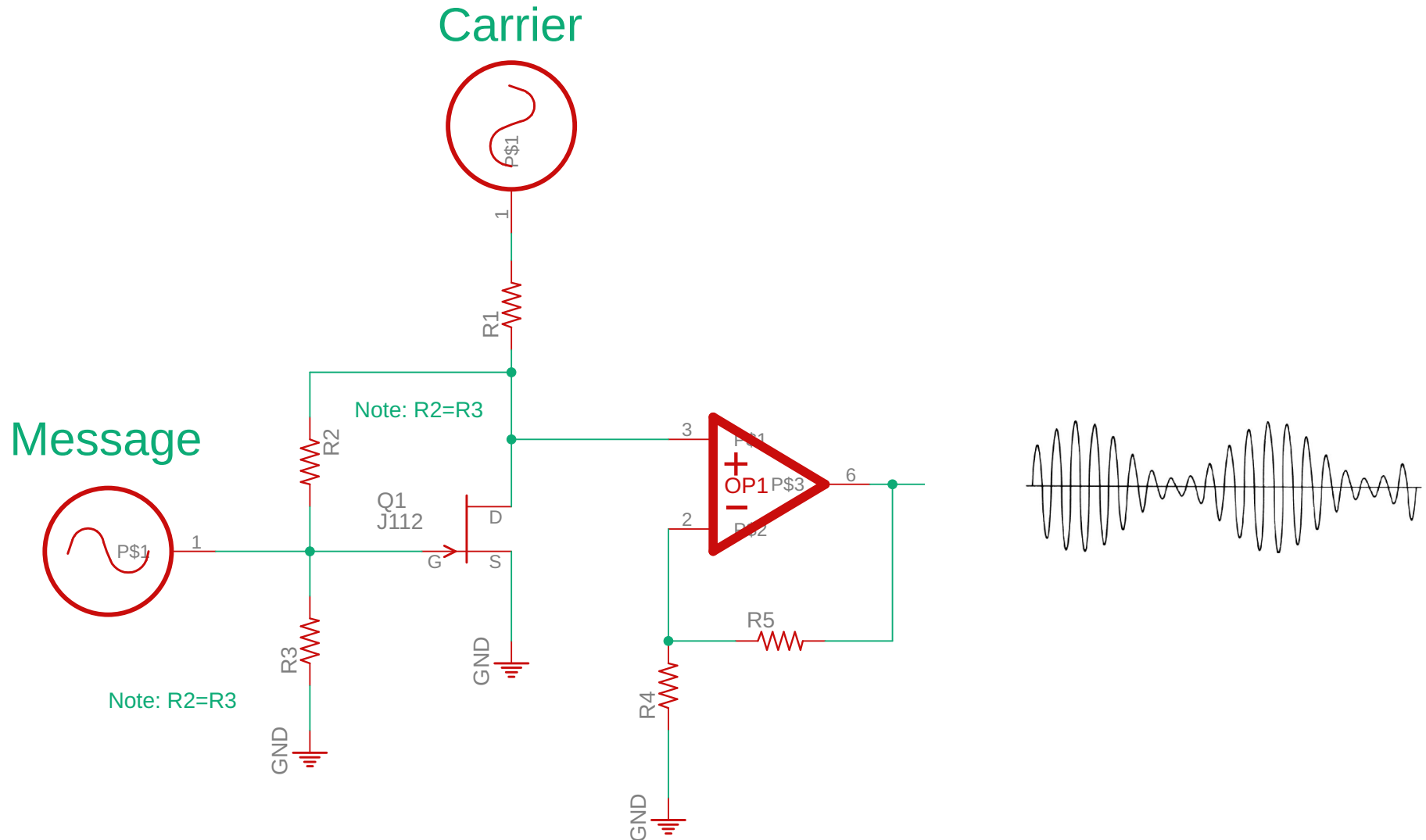
# AM radio modulating circuit


To modulate the signal onto the carrier, you could use a variable resistance voltage divider. We want a voltage-controlled variable resistance.





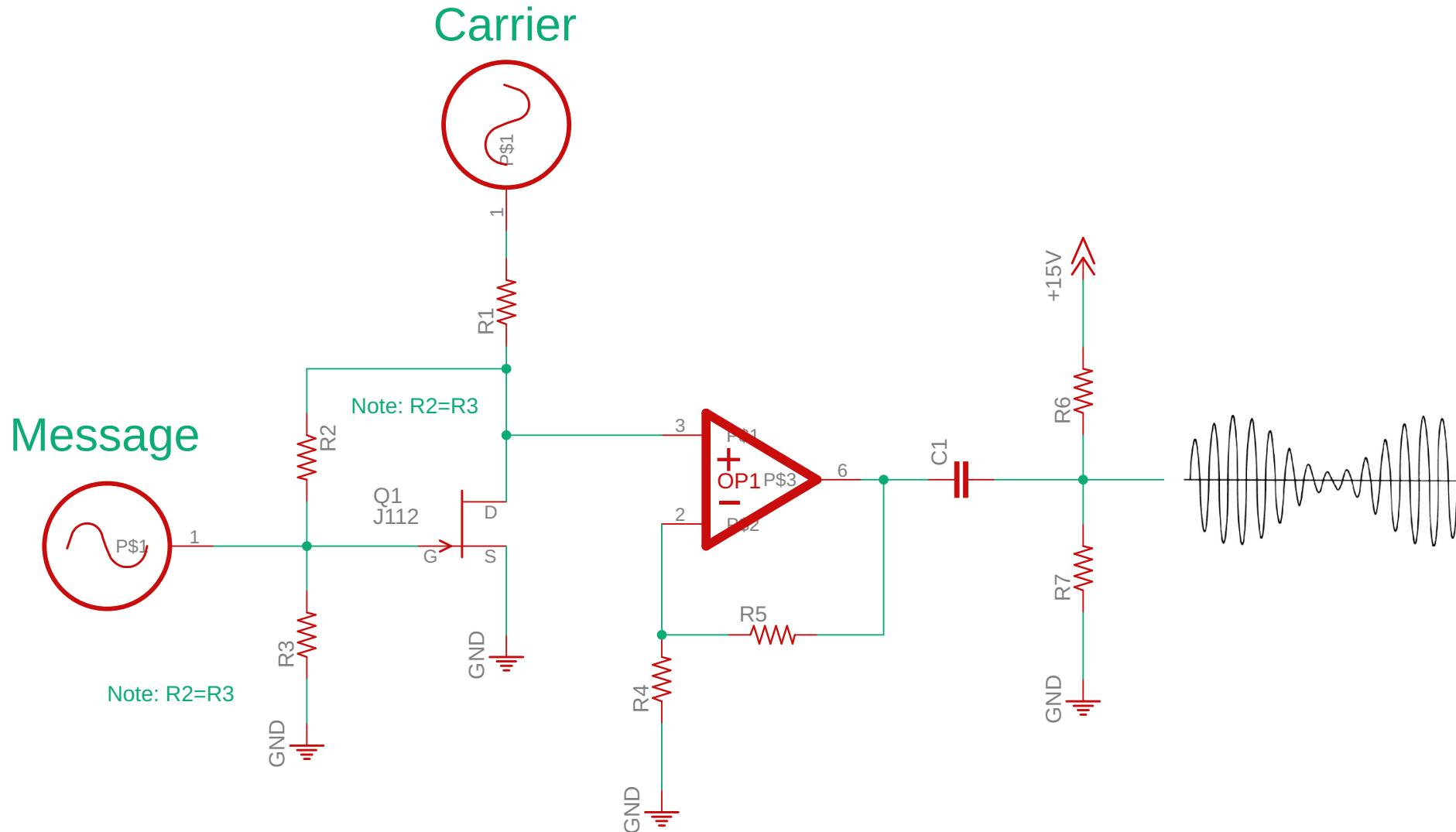
# AM radio modulating circuit

To modulate the signal onto the carrier, you could use a variable resistance voltage divider. We want a voltage-controlled variable resistance.


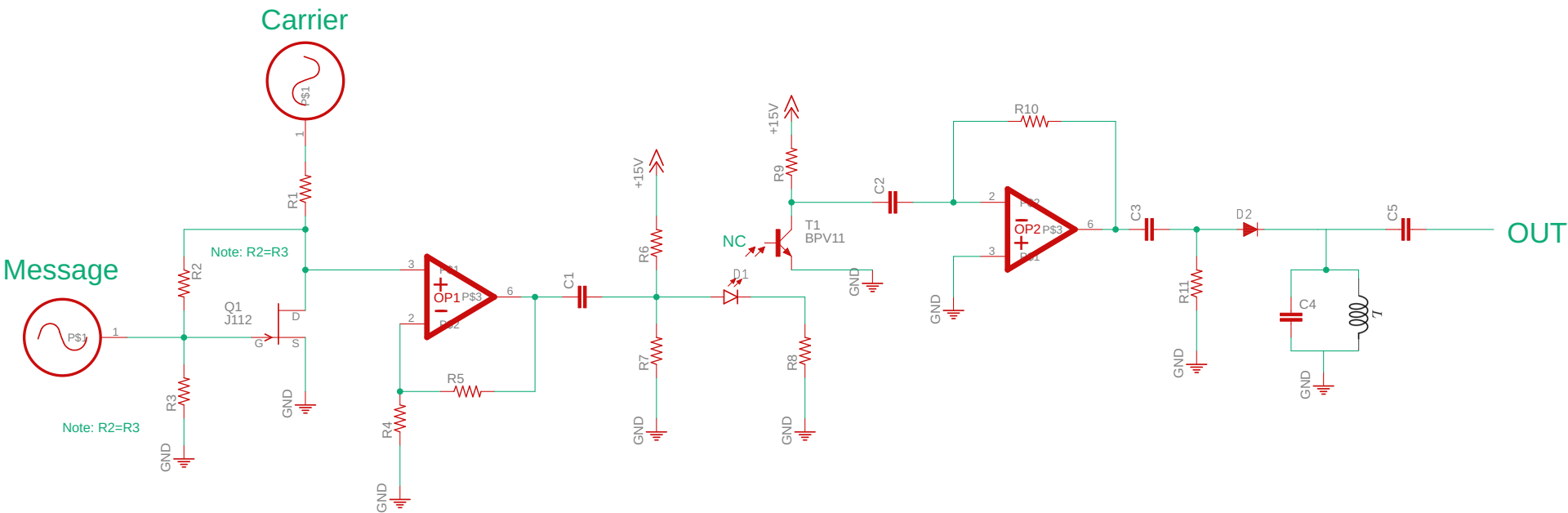
# AM radio with LED TX/RX

In lab next week, you will build an AM transmitter and receiver, but use an LED & phototransistor to send and receive.




Rather than carefully tuning the LC resonator to your carrier, you can tune the carrier to the receiving channel.

You need two oscillators for this.
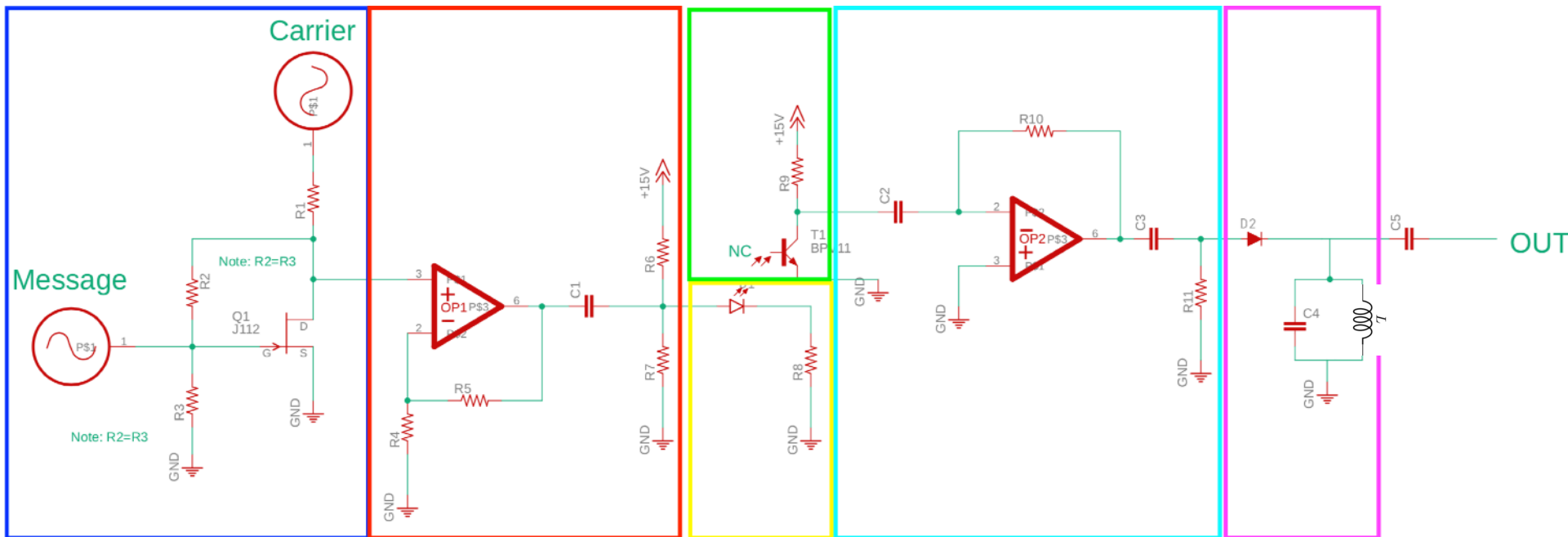
# AM radio with LED TX/RX

In lab next week, you will build an AM transmitter and receiver, but use an LED & phototransistor to send and receive.



It is important to factorize the stages to ease debugging.

Verify signal shape at each stage, e.g., measure LED output as current through R8.

# This circuit is getting complex; how to simplify?

Careful layout and stage-by-stage debugging is key.

Separate stages with easy probe points to recheck their behavior.

Documentation is important to recheck previous behavior.

Allow each stage to be self tested.


Make a simple test circuit with just a morse-code modulator.

Feed the LED a separately controlled signal.

Measure LED output as current through R8.

Feed the integrator a separately controlled signal.

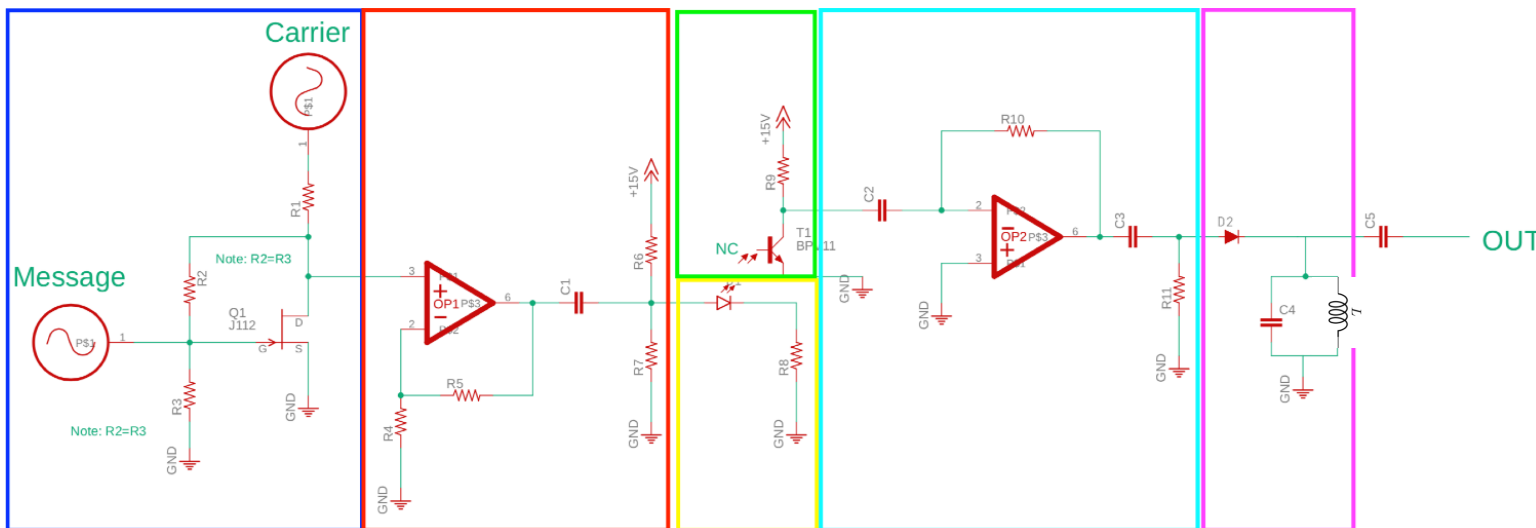ASICs often have a Built-In Self Test mode (BIST)




# AM radio without power



Asymmetric conduction between a crystal and thin wire acted like a diode.


## Crystal Radio Receiver from 1922

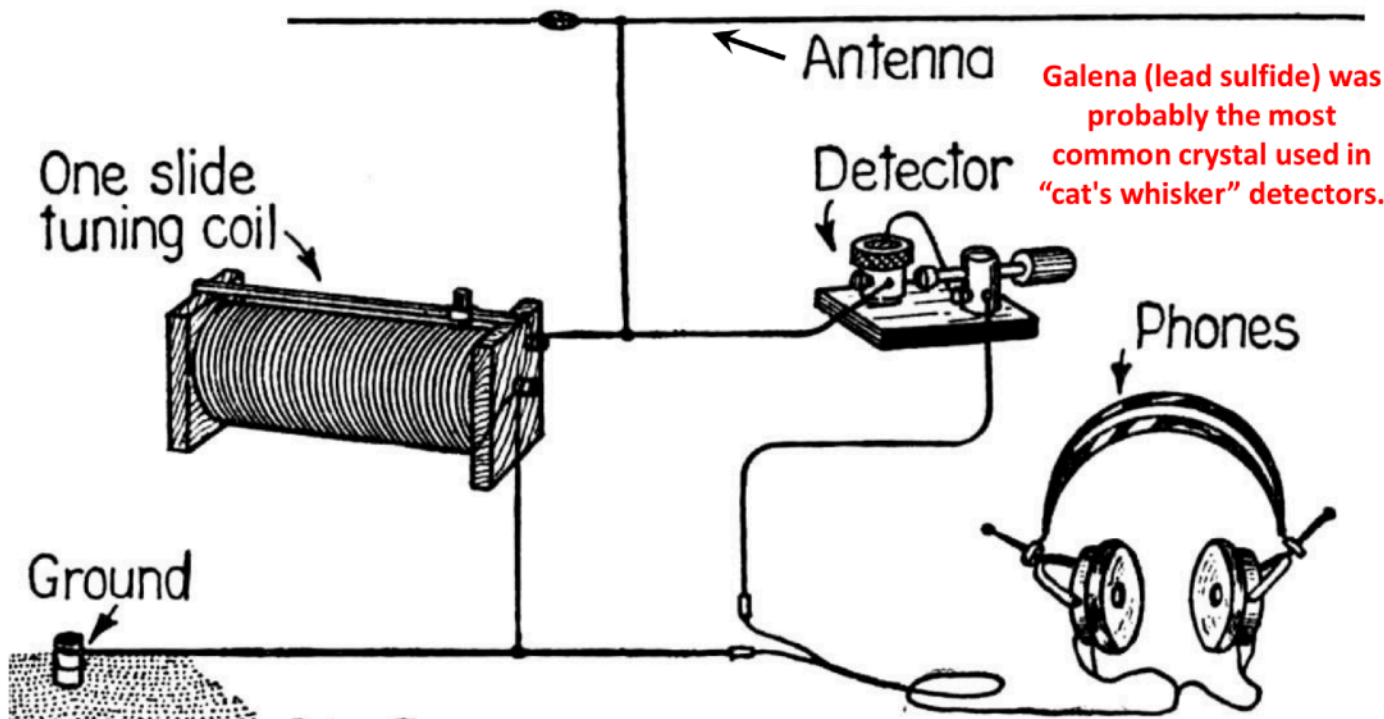

Galena (lead sulfide) was probably the most common crystal used in "cat's whisker" detectors.

Diagram from 1922 showing the circuit of a crystal radio. This common circuit did not use a tuning capacitor, but used the capacitance of the antenna to form the tuned circuit with the coil.

# A modern AM radio

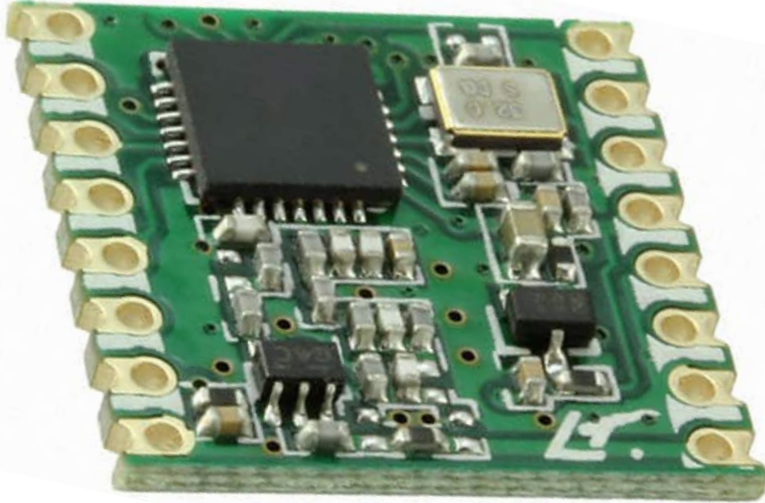

The AM band is rather low frequency:  
540 kHz - 1600 kHz  
Can just sample and process with DSP.

With digital electronics running at  
 $\sim 1$ GHz, even the FM range of  
88 - 108 MHz is low enough to sample  
and process.

This is done with "software defined radio". Configurable filters, and ADC then process in real time. Very flexible, e.g., directional, data path, etc.

