 


PHYS127AL Lecture 15

David Stuart, UC Santa Barbara

Non-ideal op-amp properties




Review: Op-amp golden rules

The op-amp golden rules were:

 - 1). No input current, $I_+ = 0$ and $I_- = 0$, i.e., $X_{in} = \infty$
- 2). $V_- = V_+$ with negative feedback

Or, output is enormous gain differential amp




This simple view allowed analyzing many op-amp circuits, but it is only a first approximation.

Now we'll see some of the corrections, or limitations of this model and how to mitigate them.



Rail-to-rail

What is the output of this circuit?

 



Rail-to-rail

  What is the output of this circuit? And this one?



Rail-to-rail

  What is the output of this circuit? And this one?



The golden answers are V_{DD} and V_{SS} .


The “non-ideal” answers are *a bit below* V_{DD} and *a bit above* V_{SS} .

Real op-amps can't go all the way to the power supply rails.

Rail-to-rail


Real op-amps can't go all the way to the power supply rails.

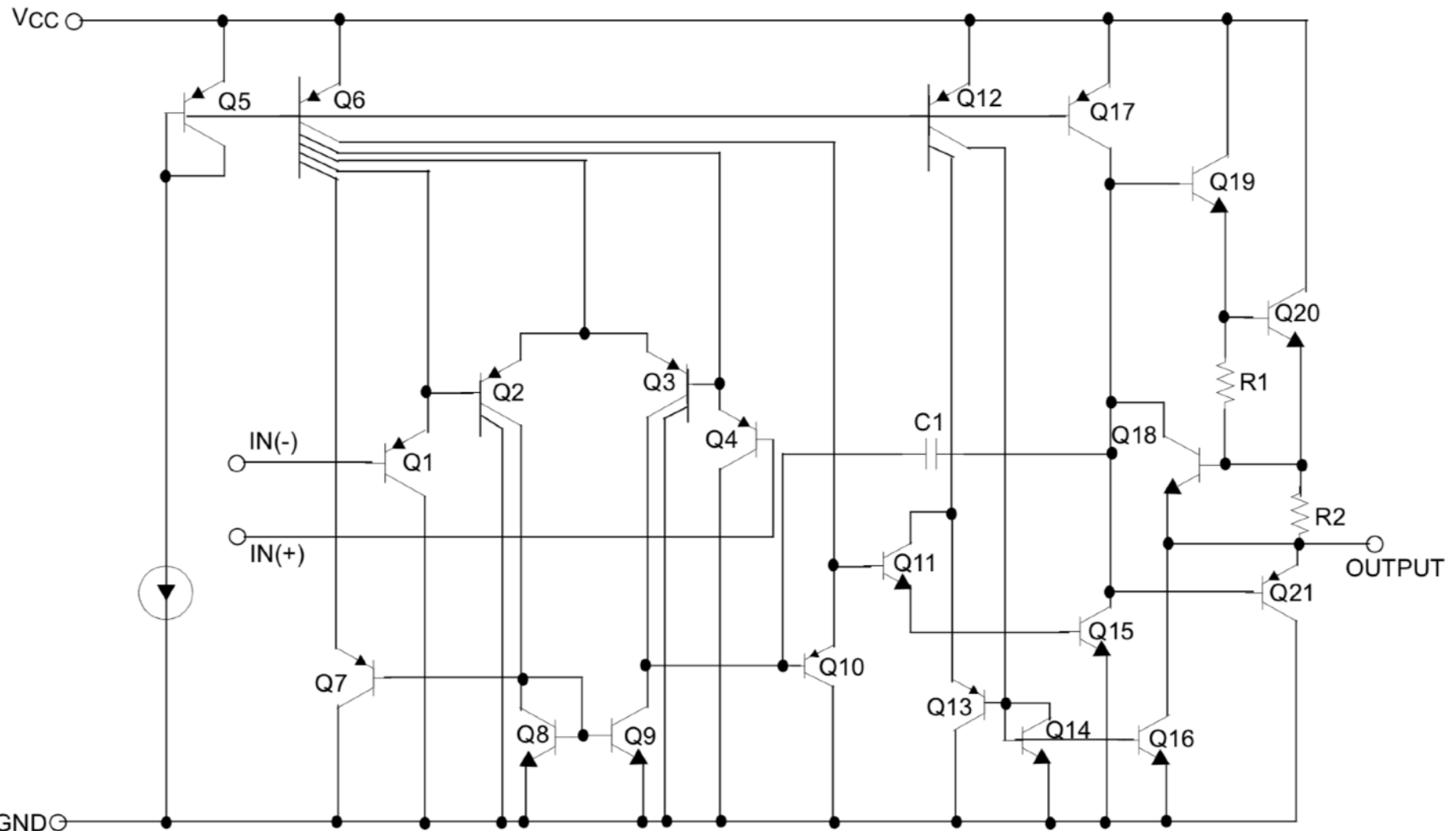E.g., here is a simplified schematic of the KA358; note the output stage.




Slew rate

What is the output of this circuit?

 

Slew rate



What is the output of this circuit?

 

The output has a maximum “slew rate” that is \sim linear.


KA358 slew rate is ~ 0.15 V/ μ s.
Fast amps can reach > 1000 V/ μ s.

  This limits speed, particularly for large V_{DD} .



Slew rate



What is the output of this circuit?

 

The output has a maximum “slew rate” that is \sim linear.

KA358 slew rate is $\sim 0.15 \text{ V}/\mu\text{s}$.
Fast amps can reach $> 1000 \text{ V}/\mu\text{s}$.

  This limits speed, particularly for large V_{DD} .




Also can have a propagation delay.

Roll off of open-loop gain

The gain degrades at high frequency

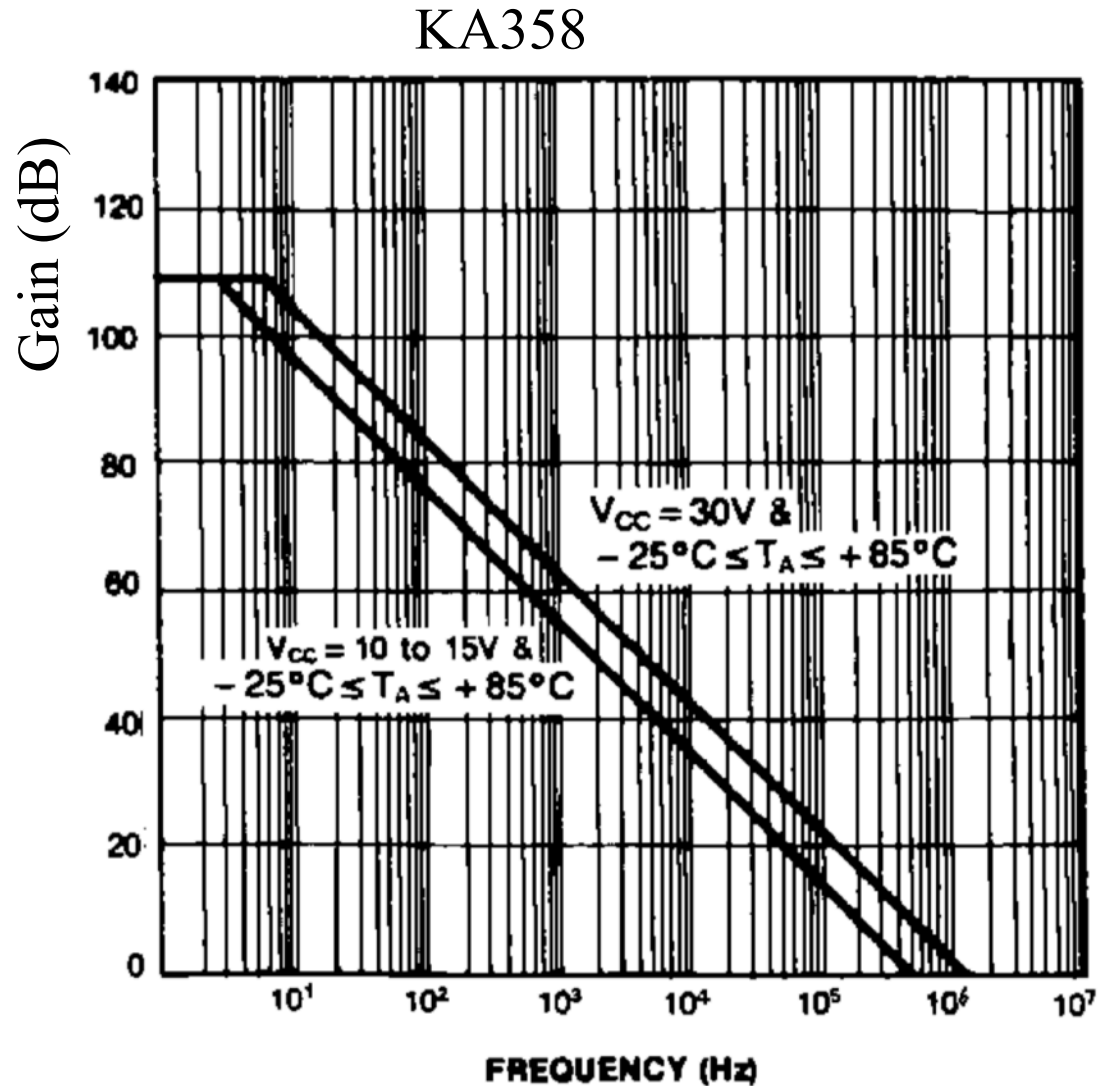Datasheet often specifies the “gain bandwidth product” which is frequency (aka bandwidth) at which open-loop gain falls to one.





Roll off of open-loop gain

The gain degrades at high frequency


Datasheet often specifies the “gain bandwidth product” which is frequency (aka bandwidth) at which open-loop gain falls to one.

  Roll off is often intentional to avoid oscillation at high frequency due to parasitic positive feedback.





Roll off of open-loop gain

The gain degrades at high frequency
(This op-amp has lower supply limits, 5V not 15V)

 


THS4304
\$6 op-amp

  

Input offset



What is the output of this circuit?

 

Input offset

What is the output of this circuit?


 
 
Nearly V_{DD} or V_{SS} . Which one it will be is set by "input offset voltage".




Input offset

What is the output of this circuit?

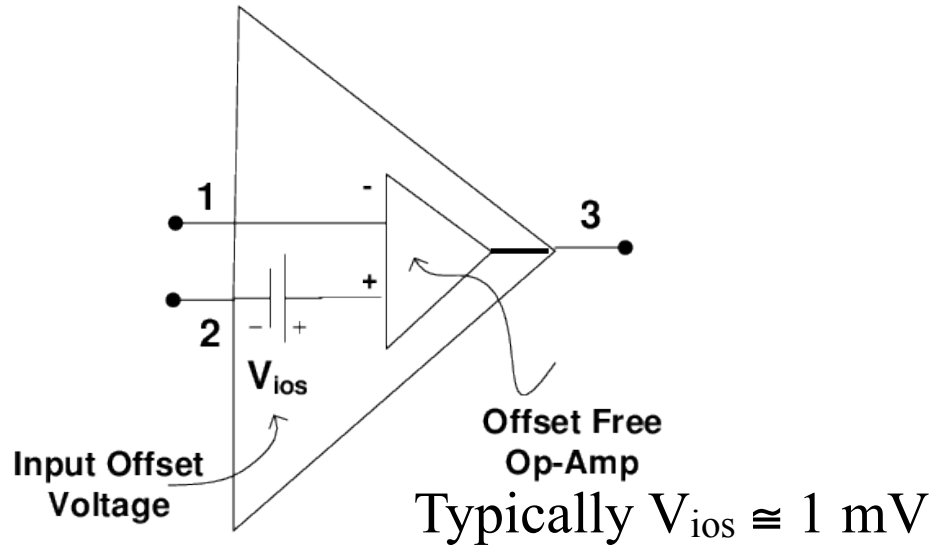  Nearly V_{DD} or V_{SS} . Which one it will be is set by "input offset voltage".





LM741 Pinout Diagram

 


Input offset

Typically $V_{ios} \cong 1 \text{ mV}$

  

Input offset current

What is the output of this circuit?

 


Input offset current

What is the output of this circuit?

The output “follows” the voltage across the capacitor.

 Golden rules say $I_+ = 0$ so capacitor maintains same charge.




Input offset current

What is the output of this circuit?

The output “follows” the voltage across the capacitor.

 Golden rules say $I_+ = 0$ so capacitor maintains same charge.



There is a small leakage current, typically 10's of pA to 10's of nA.


This limits stability time for integrators or S&H.

Input offset current

What is the output of this circuit?


The output “follows” the voltage across the capacitor.

 Golden rules say $I_+ = 0$ so capacitor maintains same charge.



There is a small leakage current, typically 10's of pA to 10's of nA. Most often I_{OS} is much smaller than I_B .

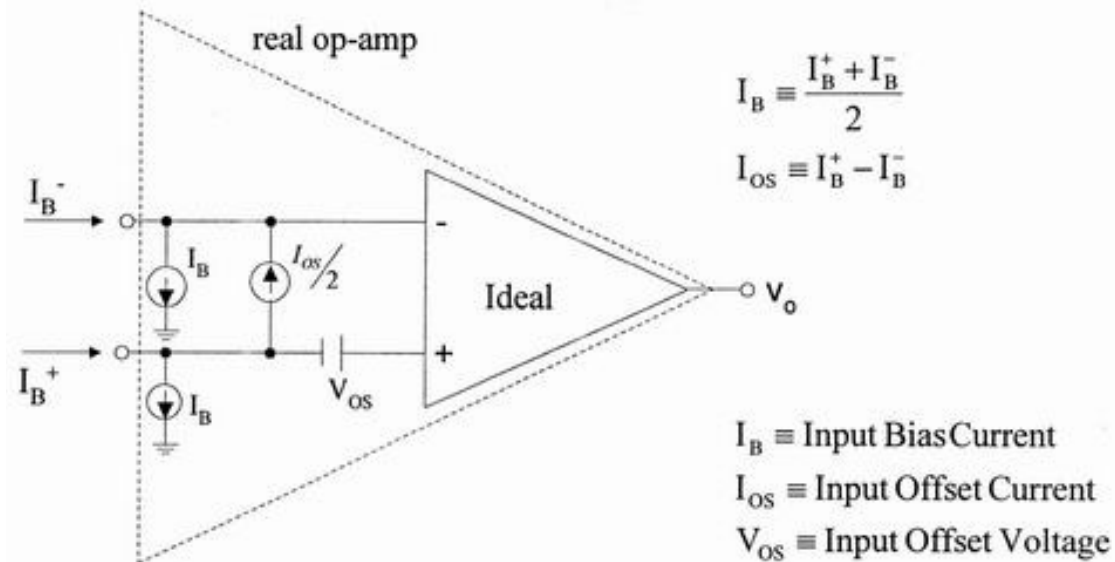
This limits stability time for integrators or S&H.



Input offset current

This biases an inverting amplifier with large resistors.

 Want R_1 large for input impedance, but $I_B * R$ is a voltage offset.




$10 \text{ nA} * 1M = 10\text{mV}$. Then gain of 10 gives an output bias of 100 mV.

Input offset current

This biases an inverting amplifier with large resistors.

 Want R_1 large for input impedance, but $I_B * R$ is a voltage offset.




$10 \text{ nA} * 1\text{M} = 10\text{mV}$. Then gain of 10 gives an output bias of 100 mV.

Solution is to give the other input the same voltage offset; works if I_{OS} small compared to I_B .


Input offset current

 Similar solution works for non-inverting amplifiers.




Input offset current

 Similar solution works for non-inverting amplifiers.



Input offset current

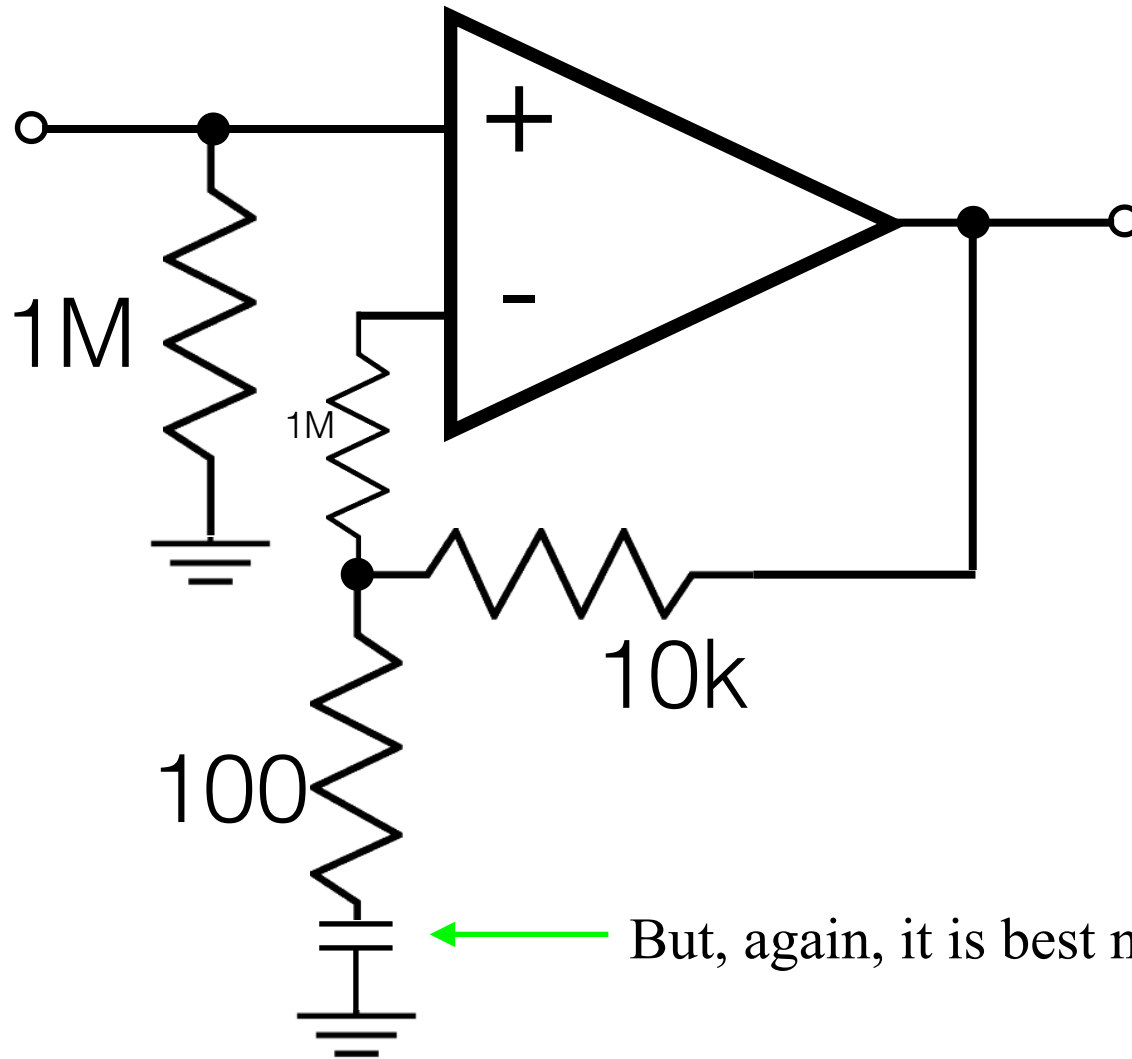Similar solution works for non-inverting amplifiers.



← But, again, it is best not to amplify the DC offsets.

Noise

There is intrinsic noise in the inputs.

Typically $10 \text{ nV}/\sqrt{\text{Hz}}$ and $1 \text{ pA}/\sqrt{\text{Hz}}$

Really only critical for precision measurements, and we will talk about ways to suppress it next week.

Pick your optimum

There are thousands of op-amp designs. They optimize on various parameters:

Rail-to-rail

Power supply range

Power consumption

Speed

 GBP, Slew-rate

Input bias current

Input offset current

Input offset voltage

Flexibility

 Multi-circuits

 Offset-null

 Package

Operating temperature range

Price

 Often dominated by batch size.

Pick your optimum

There are thousands of op-amp designs. They optimize on various parameters:

Rail-to-rail

Power supply range

Power consumption

Speed

GBP, Slew-rate

Input bias current

Input offset current

Input offset voltage

Flexibility

Multi-circuits

Offset-null

Package

Operating temperature range

Price

Often dominated by batch size.

Electronics component vendors:

[Newark](#)

[Digikey](#)

[Arrow](#)

Lab 9 and extra credit projects





Lab 9 will be a grab-bag of options

No lab 10 during dead week.


That time available for extra credit project work.

Extra credit projects due (ELOG complete) Sunday, June 13th at noon.

Email me when you have completed it.

    

What is wrong with this circuit?

 

What is wrong with this circuit?

