

# PHYS127AL Lecture 6

David Stuart, UC Santa Barbara


Transistors and amplifiers


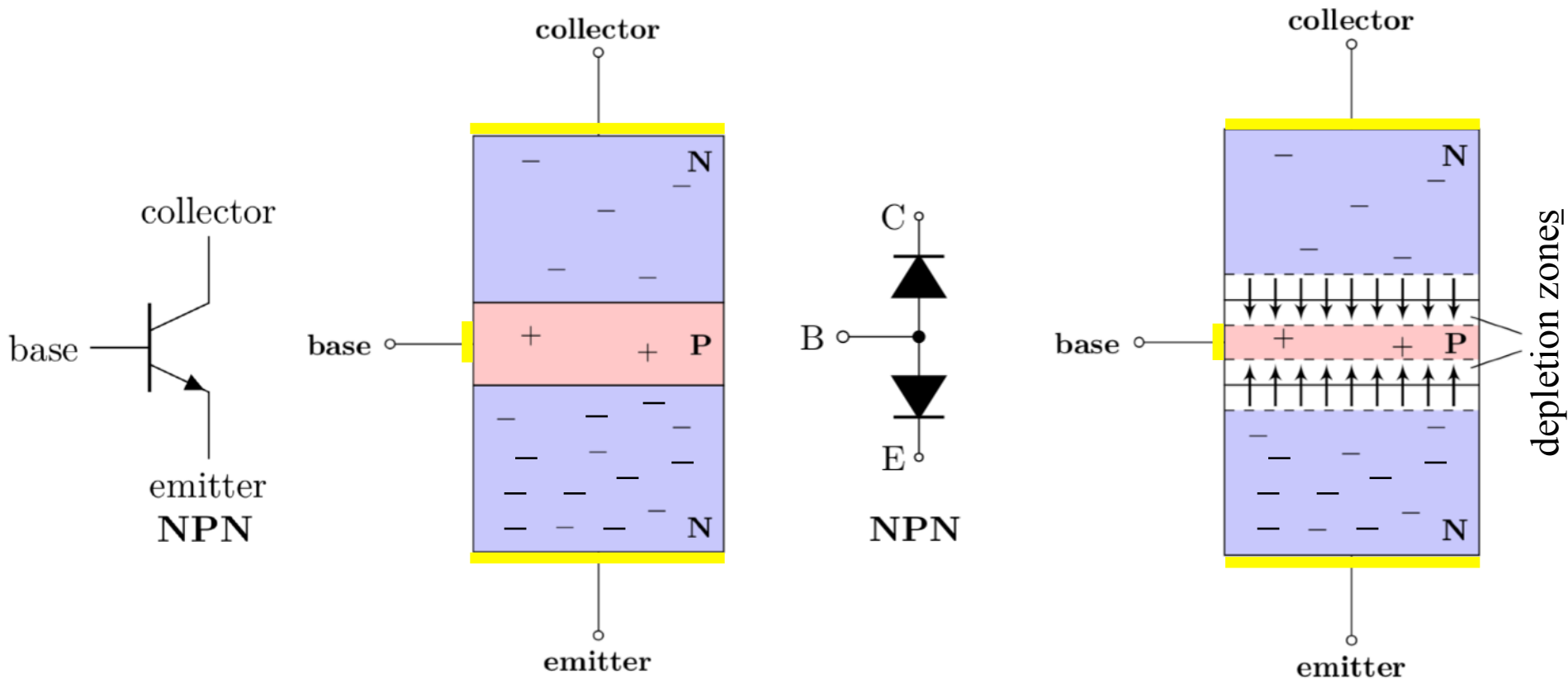
# Transistors

A transistor operates by amplifying current.  
It is *active*, meaning more power out than in.  
Previous components were *passive*.


Made by sandwiching a thin, lightly-doped p-type layer between n-type regions.


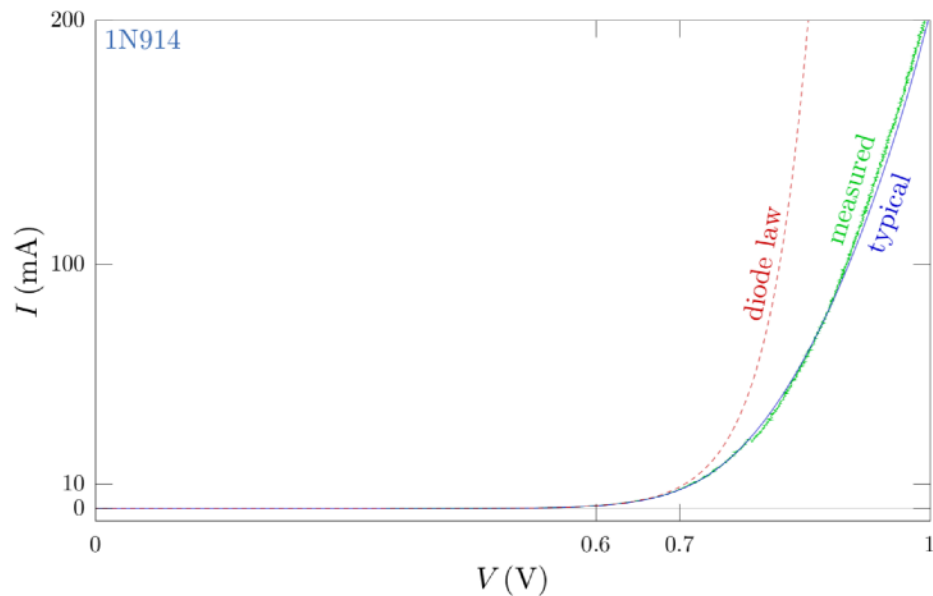
# Transistors


If we have a voltage across the base-emitter junction  $> 0.6$  V it becomes forward biased.

Negative charge carriers move from the emitter to the base, but they can also move across the field region to the collector.



This corresponds to a small current into the base and a larger current into the collector.

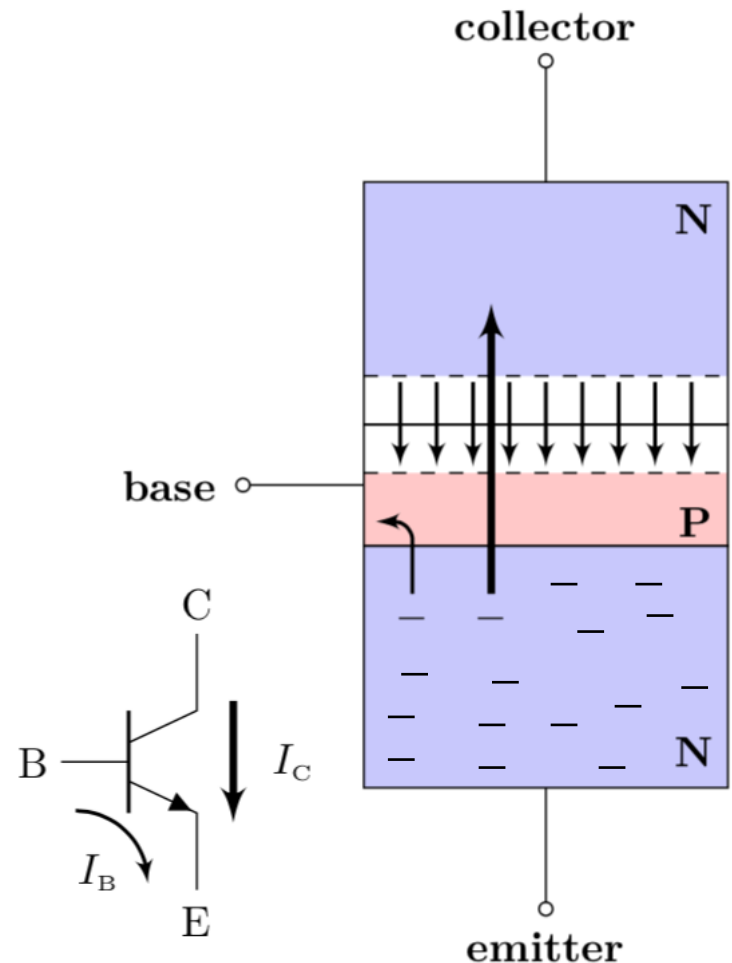$I_B$  controls  $I_C$  and amplifies it by a factor  $\beta \cong 100$ .




# Transistor rules of operation

1).  $V_{BE} = 0.6 \text{ V}$  or the transistor is off  
I.e.,  $V_B = V_E + 0.6 \text{ V}$   
Once the transistor is on,  $\Delta V_B = \Delta V_E$ .

2).  $I_C = \beta I_B$ .  
And by charge conservation  $I_E = I_B + I_C$  so  $I_E \cong I_C$

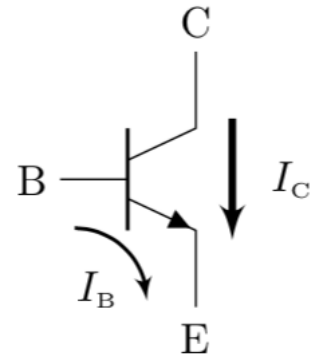3).  $V_{CE} > 0.2 \text{ V}$

With these simple rules we can analyze most transistor circuits.  
We'll add some nuance later.



# Transistor rules of operation

1).  $V_{BE} = 0.6 \text{ V}$  or the transistor is off

I.e.,  $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on,  $\Delta V_B = \Delta V_E$ .


2).  $I_C = \beta I_B$ .

And by charge conservation  $I_E = I_B + I_C$  so  $I_E \cong I_C$

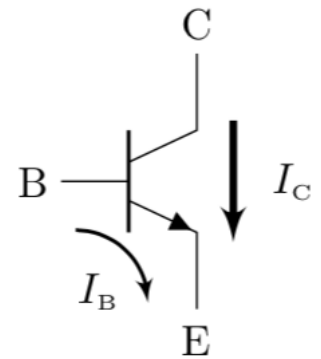
3).  $V_{CE} > 0.2 \text{ V}$

With these simple rules we can analyze most transistor circuits.  
We'll add some nuance later.

The 2N3904 is an NPN transistor.  
You also have others we will discuss later.



2N3904

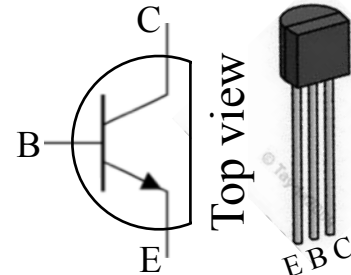

# Transistor rules of operation

1).  $V_{BE} = 0.6 \text{ V}$  or the transistor is off

I.e.,  $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on,  $\Delta V_B = \Delta V_E$ .

2).  $I_C = \beta I_B$ .

And by charge conservation  $I_E = I_B + I_C$  so  $I_E \cong I_C$

3).  $V_{CE} > 0.2 \text{ V}$

With these simple rules we can analyze most transistor circuits.  
We'll add some nuance later.


The 2N3904 is an NPN transistor.

You also have others we will discuss later.


Some terminology:

The power supply connected to the collector is called  $V_{CC}$ .

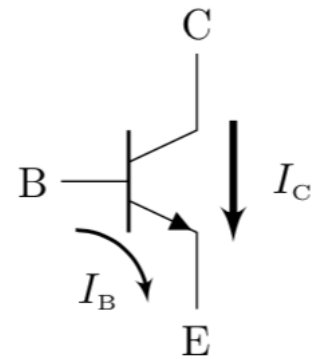The power supply connected to the emitter is called  $V_{EE}$ .




2N3904

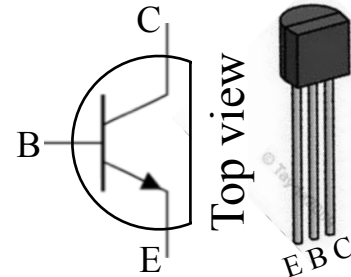

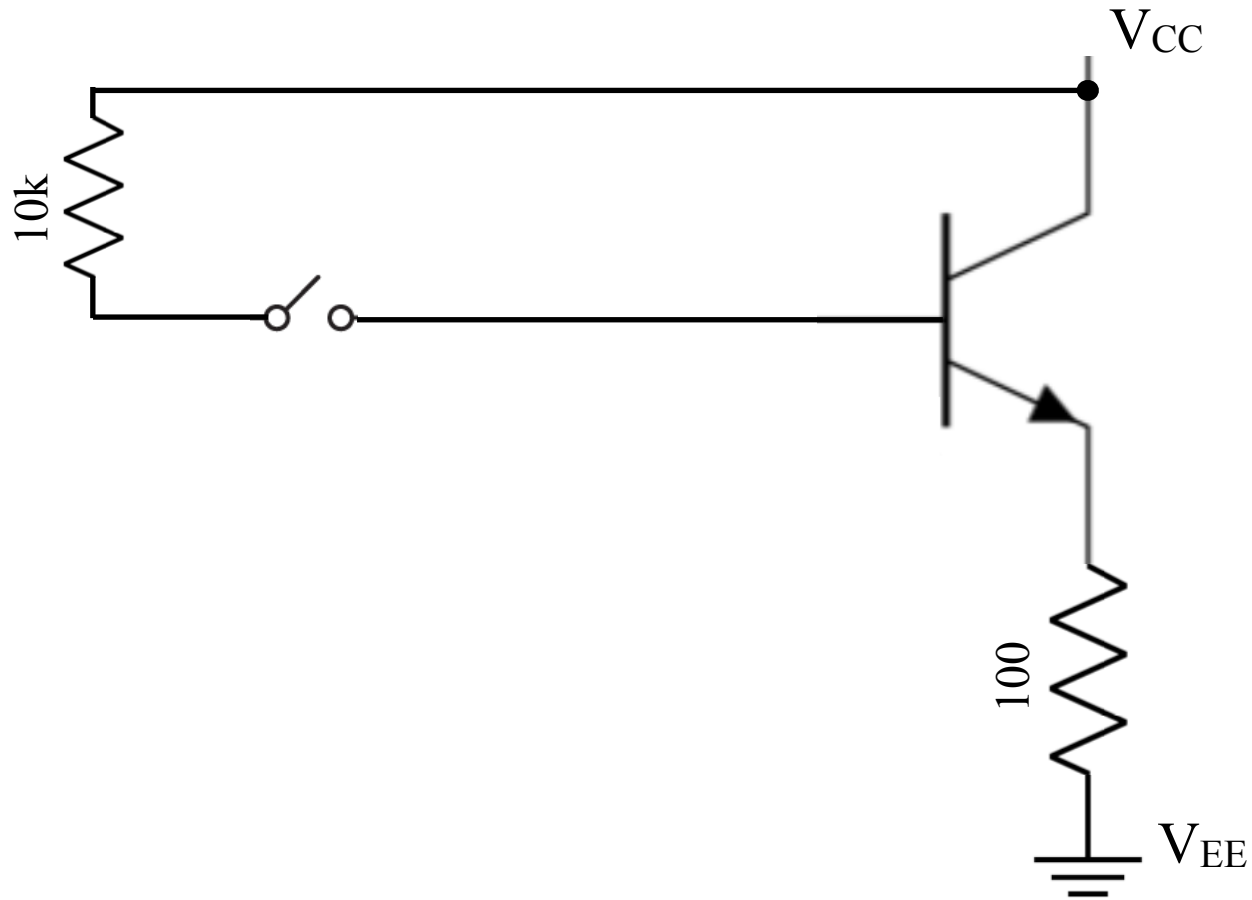
# Simplest transistor circuit

A transistor allows us to switch a large current with a small current.


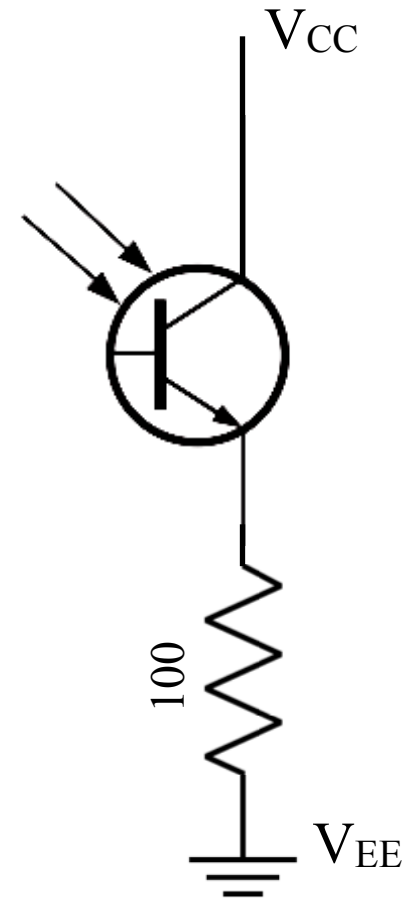
# Simplest transistor circuit


A transistor allows us to switch a large current with a small current.





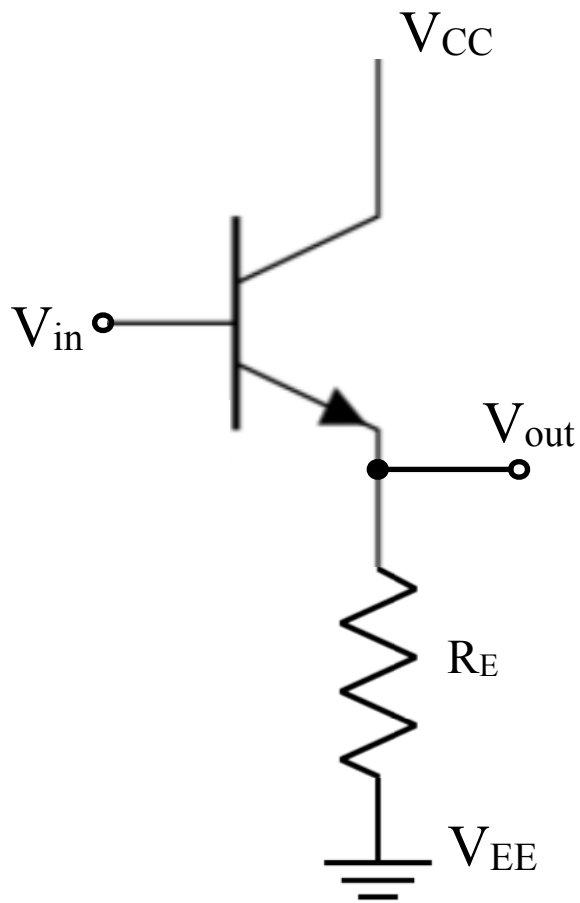
# Emitter follower

This transistor circuit has the output “follow” the input, with a 0.6 V drop.




$$V_{in} = 4 + 2 \sin \omega t$$

$$V_{out} = 3.4 + 2 \sin \omega t$$

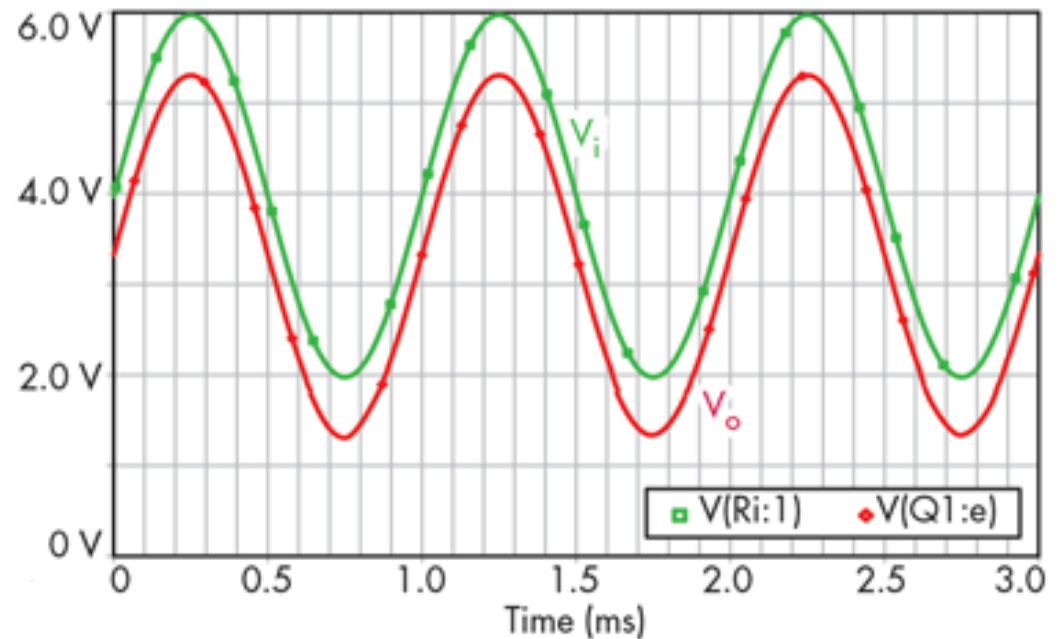

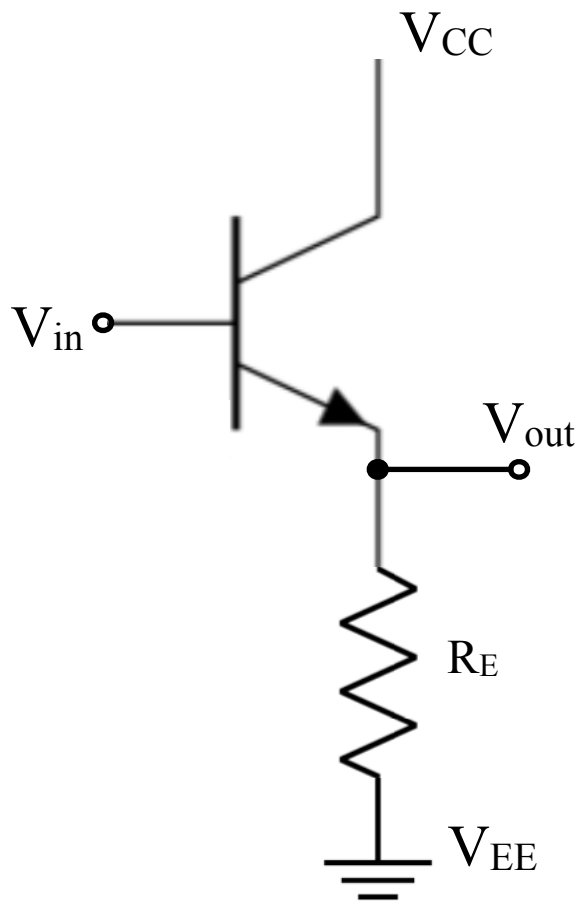
# Emitter follower

This transistor circuit has the output “follow” the input, with a 0.6 V drop.




$$V_{in} = 2.2 + 2 \sin \omega t$$
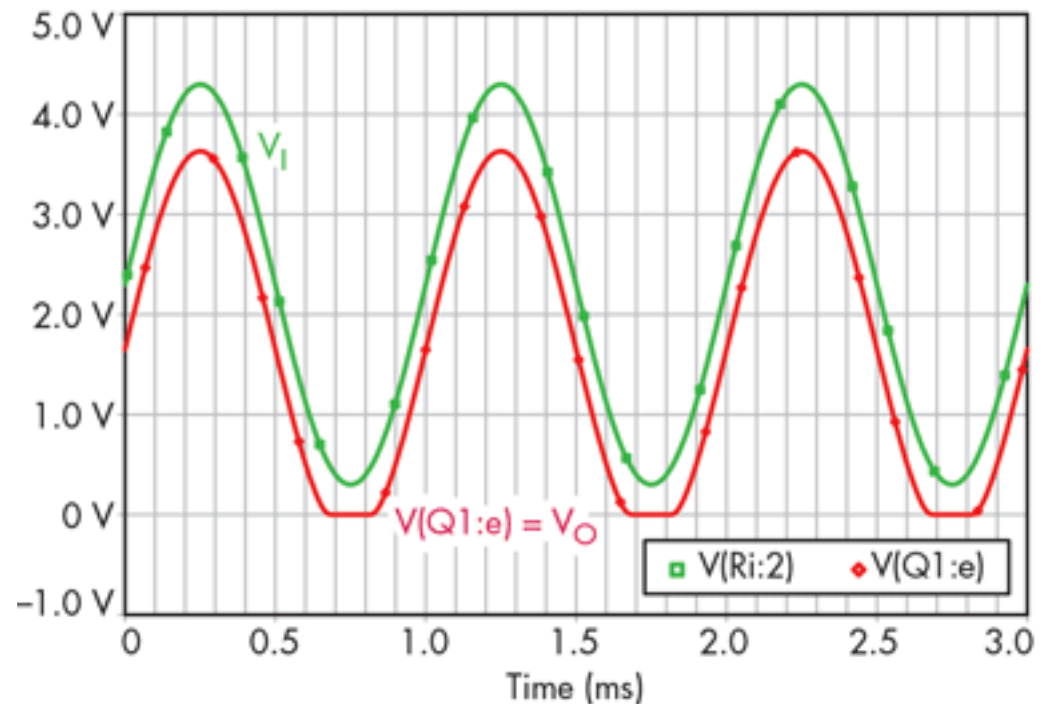
$$V_{out} = 1.6 + 2 \sin \omega t \quad \text{but output clips at 0 V}$$


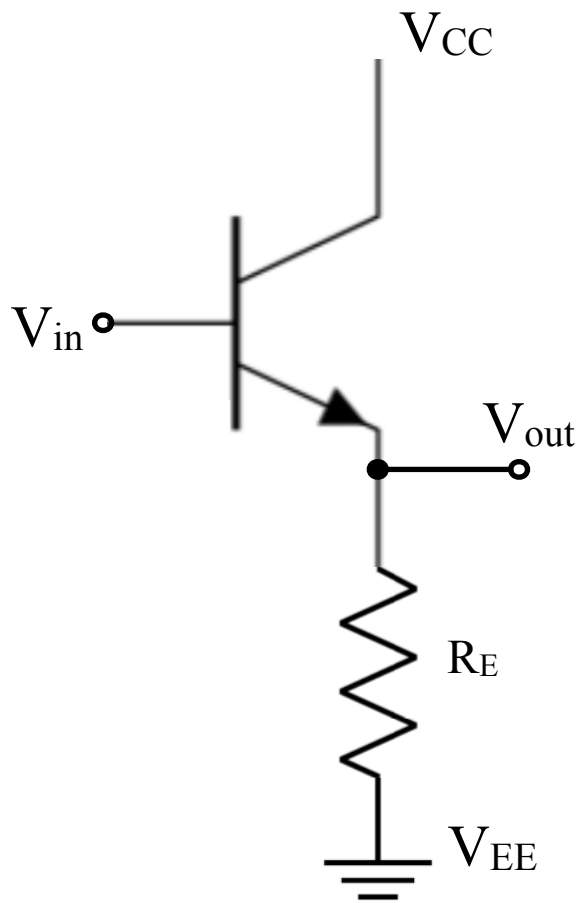
# Emitter follower


This transistor circuit has the output “follow” the input, with a 0.6 V drop.



$$V_{in} = 2.2 + 2 \sin \omega t$$


$$V_{out} = 1.6 + 2 \sin \omega t \quad \text{but output clips at 0 V}$$

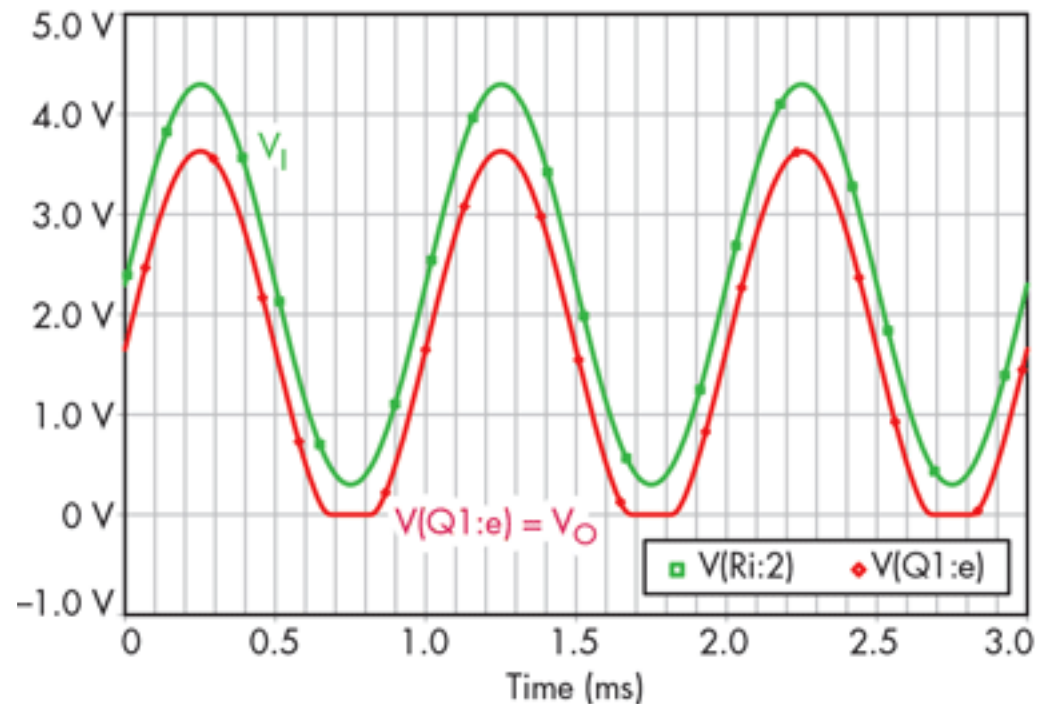We will soon find work-arounds to avoid clipping.


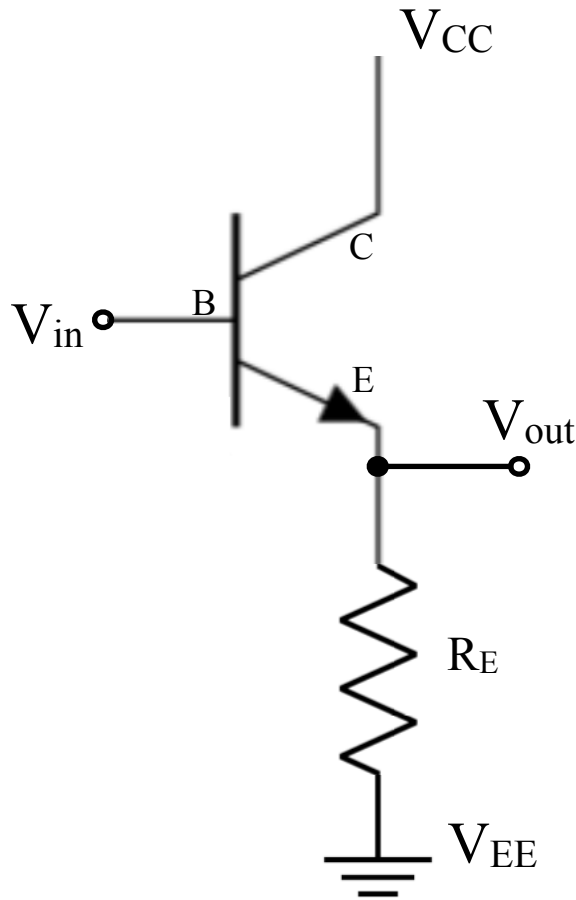
# Emitter follower

The benefit here is increased input impedance. Recall that impedance is  $R = \Delta V / \Delta I$



Without the transistor we need to flow  $\Delta I = \Delta V / R_E$  to change  $V_{in}$  by  $\Delta V$

With the transistor, we can calculate  $R_{in}$  from

$$R_{in} = \Delta V_{in} / \Delta I_{in} = \Delta V_B / \Delta I_B$$


The base current is  $1/\beta$  of the emitter current, since  $I_E \approx I_C = \beta I_B$ . So,

$$R_{in} = \Delta V_{in} / \Delta I_{in} = \Delta V_B / (\Delta I_E / \beta) = \beta \Delta V_B / \Delta I_E$$

We also had from the transistor rules that  $V_B = V_E + 0.6$ , so  $\Delta V_B = \Delta V_E$ , so


$$R_{in} = \beta \Delta V_B / \Delta I_E = \beta \Delta V_E / \Delta I_E = \beta R_E$$

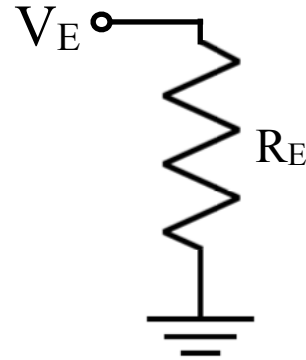The input impedance is  $\beta$  times larger than  $R_E$ .  
The transistor amplifies the impedance by  $\beta \approx 100$ .


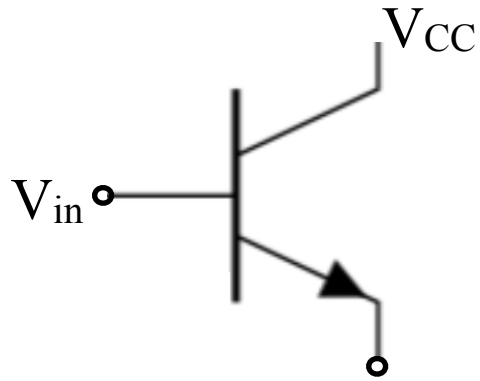
# Emitter follower

The benefit here is increased input impedance. Recall that impedance is  $R = \Delta V / \Delta I$





The transistor amplifies the impedance by  $\beta \approx 100$ .

This is the way to make each stage have large input impedance; put a transistor at its input.


The emitter will follow the *variations* in the input. The DC shift of 0.6 V is not a problem because *the variation of  $V_{in}$  is the signal*.

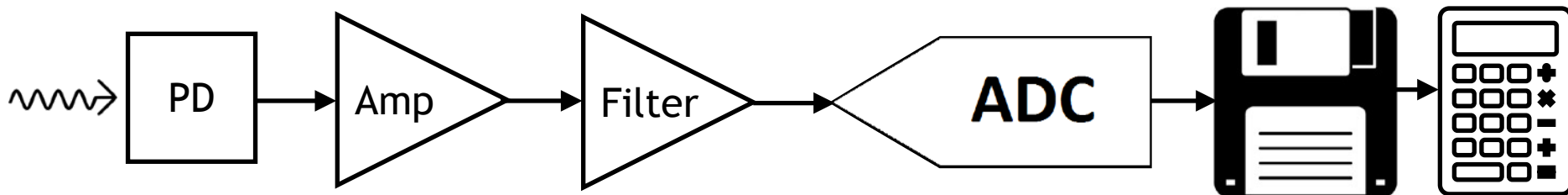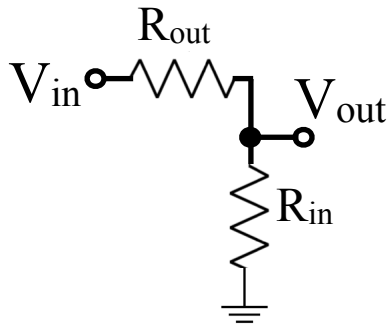The additional power needed is supplied by  $V_{CC}$ .


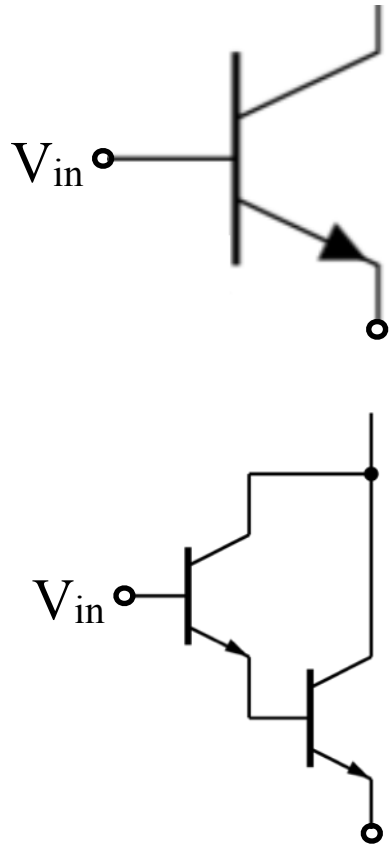
# Emitter follower

The benefit here is increased input impedance. Recall that impedance is  $R = \Delta V / \Delta I$




The transistor amplifies the impedance by  $\beta \approx 100$ .

This is the way to make each stage have large input impedance; put a transistor at its input.

The emitter will follow the *variations* in the input. The DC shift of 0.6 V is not a problem because *the variation of  $V_{in}$  is the signal*.


The additional power needed is supplied by  $V_{CC}$ .

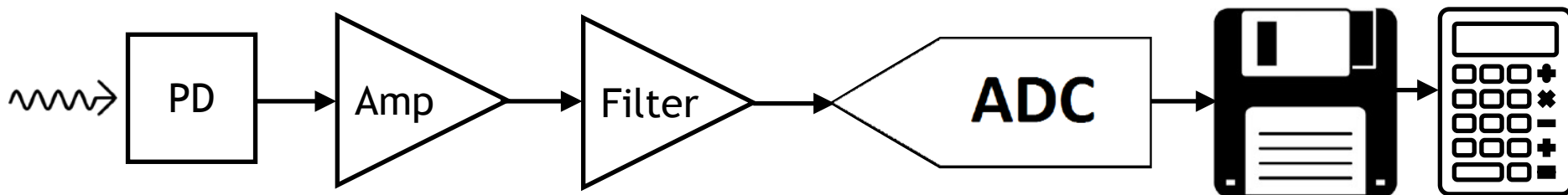Can get a factor of  $\beta^2$  with two followers. (Darlington configuration.) However, that costs two diode drops.



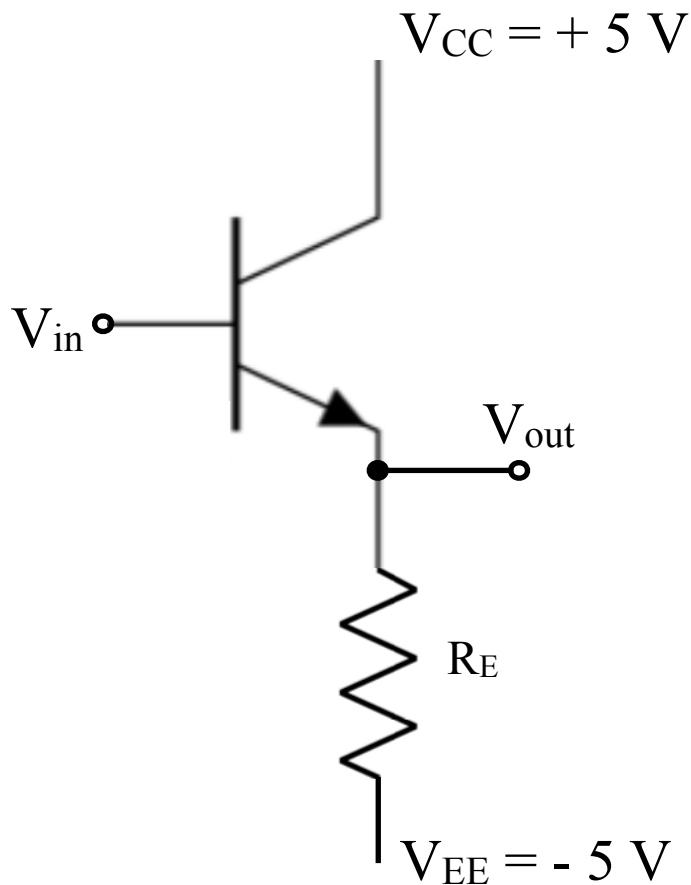
# Emitter follower

We can remove the clipping at 0 V by setting  $V_{EE}$  to a negative supply.



$$V_{in} = 2.2 + 2 \sin \omega t$$


$$V_{out} = 1.6 + 2 \sin \omega t$$

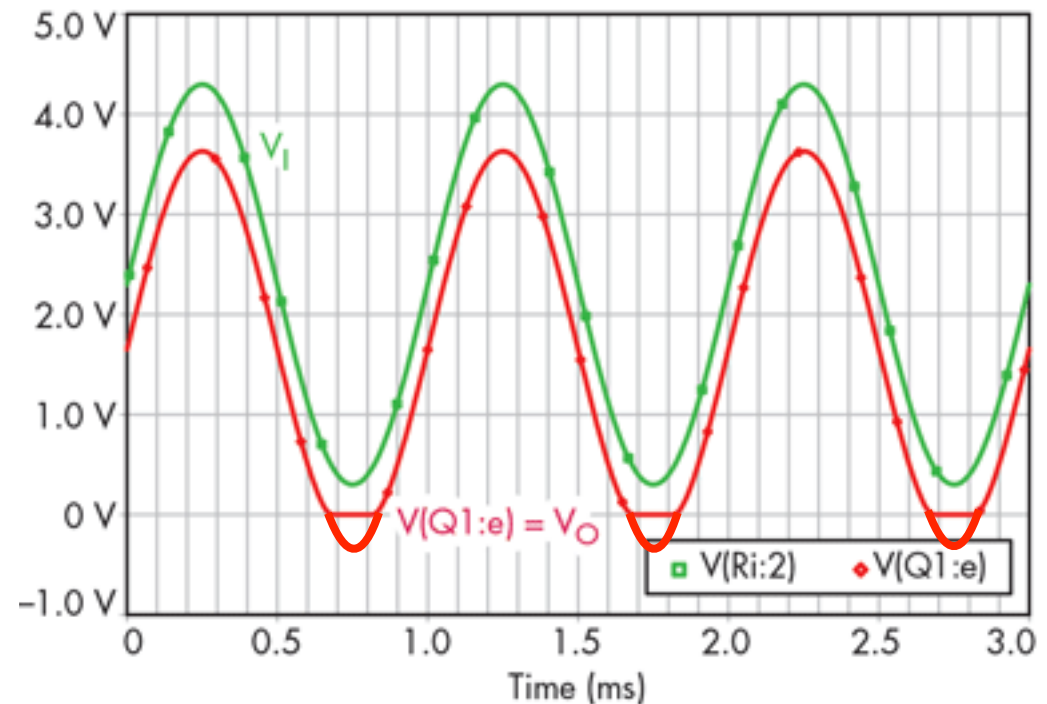

Output clips at  $V_{CC}$  and 0.6 V above  $V_{EE}$ .
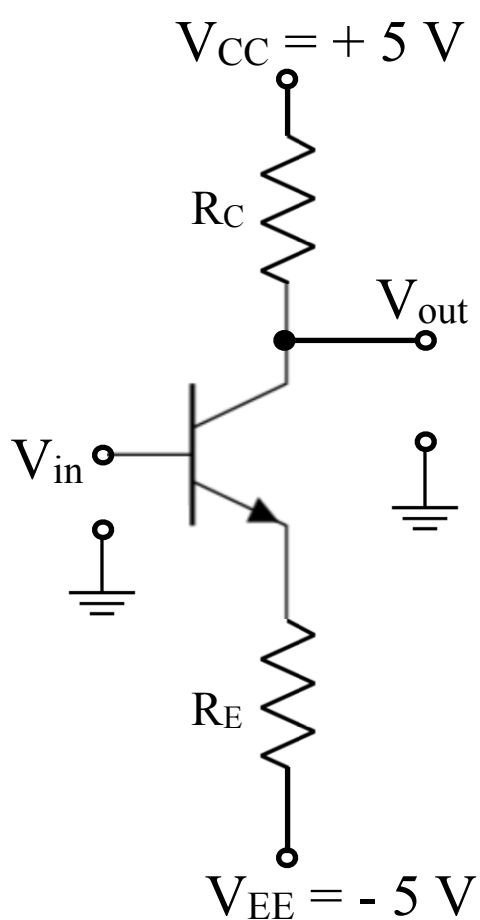
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.




The input and output are with respect to ground, but we don't really need to show ground here. The transistor only cares about relative voltage differences.


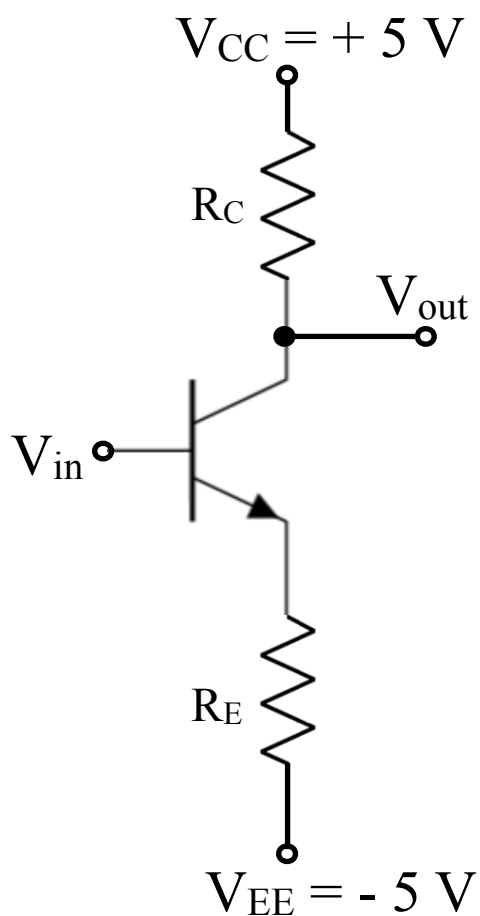
# Common-emitter amplifier


We can use the current amplification of the transistor to get voltage amplification.



The input and output are with respect to ground, but we don't really need to show ground here. The transistor only cares about relative voltage differences. So no explicit ground references need to be shown.
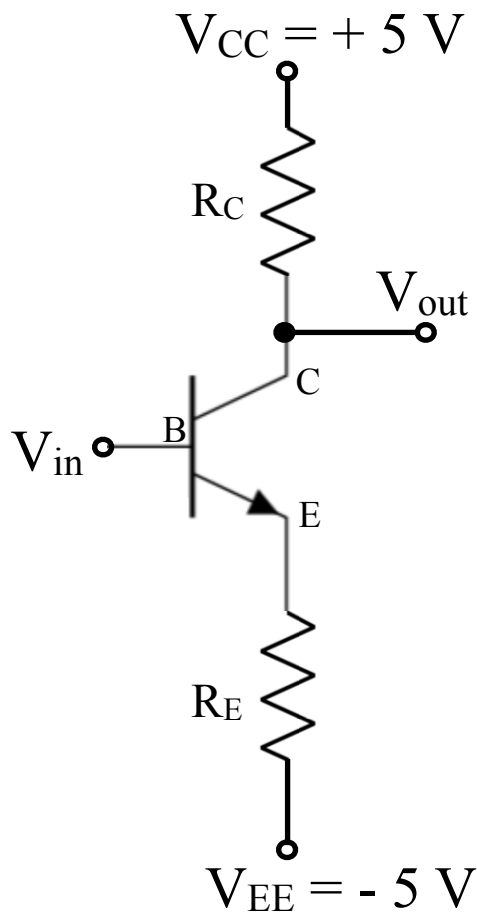
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.




The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .  
So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .  
First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = ?$$

$$\text{and } \Delta V_E = ?$$
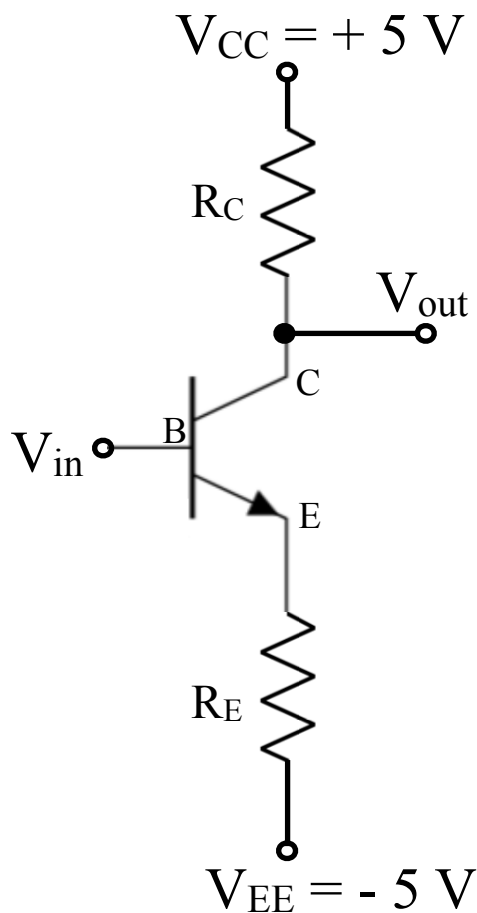
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .


So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .

First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$
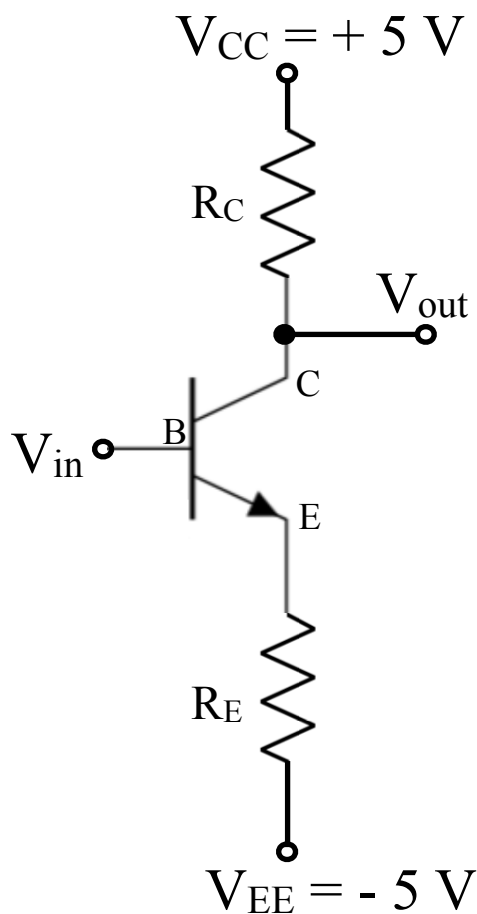
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .

So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .


First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$

$$V_{out} = ?$$
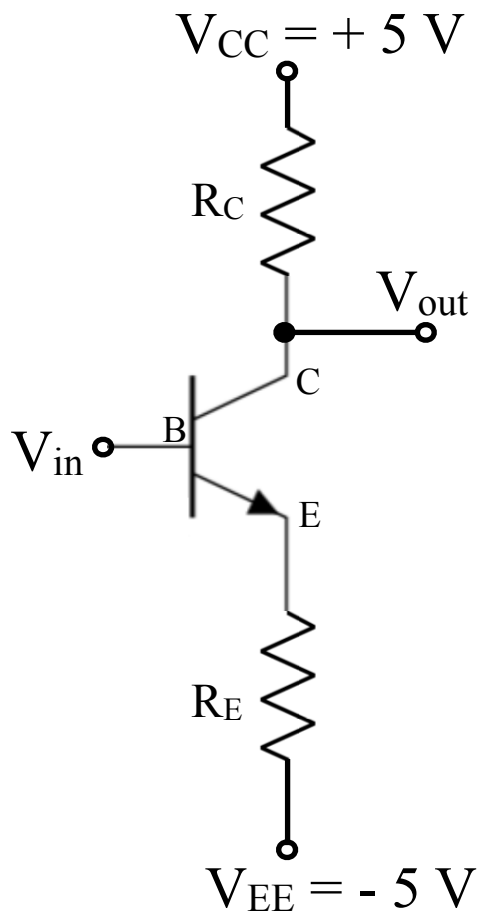
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .

So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .

First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .


$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$

$$V_{out} = V_{CC} - I_C R_C \cong V_{CC} - I_E R_C. \quad \text{Because } I_E = I_B + I_C \text{ \& } I_E \cong I_C$$

$$I_E = ?$$
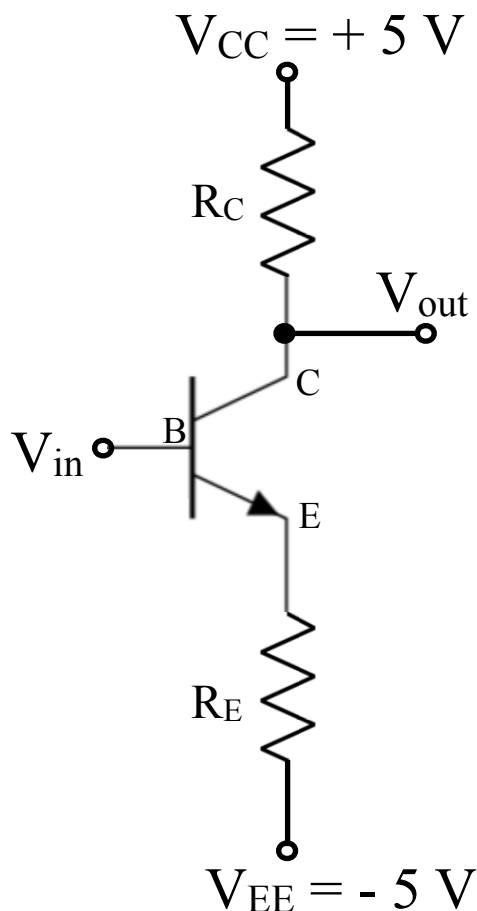
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .

So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .

First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$

$$V_{out} = V_{CC} - I_C R_C \cong V_{CC} - I_E R_C. \quad \text{Because } I_E = I_B + I_C \text{ \& } I_E \cong I_C$$

$$I_E \text{ can be found from } V_E - I_E R_E = V_{EE}. \quad \text{So } I_E = (V_E - V_{EE})/R_E.$$


$$V_{out} = V_{CC} - I_E R_C = V_{CC} - (V_E - V_{EE})R_C/R_E$$

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E)$$

$$\Delta V_{out} = ?$$
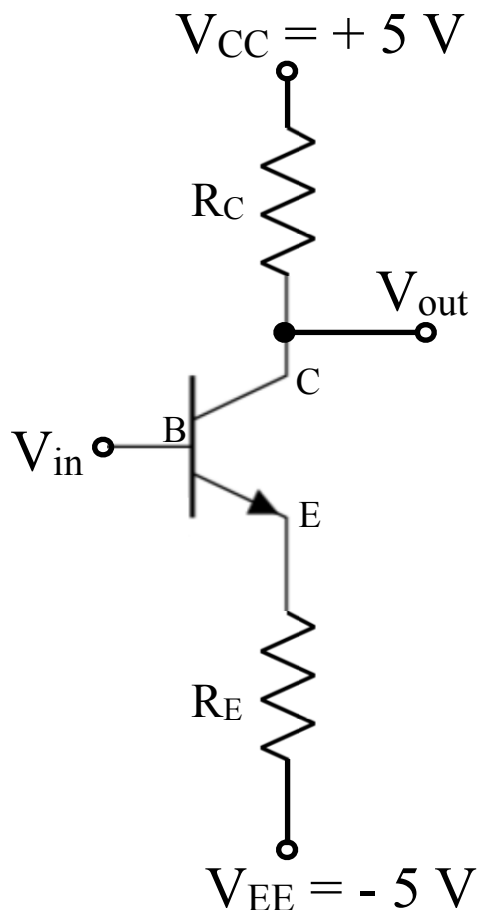
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .

So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .

First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$

$V_{out} = V_{CC} - I_C R_C \cong V_{CC} - I_E R_C$ . Because  $I_E = I_B + I_C$  &  $I_E \cong I_C$   
 $I_E$  can be found from  $V_E - I_E R_E = V_{EE}$ . So  $I_E = (V_E - V_{EE})/R_E$ .

$$V_{out} = V_{CC} - I_E R_C = V_{CC} - (V_E - V_{EE})R_C/R_E$$

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E)$$

$$\Delta V_{out} = -\Delta V_E(R_C/R_E) = -\Delta V_B(R_C/R_E) = -\Delta V_{in}(R_C/R_E)$$


$$\text{Gain} = \Delta V_{out} / \Delta V_{in} = -R_C/R_E$$

Negative gain OK for music.

Choose amplification by choosing resistance values.
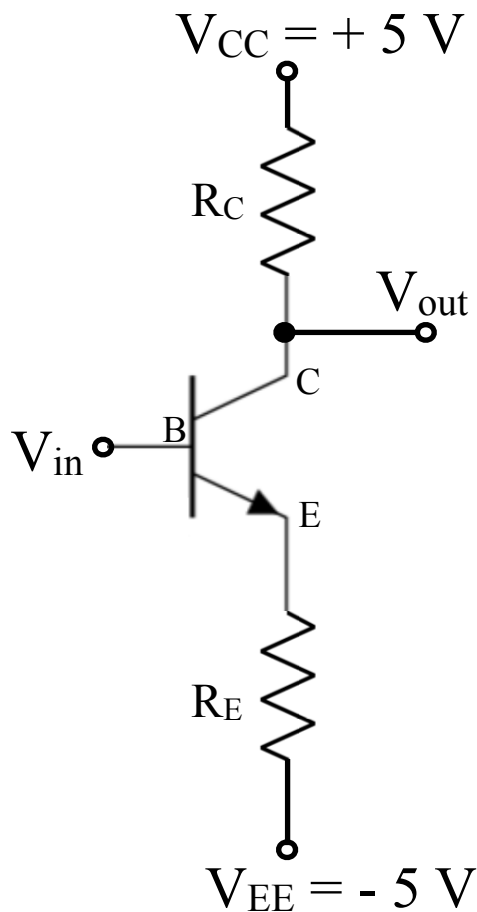
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.



The signal is  $\Delta V_{in}$  not just the value of  $V_{in}$ .

So we want to calculate both  $V_{out}$  and  $\Delta V_{out}$ .

First we'll do the DC part,  $V_{in}$ , then the AC part,  $\Delta V_{in}$ .

$$V_E = V_B - 0.6\text{ V} = V_{in} - 0.6\text{ V} \quad \text{and} \quad \Delta V_E = \Delta V_B = \Delta V_{in}$$

$V_{out} = V_{CC} - I_C R_C \cong V_{CC} - I_E R_C$ . Because  $I_E = I_B + I_C$  &  $I_E \cong I_C$   
 $I_E$  can be found from  $V_E - I_E R_E = V_{EE}$ . So  $I_E = (V_E - V_{EE})/R_E$ .

$$V_{out} = V_{CC} - I_E R_C = V_{CC} - (V_E - V_{EE})R_C/R_E$$

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E)$$

$$\Delta V_{out} = -\Delta V_E(R_C/R_E) = -\Delta V_B(R_C/R_E) = -\Delta V_{in}(R_C/R_E)$$

$$\text{Gain} = \Delta V_{out} / \Delta V_{in} = -R_C/R_E$$

Negative gain OK for music.

Choose amplification by choosing resistance values.





# Common-emitter amplifier



We can use the current amplification of the transistor to get voltage amplification.

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E) \quad \& \quad \Delta V_{out} = -\Delta V_{in}(R_C/R_E)$$

The AC response matters for the signal amplification, but the DC offset matters for clipping.

Transistor requires:  $V_{out} < V_{CC}$  and  $V_{out} > V_E + 0.2$

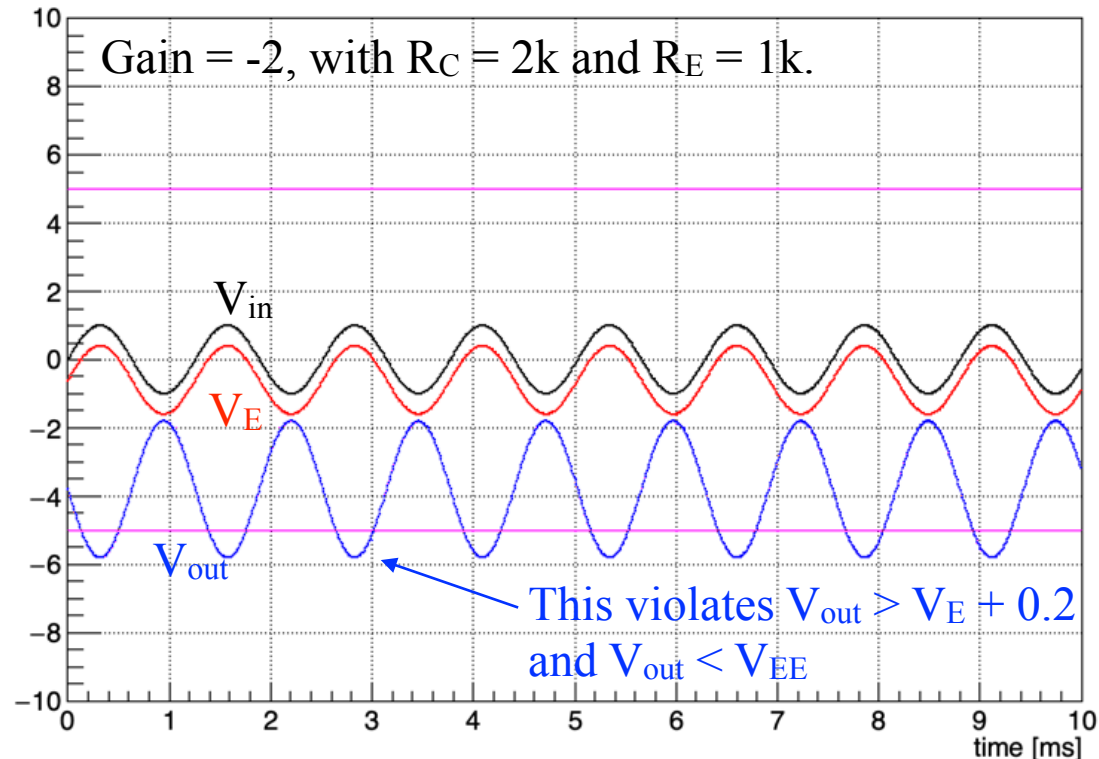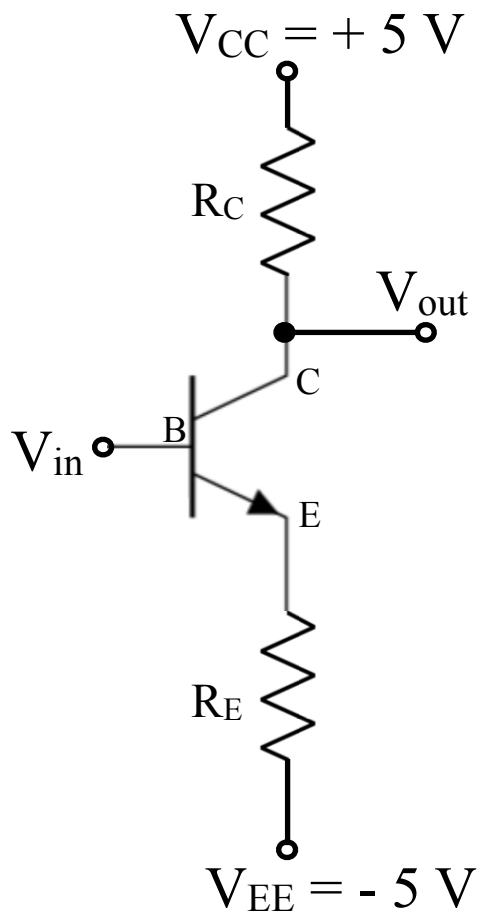Can't have  $V_{in}$  and  $V_{out}$  both oscillating around zero.



# Common-emitter amplifier



We can use the current amplification of the transistor to get voltage amplification.

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E) \quad \& \quad \Delta V_{out} = -\Delta V_{in}(R_C/R_E)$$

The AC response matters for the signal amplification, but the DC offset matters for clipping.


Transistor requires:  $V_{out} < V_{CC}$  and  $V_{out} > V_E + 0.2$

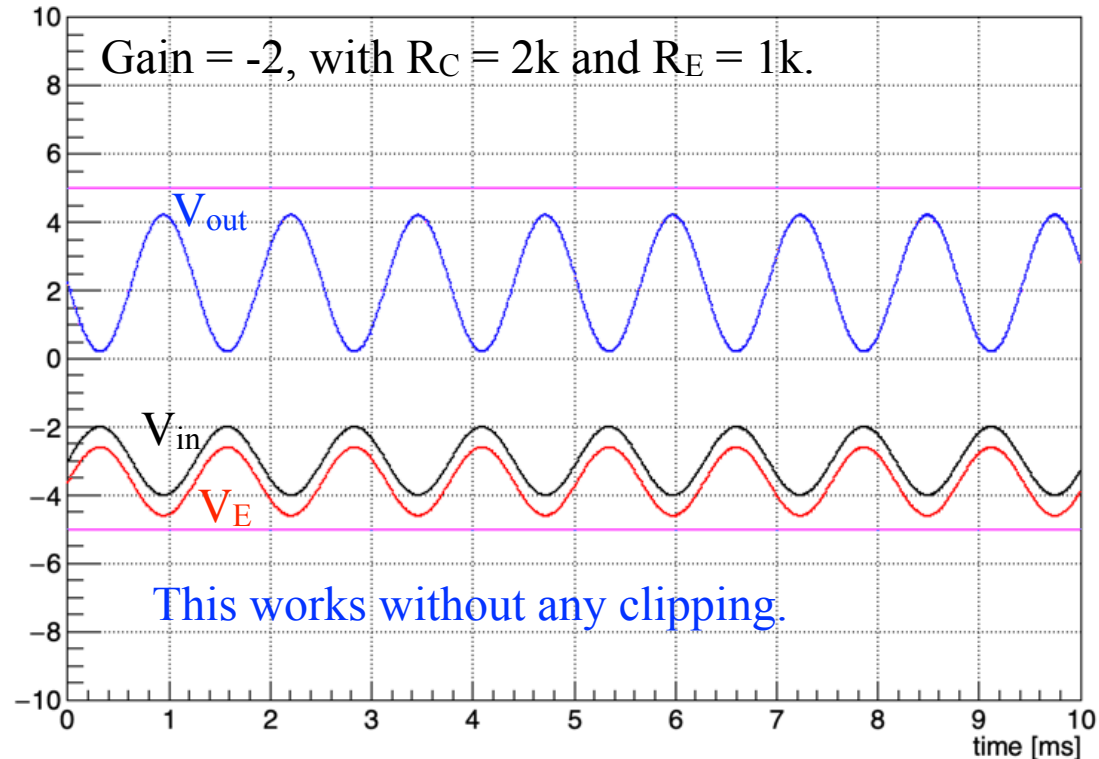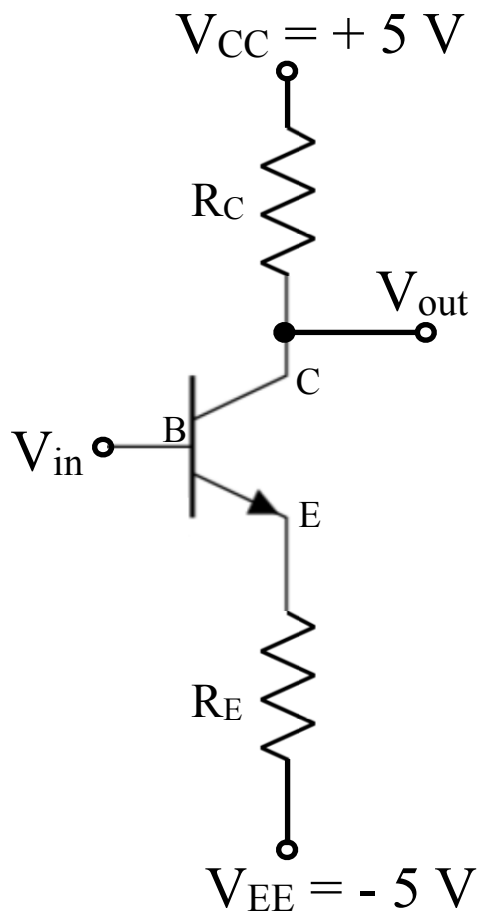Can't have  $V_{in}$  and  $V_{out}$  both oscillating around zero.


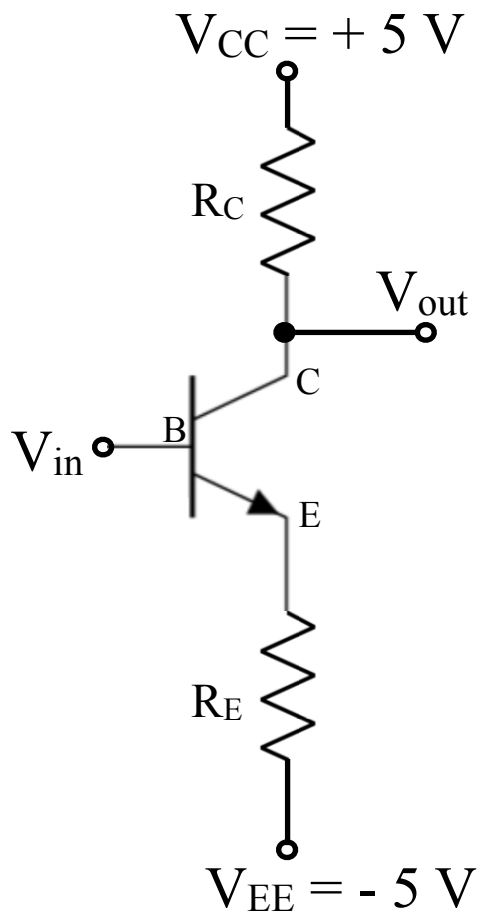
# Common-emitter amplifier

We can use the current amplification of the transistor to get voltage amplification.




$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E) \quad \& \quad \Delta V_{out} = -\Delta V_{in}(R_C/R_E)$$

The AC response matters for the signal amplification, but the DC offset matters for clipping.

Transistor requires:  $V_{out} < V_{CC}$  and  $V_{out} > V_E + 0.2$

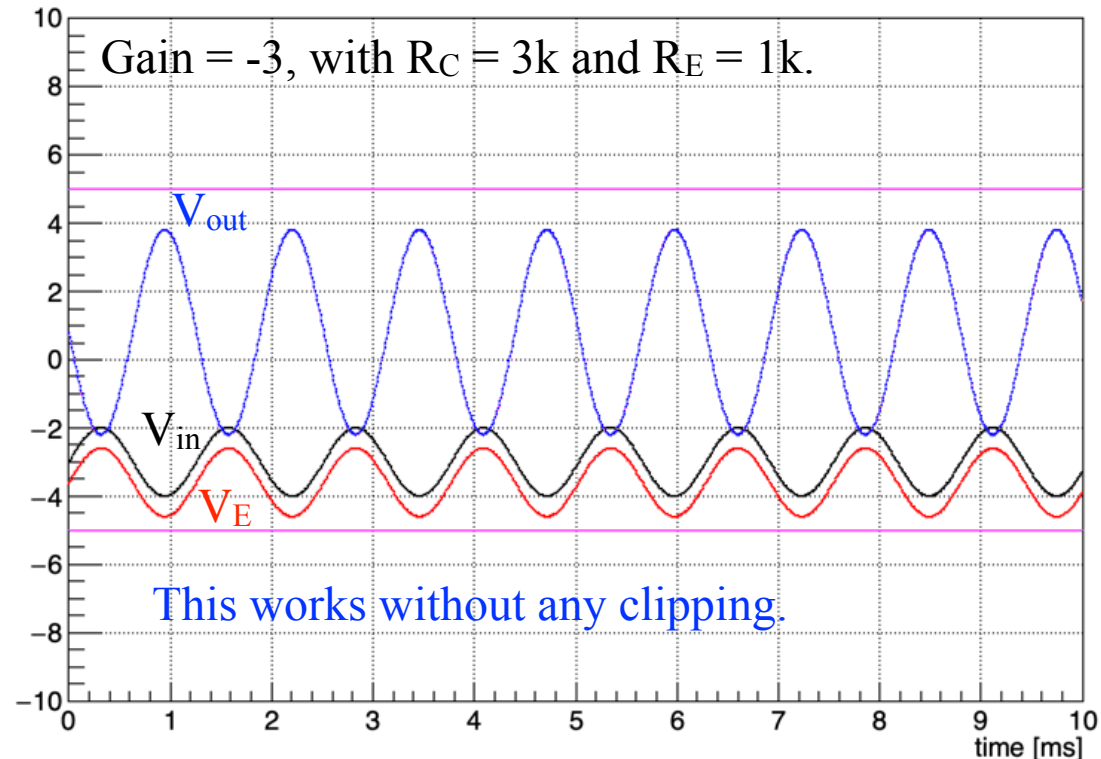Can't have  $V_{in}$  and  $V_{out}$  both oscillating around zero.



# Common-emitter amplifier



We can use the current amplification of the transistor to get voltage amplification.

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E) \quad \& \quad \Delta V_{out} = -\Delta V_{in}(R_C/R_E)$$

The AC response matters for the signal amplification, but the DC offset matters for clipping.


Transistor requires:  $V_{out} < V_{CC}$  and  $V_{out} > V_E + 0.2$

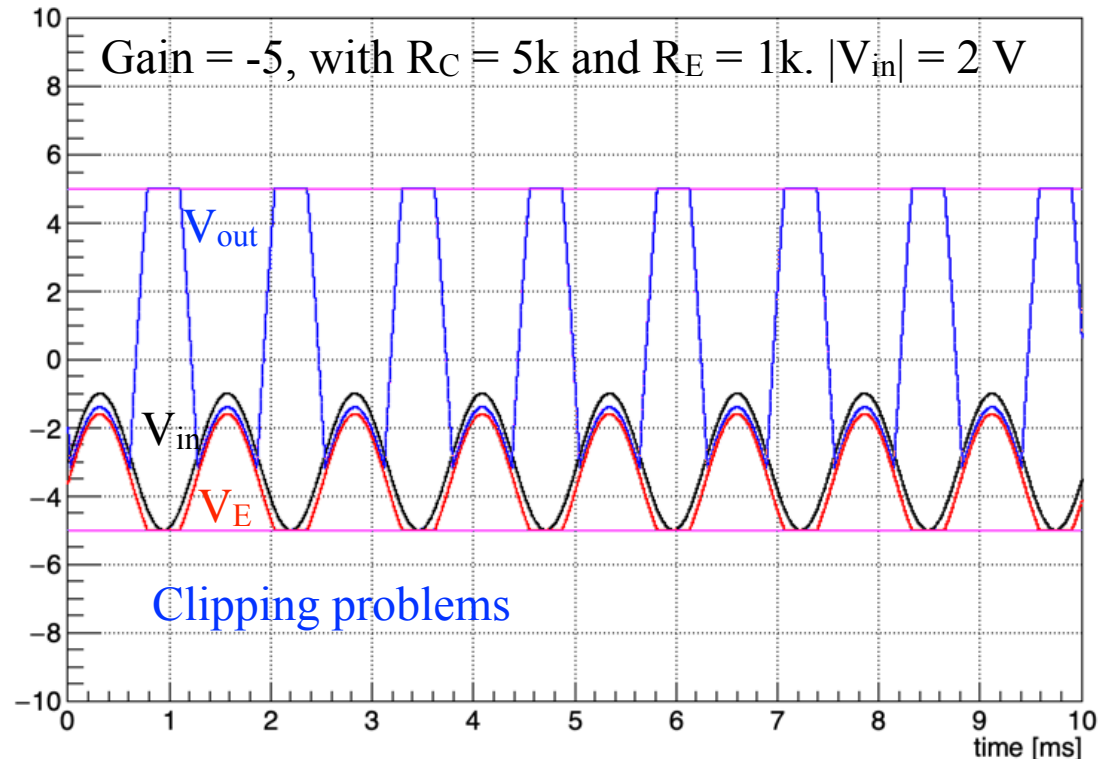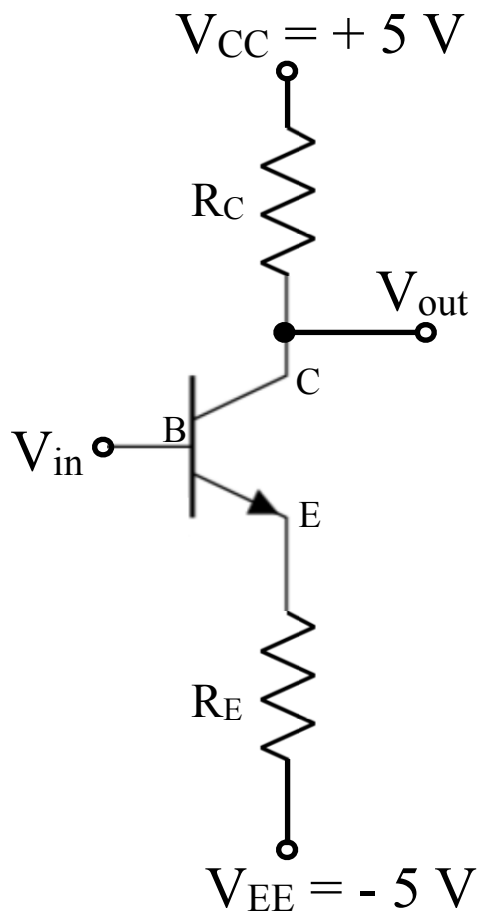Can't have  $V_{in}$  and  $V_{out}$  both oscillating around zero.


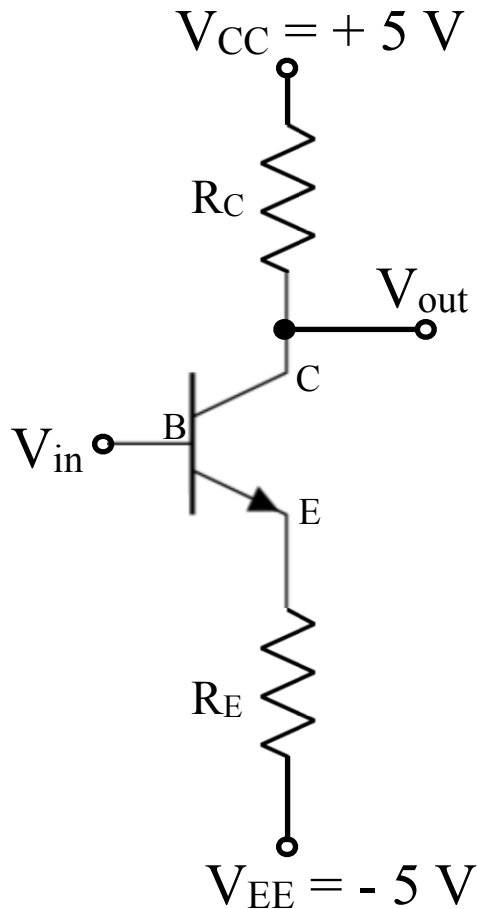
# Common-emitter amplifier input biasing


We want an amplifier stage that doesn't need the previous stage to carefully adjust the offset voltage to avoid clipping. So build it in.



Apply an “input bias” that puts the emitter close to  $V_{EE}$ , within a  $\Delta V$  that defines the max input swing.
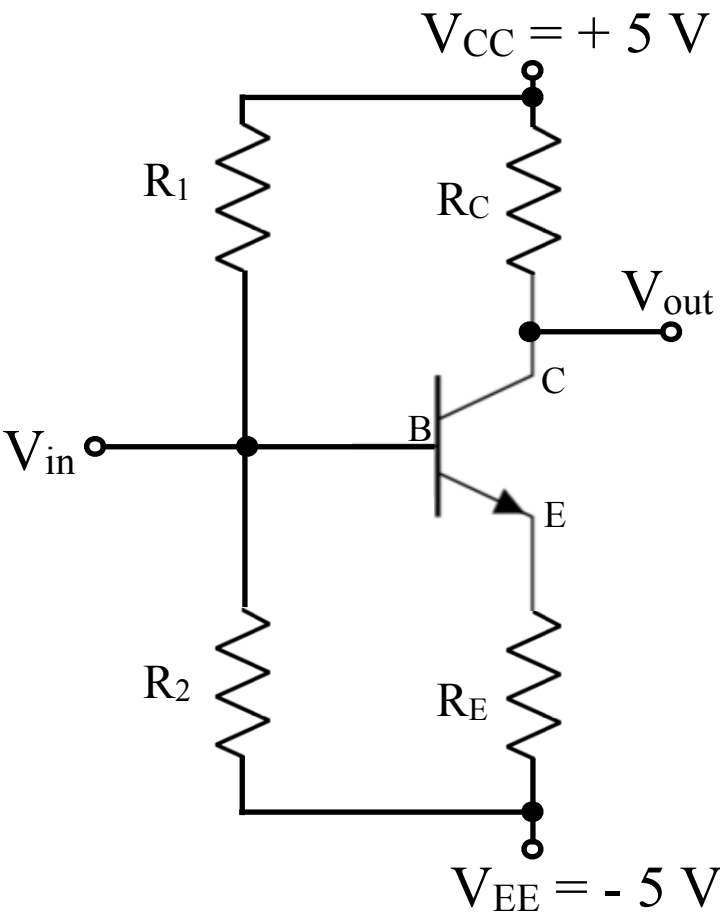
# Common-emitter amplifier input biasing

Apply an input bias that puts the emitter close to  $V_{EE}$ , within a  $\Delta V$  that defines the max input swing.



Suppose I want a max input swing of  $\pm 0.1\text{ V}$   
Set  $V_E$  to vary from  $-4.8$  to  $-5.0$ , i.e.,

DC set point for  $V_E$  is  $-4.9\text{ V}$ .

DC set point for  $V_{in}$  is  $-4.3\text{ V}$ .

These are called the *quiescent* values, meaning “when quiet, ie without signal”.

Choose  $R_1$  and  $R_2$  to be a voltage divider setting  $V_{in}$  at  $-4.3\text{ V}$ .

$$V_{in} = V_{EE} + (V_{CC} - V_{EE}) * R_2 / (R_1 + R_2)$$

$$-4.3 = -5 + 10 * 1k / (1k + R_2)$$

$$R_1 = 13k \text{ and } R_2 = 1k$$


Or I could use

$$R_1 = 130k \text{ and } R_2 = 10k$$

Which choice is better?
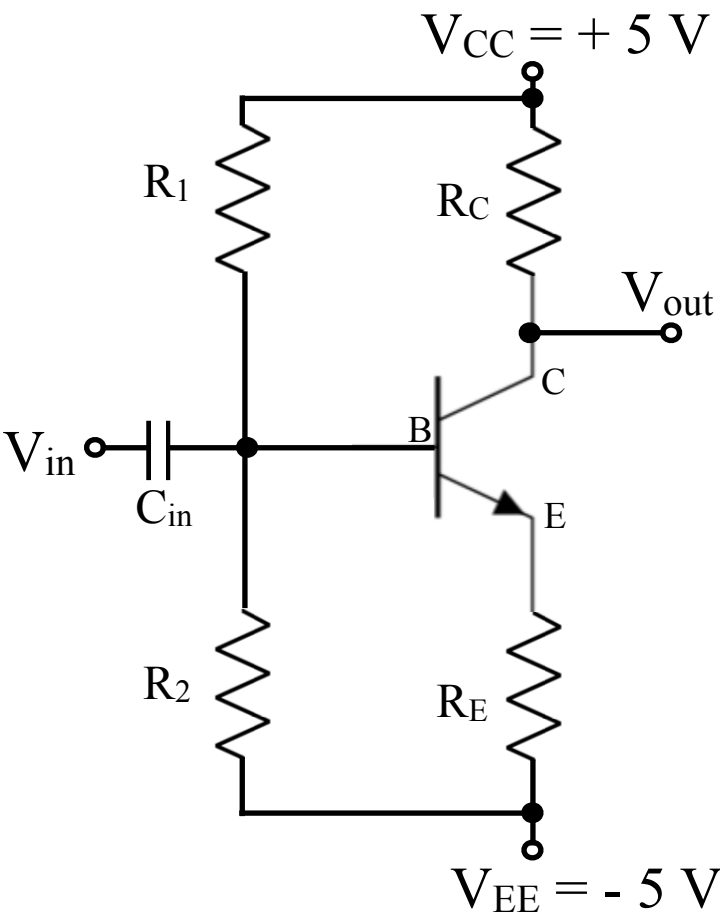
# Common-emitter amplifier input biasing

Apply an input bias that puts the emitter close to  $V_{EE}$ , within a  $\Delta V$  that defines the max input swing.




Suppose I want a max input swing of  $\pm 0.1\text{ V}$   
Set quiescent points:  $V_E = -4.9\text{ V}$  &  $V_{in} = -4.3\text{ V}$   
 $R_1 = 130\text{ k}$  and  $R_2 = 10\text{ k}$

But now this stage yanks the output of the previous stage to a different voltage.  
Fix that by *decoupling* the input from this “DC bias voltage” with a “decoupling capacitor”.

$R_{in}C_{in}$  make a high-pass filter letting the signal through and blocking the DC offsets.  
What is  $R_{in}$ ?
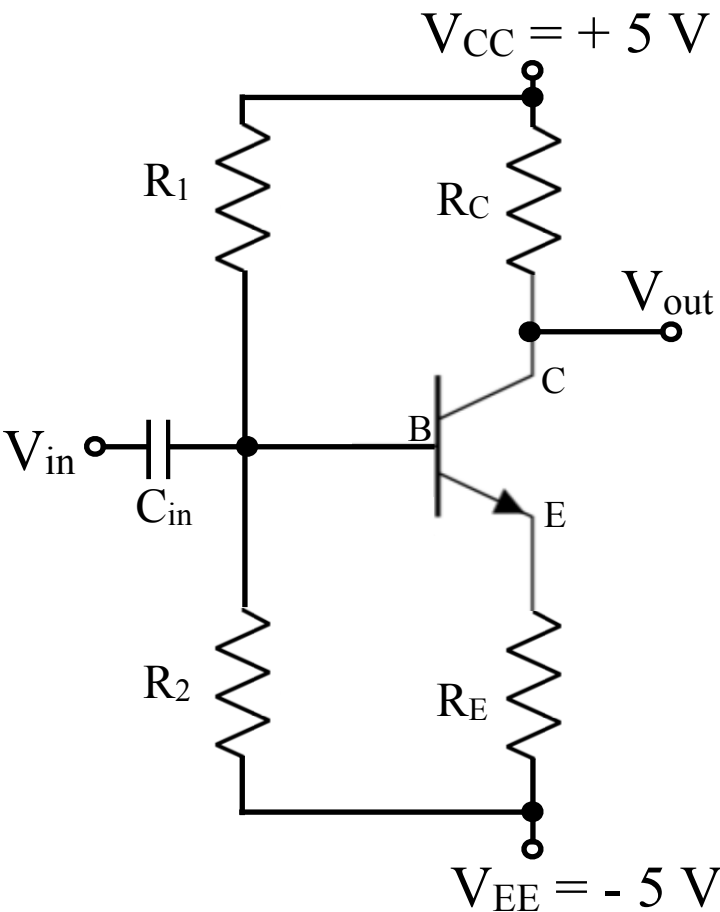
# Common-emitter amplifier input biasing

Apply an input bias that puts the emitter close to  $V_{EE}$ , within a  $\Delta V$  that defines the max input swing.



Input impedance is all paths from input to a fixed voltage ( $V_{CC}$ ,  $V_{EE}$ , or Gnd).

$$R_{in} = R_1 \parallel R_2 \parallel \beta R_E \cong 130\text{k} \parallel 10\text{k} \parallel \beta R_E \cong R_2.$$

High-pass filter should have  $f_{3\text{dB}} < \text{signal frequency range}$ .

For audio signals, that is 20 Hz, so


$$20 = 1/2\pi(10\text{k})C$$

$$C \cong 1/6 * 120 * 10\text{k} \cong 1/1\text{k} * 10\text{k} = 0.1 \mu\text{F}$$



# Common-emitter amplifier input biasing

Now we need to pick  $R_E$  and  $R_C$

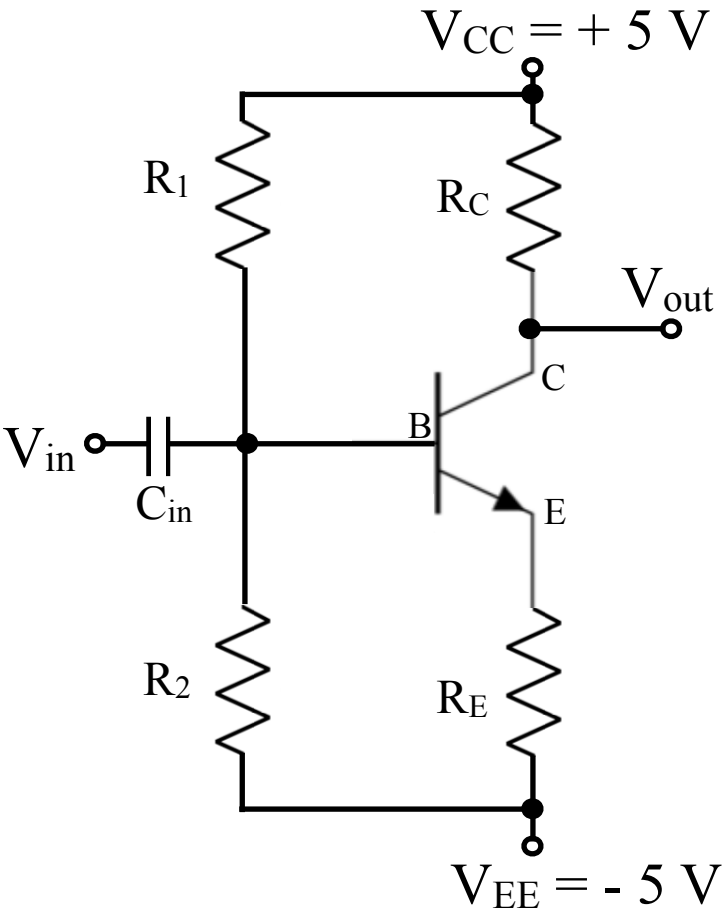

The ratio of  $R_E$  and  $R_C$  is set by the desired gain, and avoiding output clipping.

Choose gain = 10.

That means  $V_{out}$  swings by  $\pm 1\text{ V}$ .

Then quiescent point for  $V_{out}$  to be at least  $1\text{ V}$  away from  $V_{CC}$  and  $V_E$ .

But,

$$V_{out} = V_{CC} - V_E(R_C/R_E) + V_{EE}(R_C/R_E)$$



only depends on the gain ratio.

$$\begin{aligned} V_{out} &= 5 - (-4.9 \cdot 10) - 5 \cdot 10 \\ &= 4 \end{aligned}$$

That works, but just barely.

# Common-emitter amplifier input biasing

Now we need to pick  $R_E$  and  $R_C$

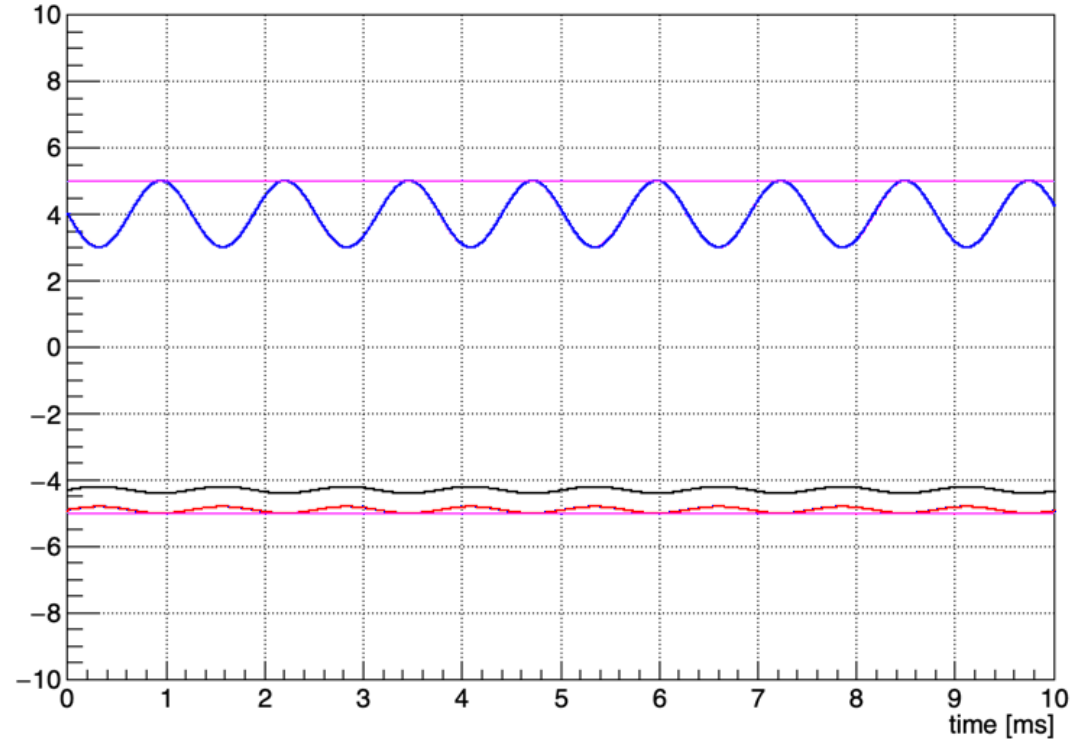
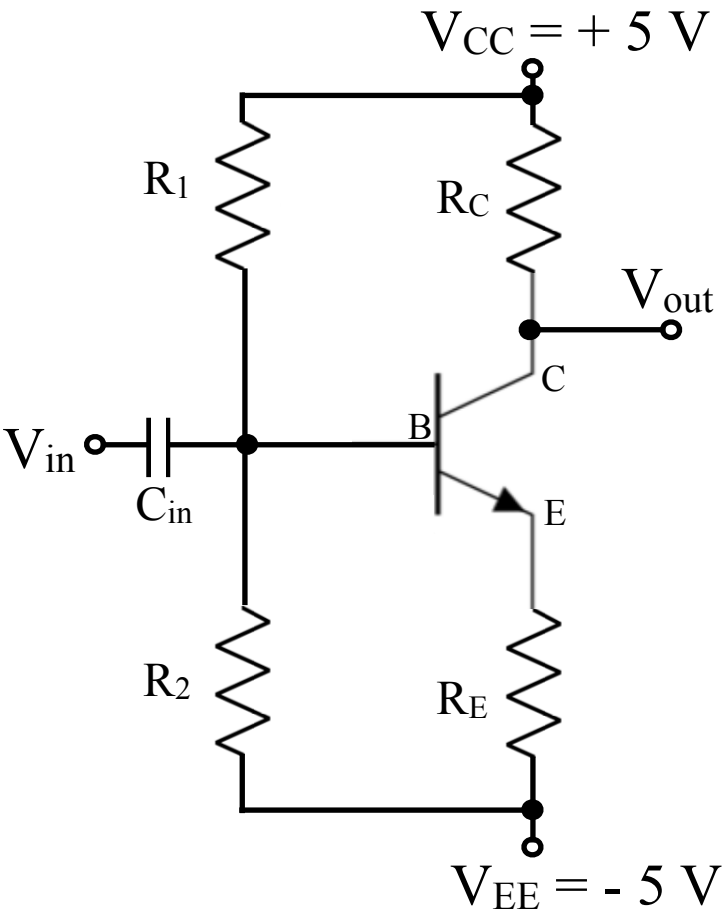


$$\begin{aligned} V_{out} &= 5 - (-4.9 \cdot 10) - 5 \cdot 10 \\ &= 4 \end{aligned}$$

That works, but just barely.

# Common-emitter amplifier input biasing


Now we need to pick  $R_E$  and  $R_C$

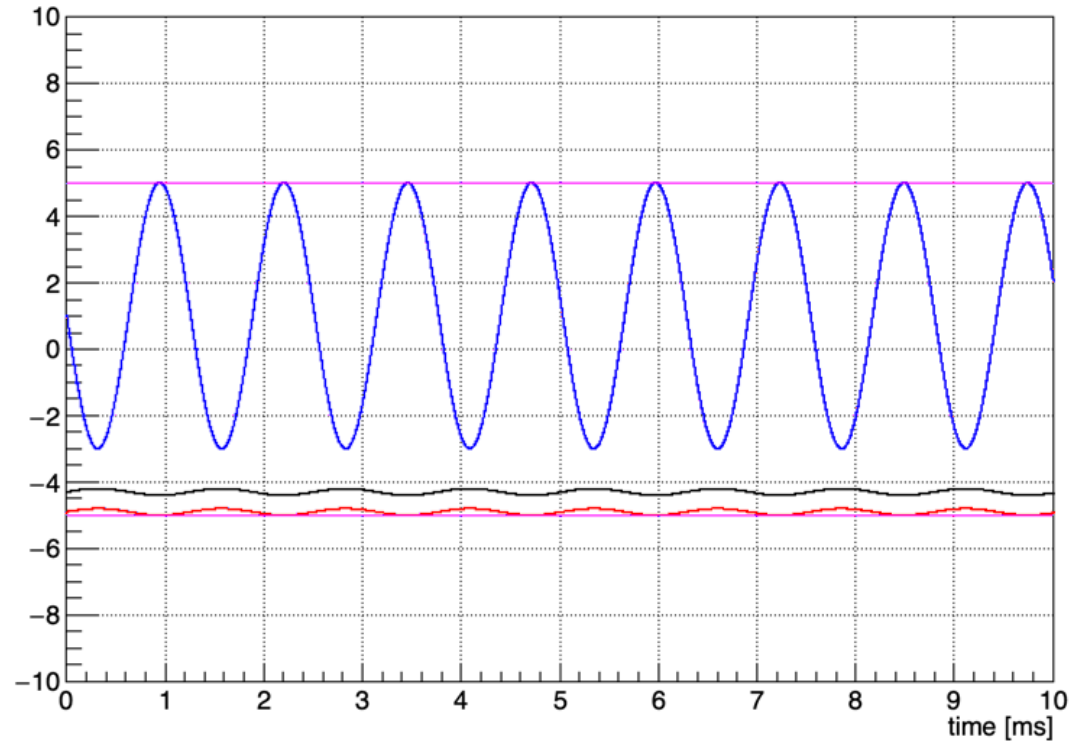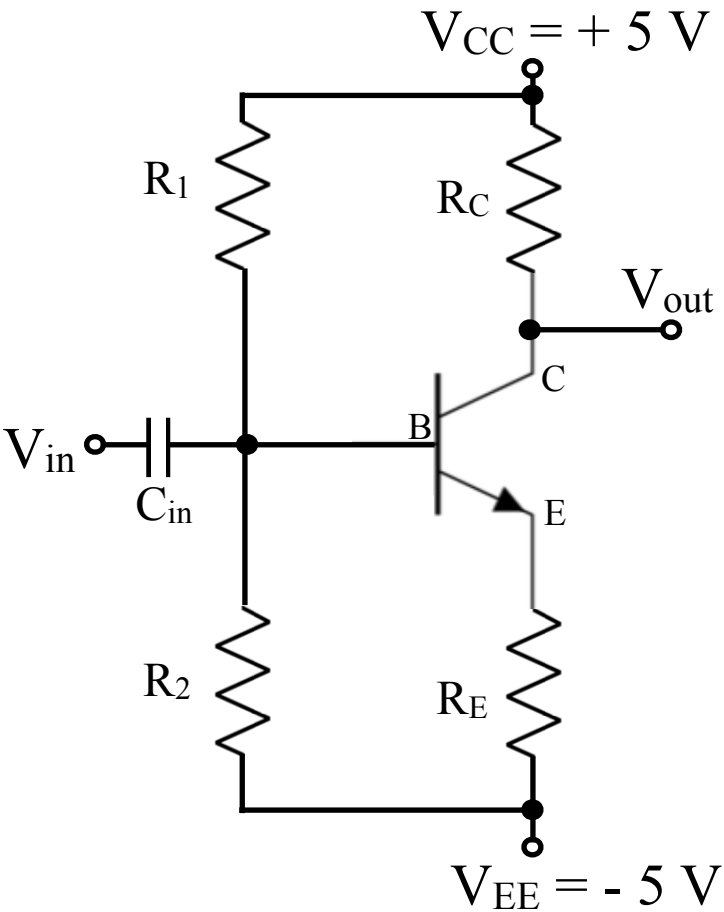

Gain of 40 also works, with  $v_{out}$  DC at 1 V.
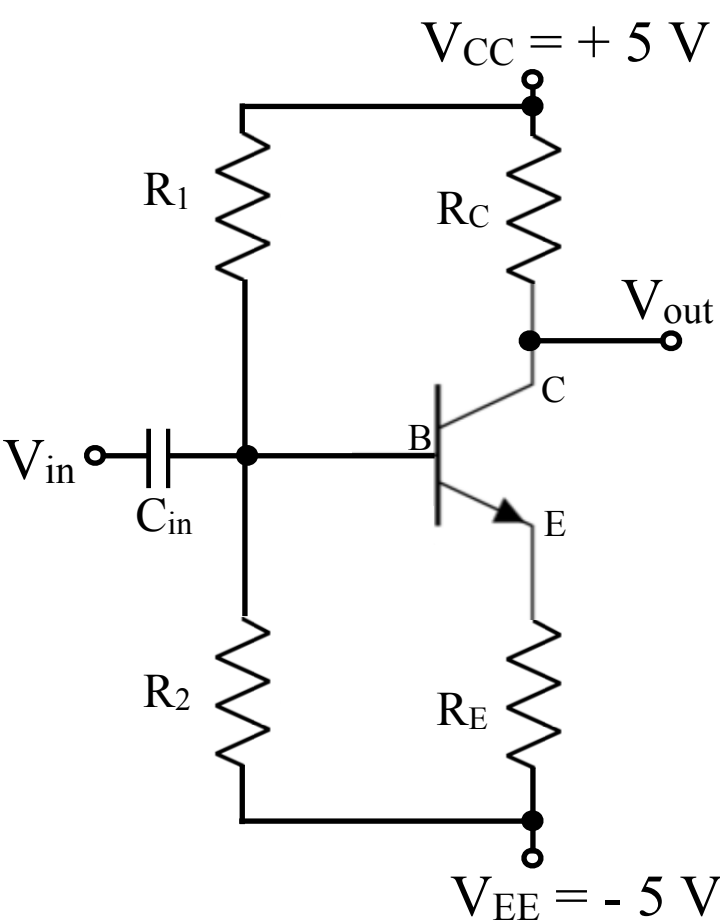
# Common-emitter amplifier input biasing


The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .



We want a large  $R_E$  for setting quiescent voltages and a small  $R_E$  for setting gain.
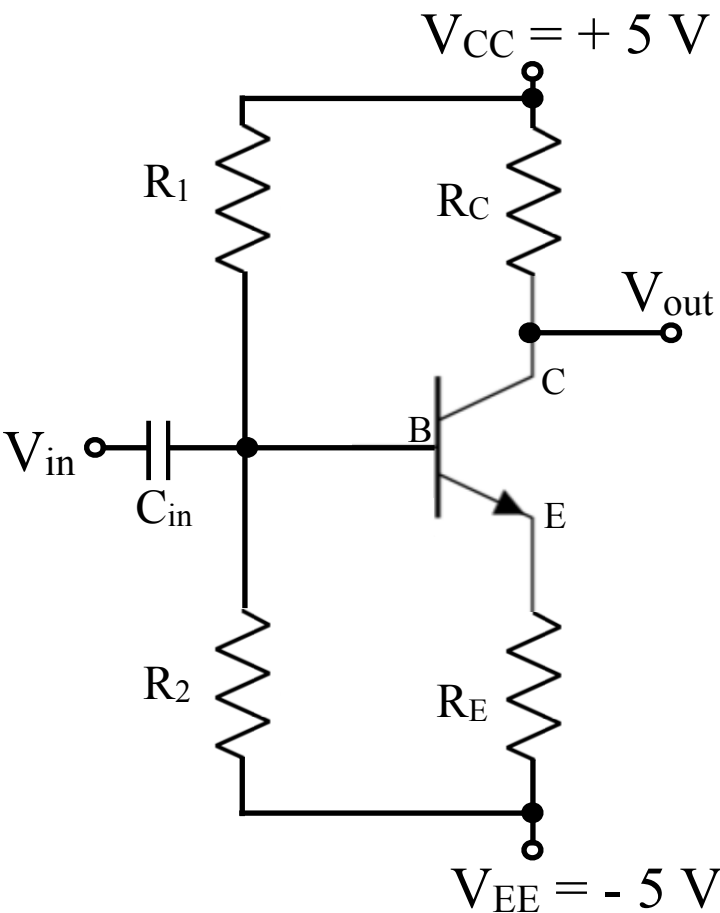
# Common-emitter amplifier input biasing


The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




We want a large  $R_E$  for setting DC quiescent voltages and a small  $R_E$  for setting AC gain.
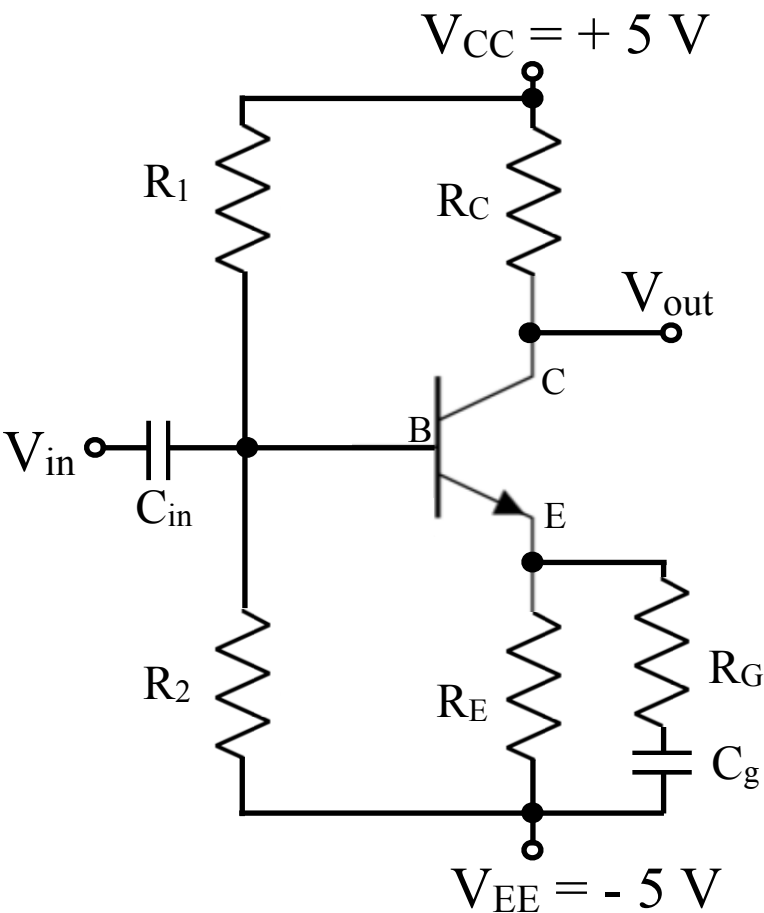
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




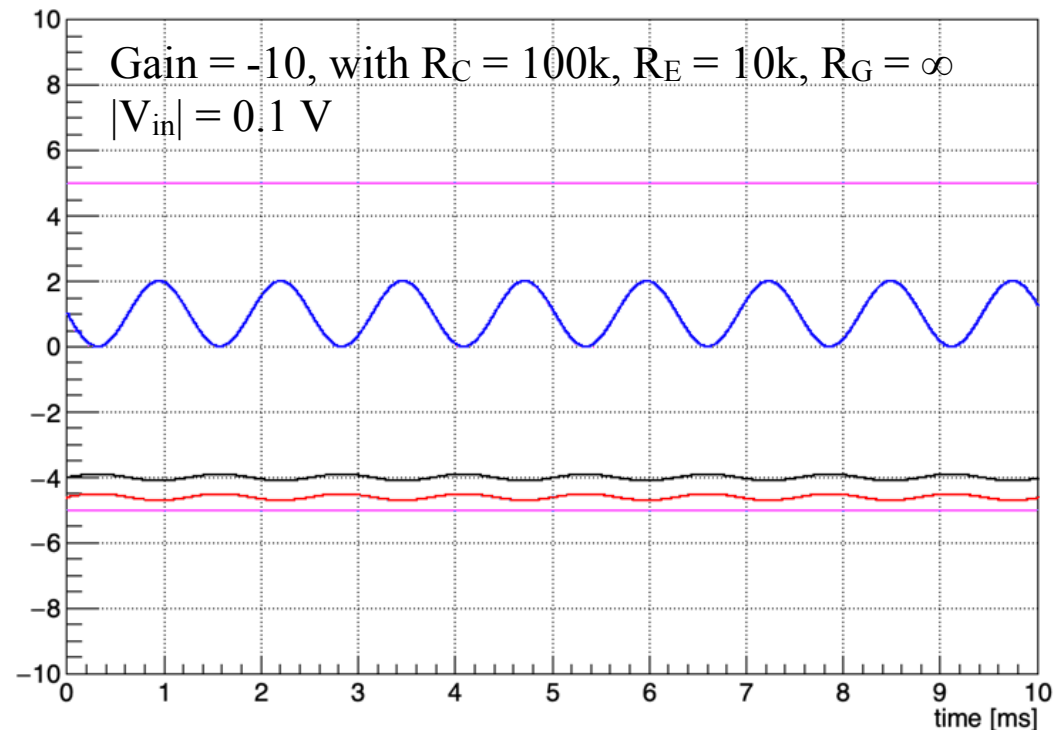Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.



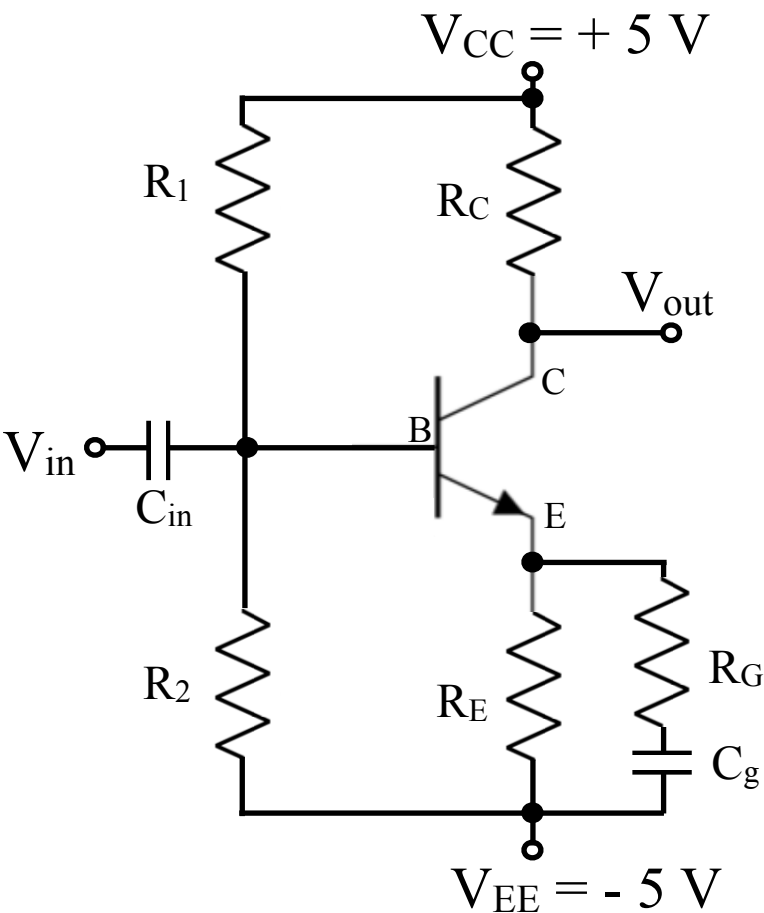
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




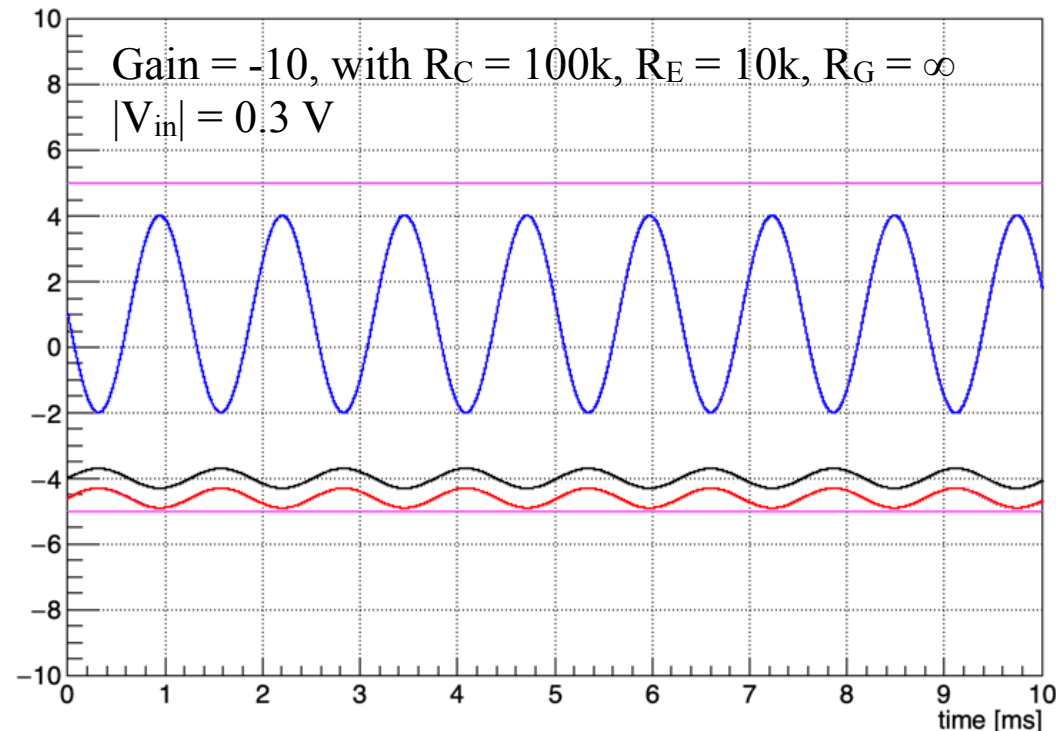Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.



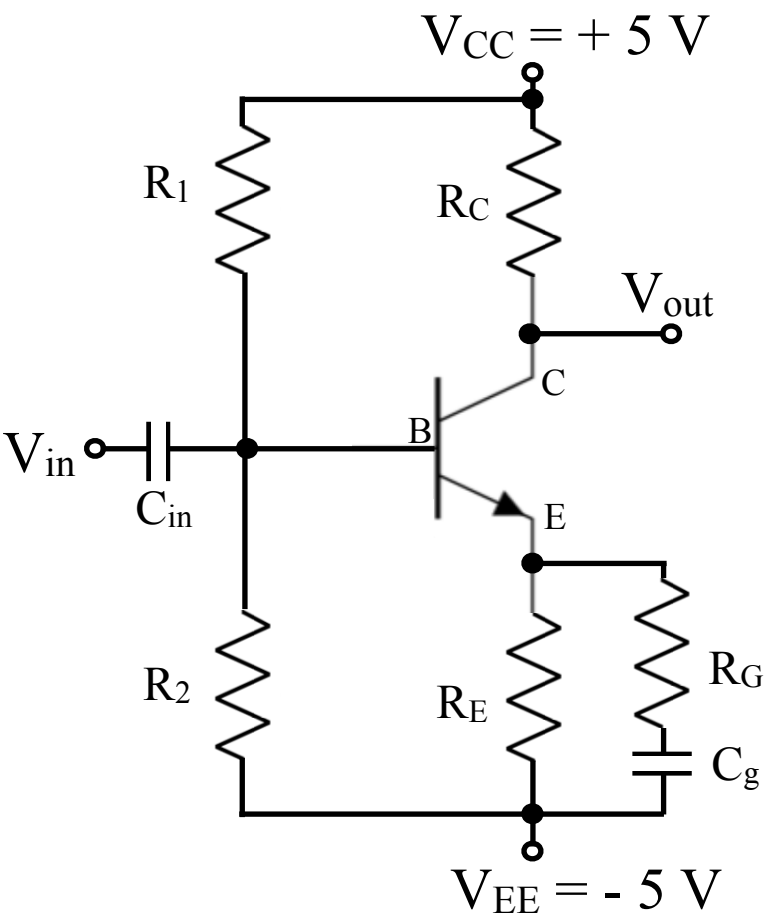
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .



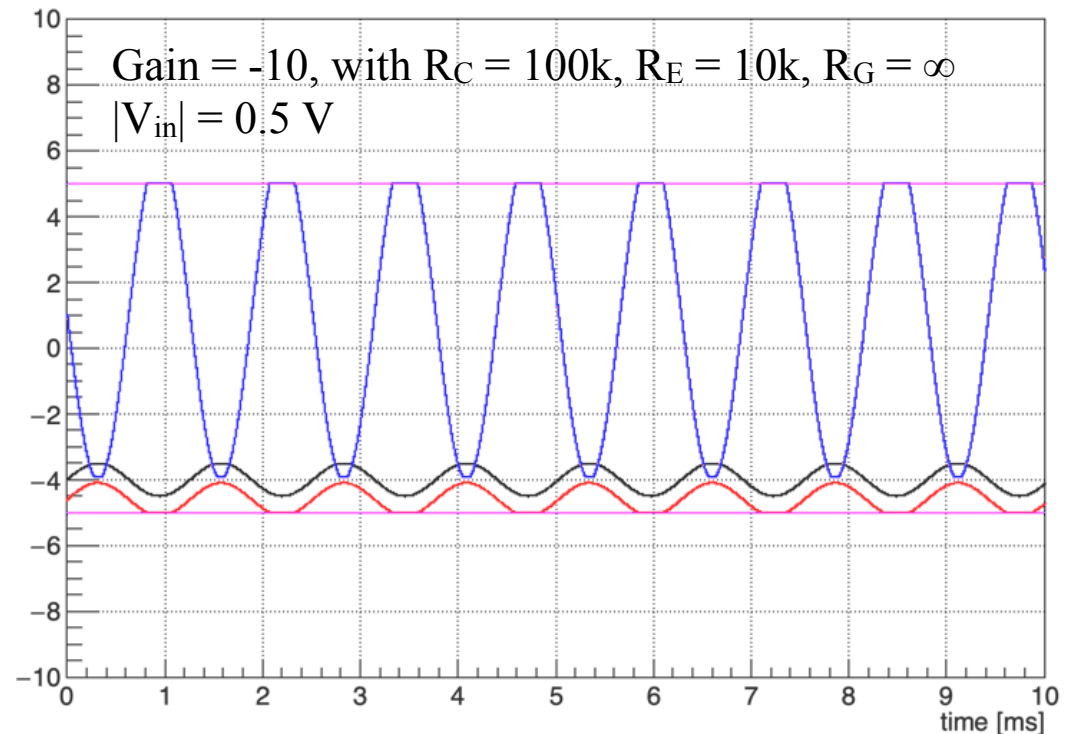
Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.





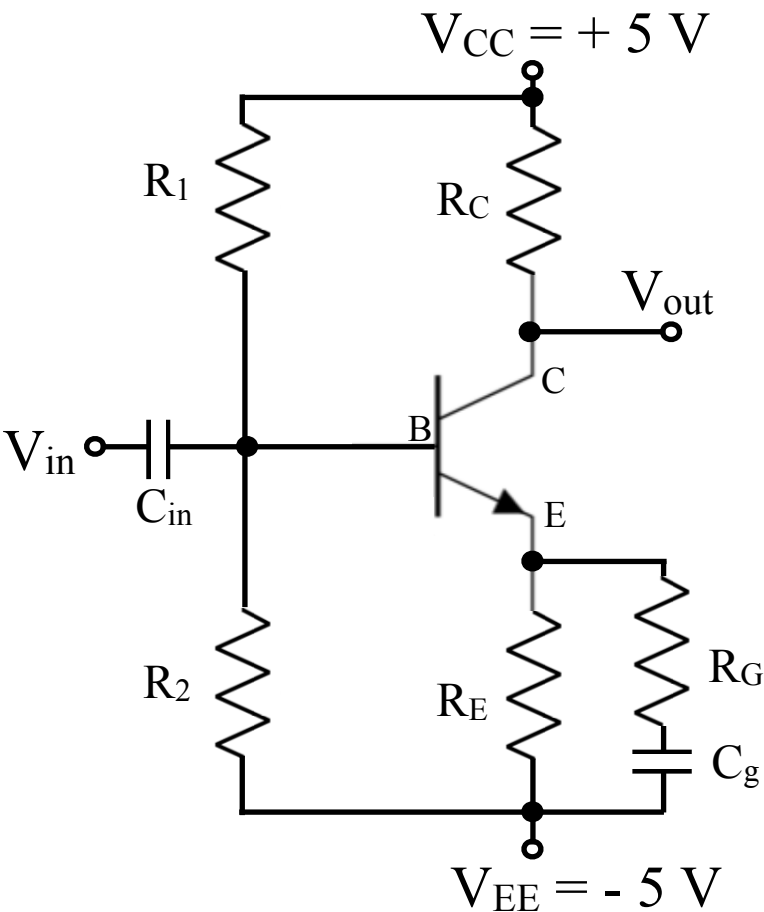
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




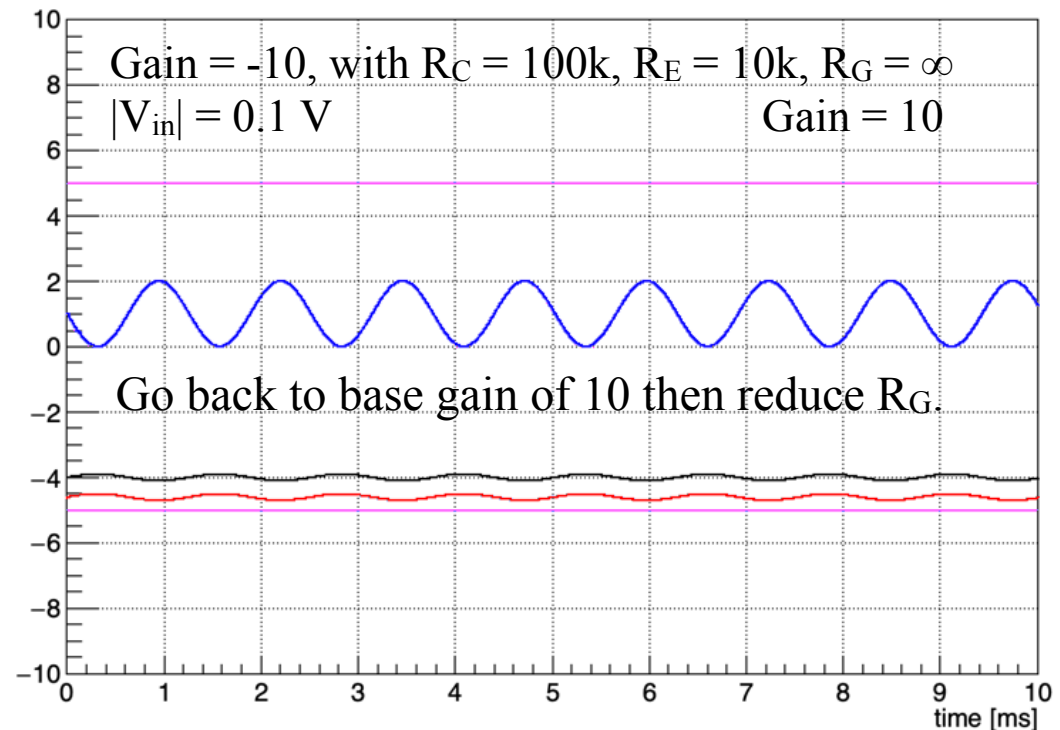Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.



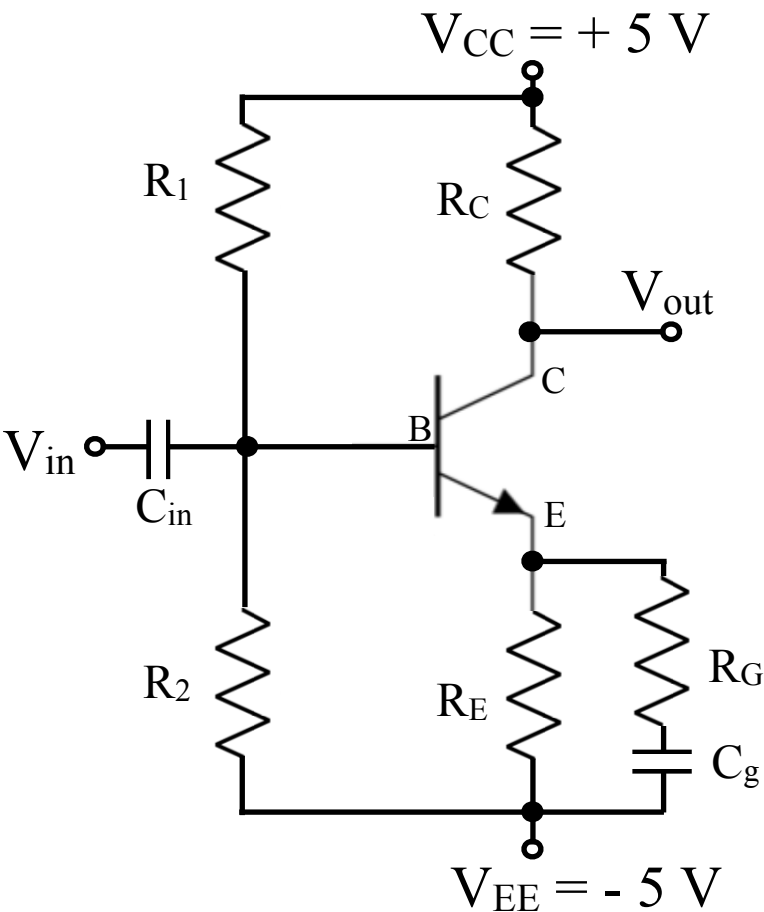
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




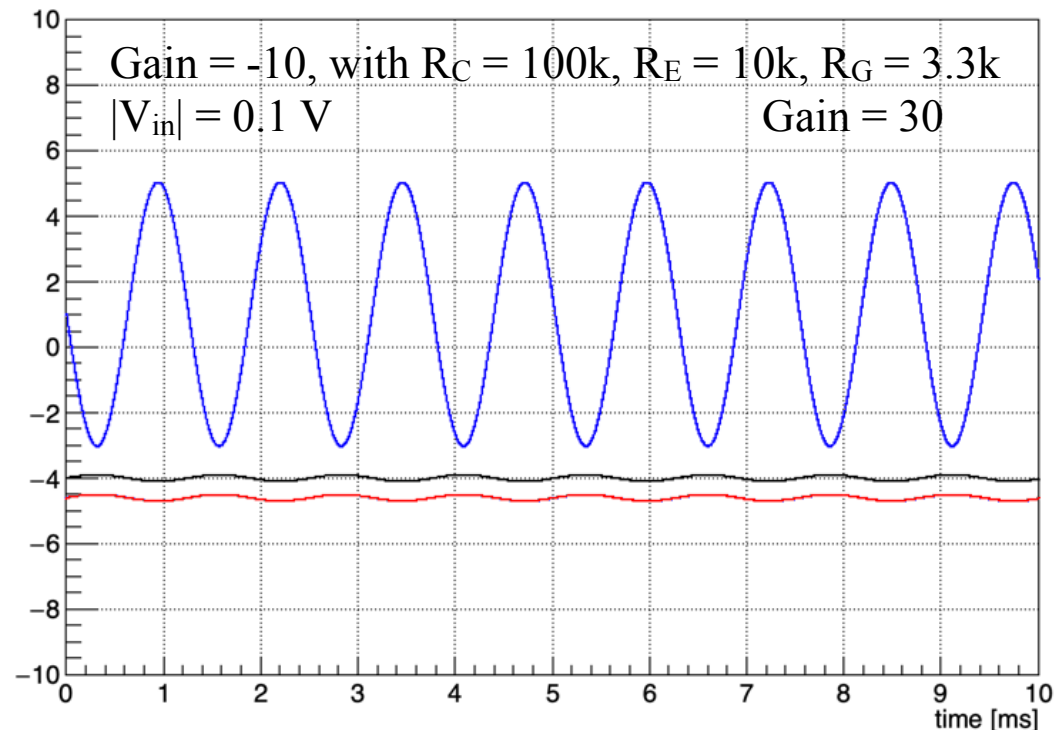Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.



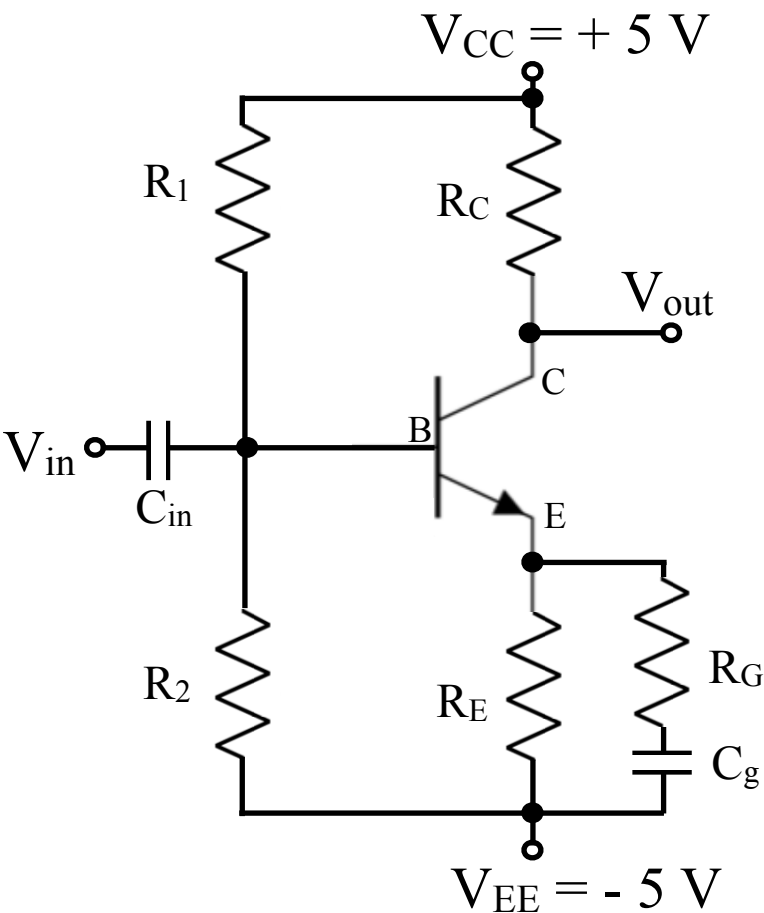
# Common-emitter amplifier input biasing

The challenge here is that  $R_E$  affects both the gain and the quiescent  $V_{out}$ . A small  $R_E$  gives big gain but large  $I_E$  which affects quiescent  $V_{out}$ .




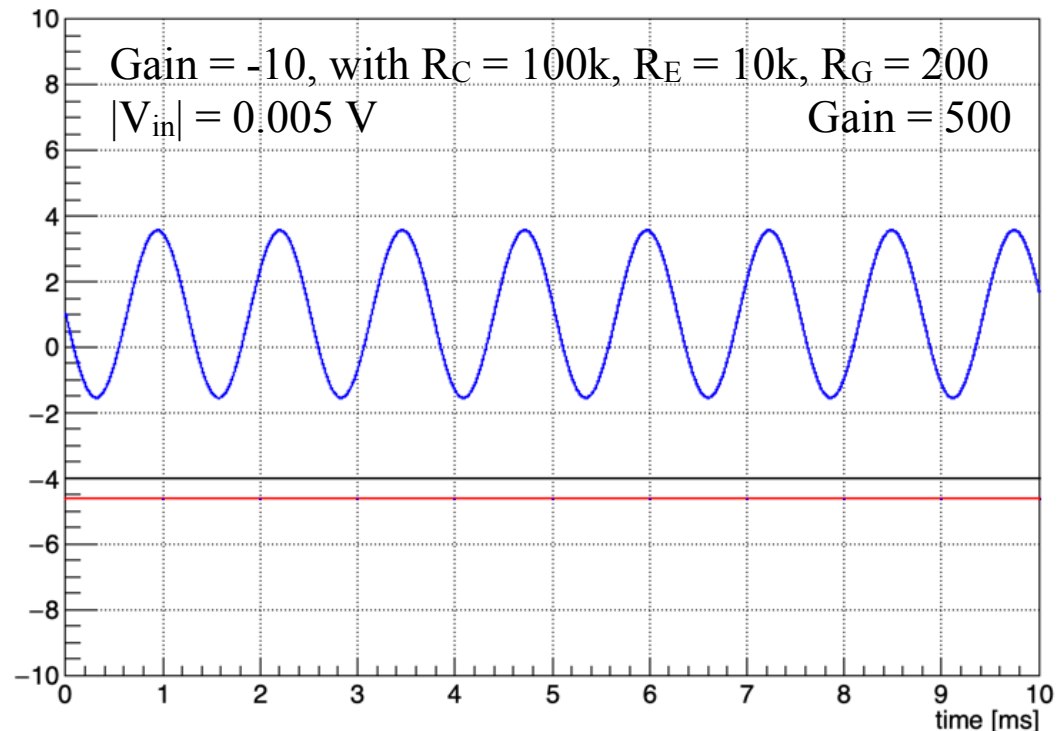Choose  $R_1$  and  $R_2$  for quiescent  $V_E = -4\text{ V}$ .  
Choose  $R_E = 10\text{ k}$  and  $R_C = 100\text{ k}$  for quiescent  $V_{out} = 1\text{ V}$  and base gain of 10.



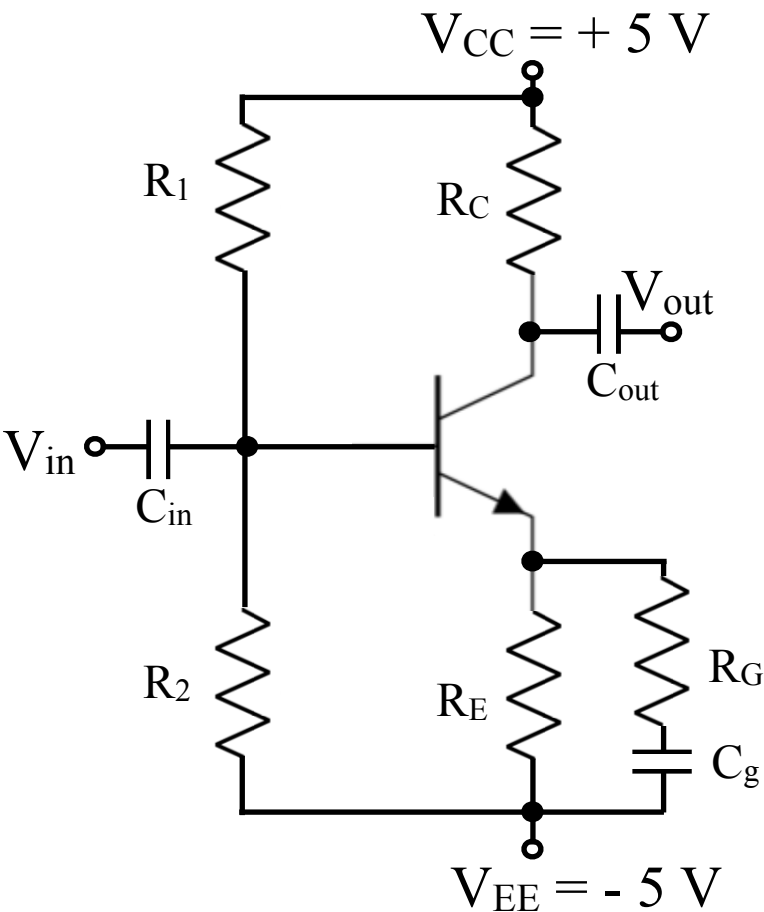
# Common-emitter amplifier input biasing

Finally, what can we do about the 1 V quiescent offset on  $V_{out}$ ?





Remove it with a decoupling capacitor.

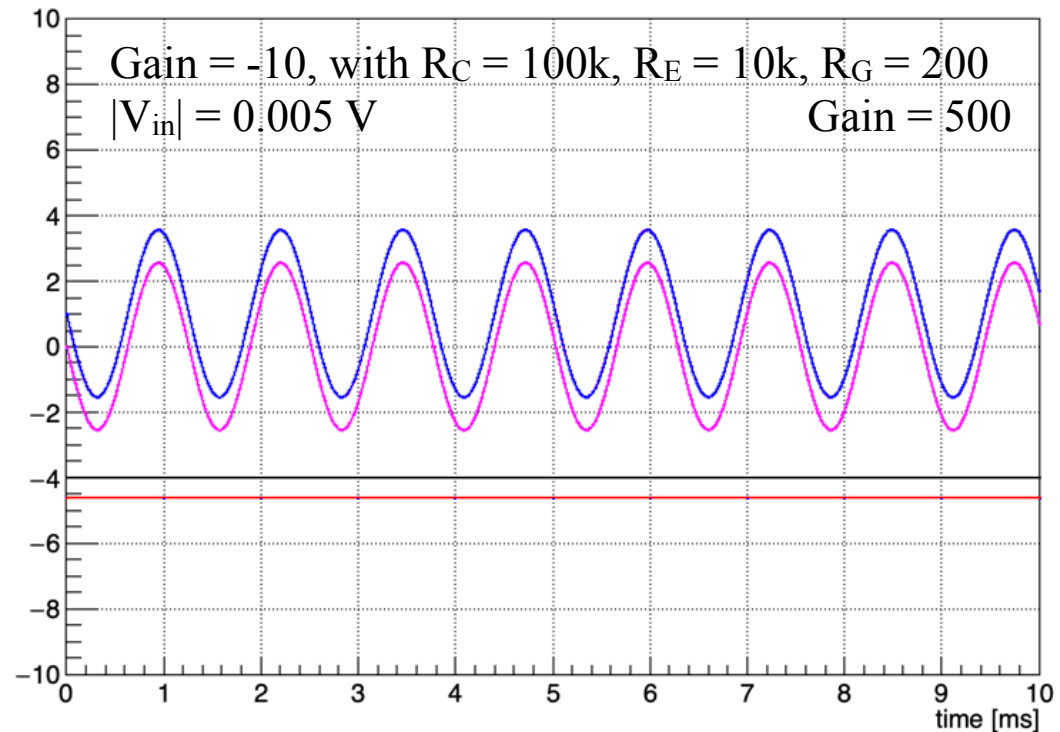

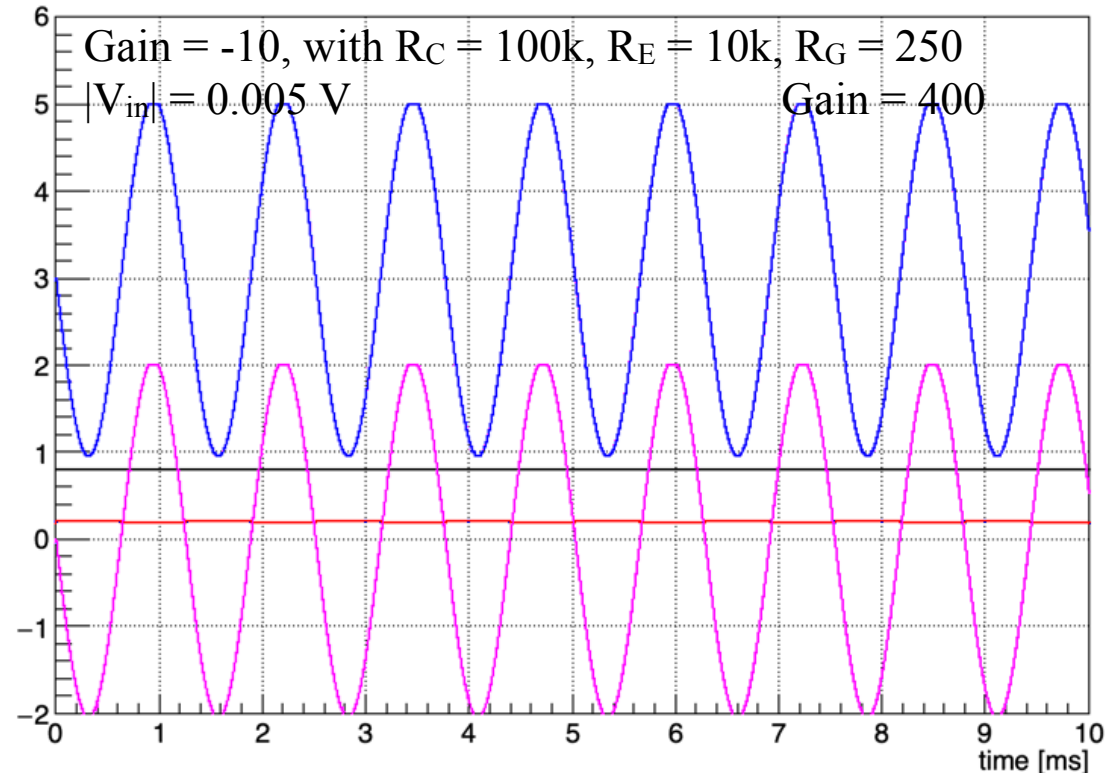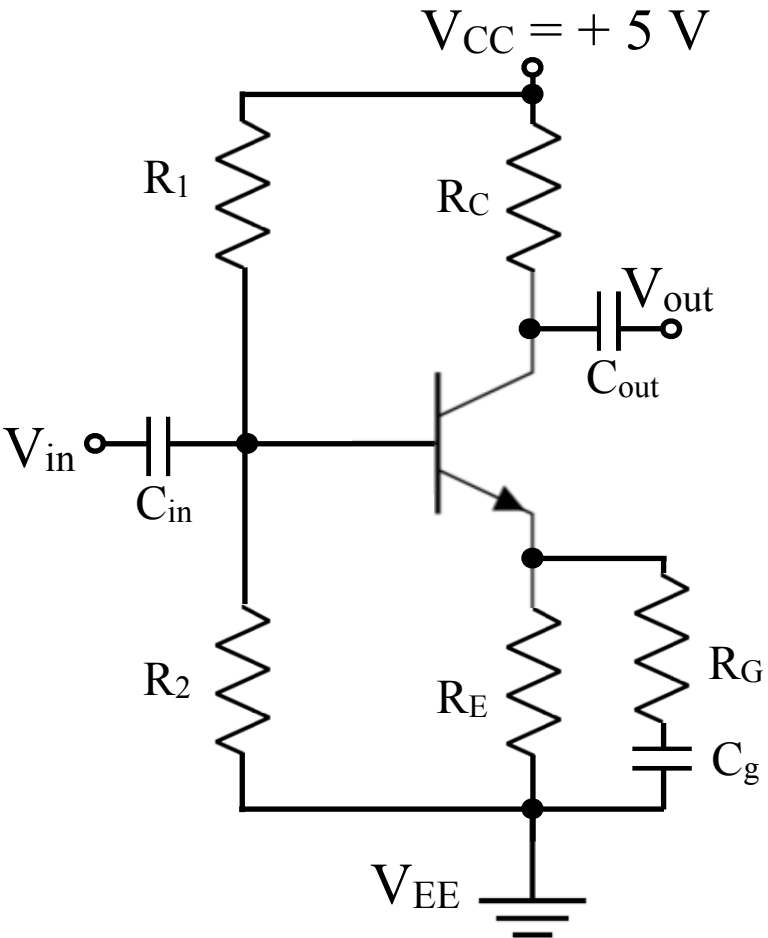
# Common-emitter amplifier input biasing

This all works if  $V_{EE}$  is ground. We just have to choose quiescent points. In fact with  $V_{EE}=\text{Gnd}$ , we *must* have input biasing.



# Common-emitter amplifier input biasing

Some checks of understanding.

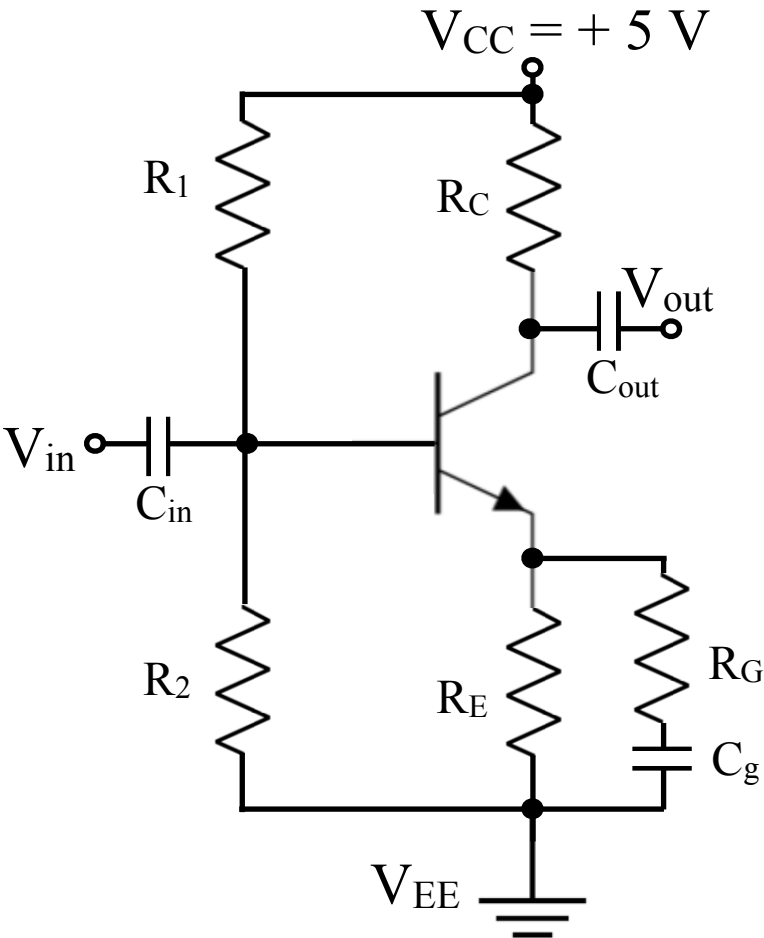

Without DC biasing, what would limit the signal?

What is the output impedance of this circuit?

What would happen if you set  $R_G = 0$ ?

With  $V_{EE} = \text{Gnd}$ , about where should you put the quiescent  $V_{out}$ ? Where is the quiescent  $V_{in}$ ?

In general, how do you maximize the *dynamic range*?

# Common-emitter amplifier operation

The transistor is changing the voltage dropped across it to satisfy the rules of operation.

Increase in  $V_{in}$  causes increase in  $V_E$   
That causes an increase in  $I_E$   
That causes a decrease in  $V_C$   
The voltage across the transistor,  $V_{CE}$ , goes down to compensate.

