
 


PHYS127AL Lecture 9

David Stuart, UC Santa Barbara



Field effect transistors (FETs)

 

PHYS127AL Lecture 9

David Stuart, UC Santa Barbara

Field effect transistors (FETs)

  

How many of you have heard of "CMOS" before?

Review: More complete transistor model

We used simplified (0th and 1st order) models:

1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off

I.e., $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on, $\Delta V_B = \Delta V_E$.

$$I_C = I_S \left(e^{V_{BE}/nV_T} - 1 \right)$$

2). $I_C = \beta I_B$.

And by charge conservation

$I_E = I_B + I_C$ so $I_E \cong I_C$

3). $V_{CE} > 0.2 \text{ V}$


A 2nd order correction incorporates effects from collector voltage differences

$$I_C = I_S \left(e^{V_{BE}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AF}} \right) - I_S \left(e^{V_{BC}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AR}} \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right)$$

$$I_B = \frac{I_S}{\beta_F} \left(e^{V_{BE}/nV_T} - 1 \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right).$$

(Ebers–Moll equations with Early correction)

Review: Differential amplifier

 

Get positive gain by selecting output from $v_2 = -v/2$

Don't need output from other side, but we do need the other side to get the common mode suppression.

To maximize the $CMRR = G_{Diff}/G_{CM}$ make R_{EE} large.


A current source has infinite impedance.

Common mode gain = $-R_C/(R_E+2R_{EE})$

Differential gain = $R_C/2R_E$

Field effect transistors (FETs)

 
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_G increases the depletion.

$$I = n A q v$$

 
So changing the gate voltage controls nA and I . Like pinching off a hose. "Depletion mode"



Changing V_{GS} will vary the depletion region and change the current.

Field effect transistors (FETs)

 
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_G increases the depletion.

$$I = n A q v$$

 
So changing the gate voltage controls nA and I . Like pinching off a hose. "Depletion mode"



A reduced voltage on the gate increases the depletion region and reduces the current.

Field effect transistors (FETs)


 
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_G increases the depletion.

$$I = n A q v$$

 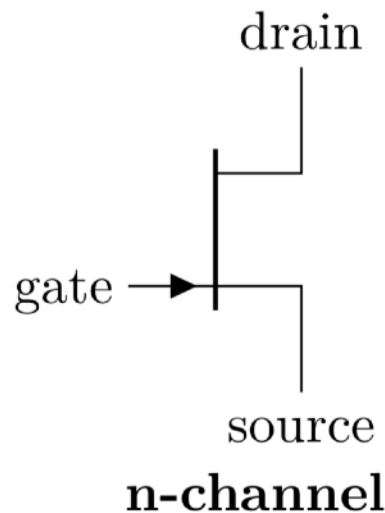
So changing the gate voltage controls nA and I . Like pinching off a hose. "Depletion mode"



A reduced voltage on the gate increases the depletion region and reduces the current.

Field effect transistors (FETs)


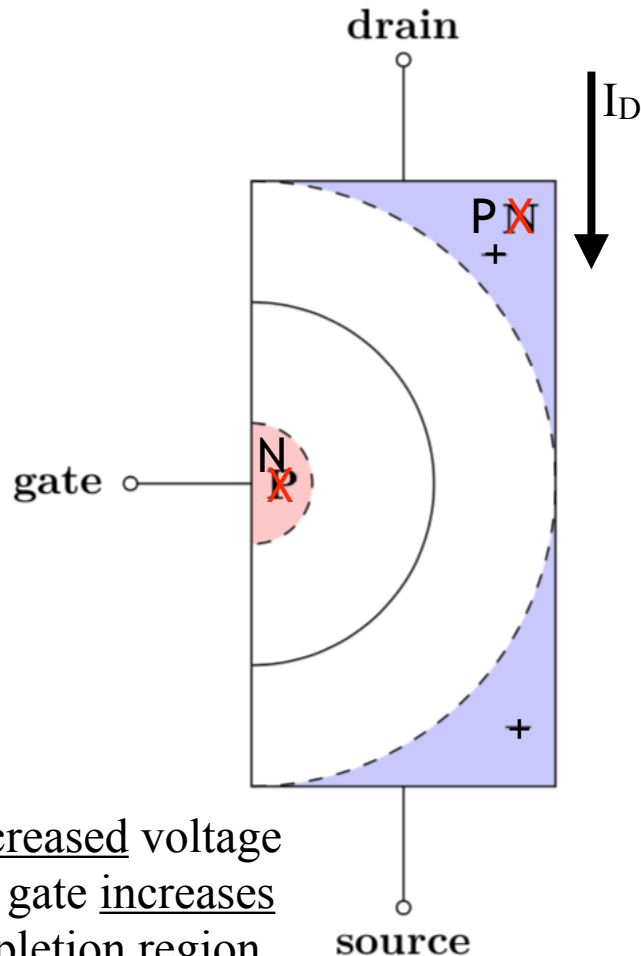
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_G increases the depletion.

$$I = n A q v$$

  So changing the gate voltage controls nA and I . Like pinching off a hose. "Depletion mode"






An increased voltage on the gate increases the depletion region and reduces the current.

Field effect transistors (JFETs)

The current is controlled by V_{GS} .

   If $V_{GS} = 0$ current flows, saturating at I_{DSS} based on doping.
If $V_{GS} > 0$ a bit more current flows.



Field effect transistors (JFETs)

The current is controlled by V_{GS} .




If $V_{GS} = 0$ current flows, saturating at I_{DSS} based on doping.

If $V_{GS} > 0$ a bit more current flows.

If $V_{GS} < 0$ less current flows.



If $V_{GS} < V_{\theta}$ then $I_D = 0$. V_{θ} is typically a couple volts.

   So a voltage (E field) controls a current, like the Ebers-Moll view, but depleting the current.




Field effect transistors (JFETs)

 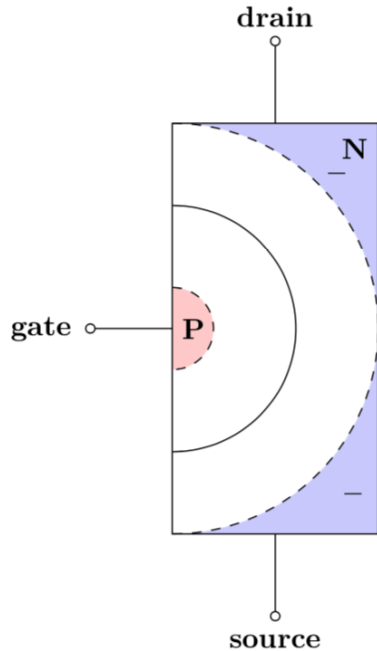In the linear region, it behaves like a voltage-controlled resistor:



$$I_D = 2k \left[(V_{GS} - V_{\Theta})V_{DS} - \frac{V_{DS}^2}{2} \right]$$


 
$$R \cong \frac{1}{2k(V_{GS} - V_{\Theta})}$$



Field effect transistors (JFETs)

In saturation region, behaves like a voltage-controlled current source:



$$I_D = k(V_{GS} - V_{\Theta})^2$$

 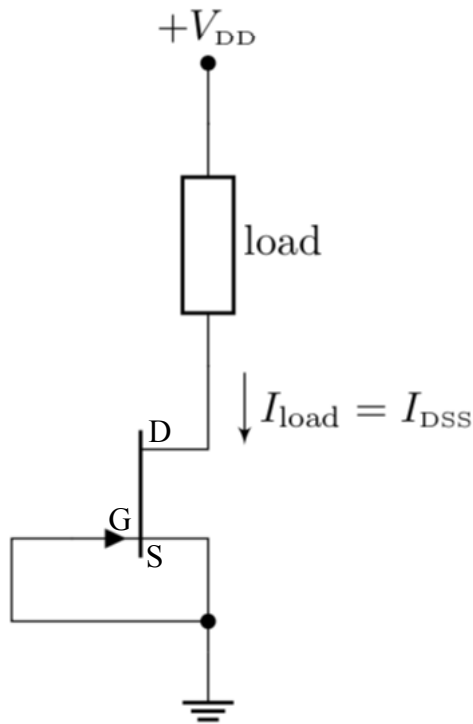

Field effect transistors (JFETs)


In saturation region, behaves like a voltage-controlled current source:

$$I_D = k(V_{GS} - V_{\Theta})^2$$

  

Field effect transistors (JFETs)

 In saturation region, behaves like a voltage-controlled current source:



Now the power supplies are called V_{DD} and V_{SS} instead of V_{CC} and V_{EE}

Field effect transistors (JFETs)

Can build the same transistor circuits: source follower

Change in V_{GS} changes current flow, so there is a transconductance relation:

$$i_D = g_m v_{GS}$$



This is from taking delta's of the linear region current relation

$$I_D = 2k \left[(V_{GS} - V_{\Theta}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

So,


$$v_S = i_{DS} R_S$$

and that is V_{out} .

  

Field effect transistors (JFETs)

 Can build the same transistor circuits: common-source amplifier



Again we have

$$i_D = g_m v_{GS}$$

And the output voltage varies as

$$v_{out} = v_D = -i_D R_D$$



$$v_{out} = -g_m R_D v_{in}$$

So,

$$G = -g_m R_D$$

The transconductance, g_m , is mho and about $1/200\Omega$. So large R_D gives large negative gain.

  Note: no biasing above ground required, just R_G to hold DC at ground.



Field effect transistors (JFETs)

Can build the same transistor circuits: common-source amplifier

Again we have

$$i_D = g_m v_{GS}$$

And the output voltage varies as

$$v_{out} = v_D = -i_D R_D$$




$$v_{out} = -g_m R_D v_{in}$$

So,

$$G = -g_m R_D$$


The transconductance, g_m , is mho and about $1/200\Omega$. So large R_D gives large negative gain.

   Note: no biasing above ground required, just R_G to hold DC at ground.



Field effect transistors (JFETs)

 
Can build the same transistor circuits: differential amplifier



Field effect transistors (MOSFETs)


Another type of FET uses a metal-oxide-semiconductor based capacitor rather than a junction to control the gate. MOSFET

 A thin capacitor is placed over a p-type region between two n-types.



Field effect transistors (MOSFETs)

 
Another type of FET uses a metal-oxide-semiconductor based capacitor rather than a junction to control the gate. MOSFET



A thin capacitor is placed over a p-type region between two n-types. No current flows because of depletion regions. But a positive voltage on the gate (wrt the body) induces negative charge carriers in the p-type region. Called n-channel since n-type carriers move.

Field effect transistors (MOSFETs)

 
Another type of FET uses a metal-oxide-semiconductor based capacitor rather than a junction to control the gate. MOSFET



A thin capacitor is placed over a p-type region between two n-types. No current flows because of depletion regions.

A positive voltage on the gate (wrt the body) induces negative charge carriers to form a conduction channel — an n-channel.

 
This is an “enhancement mode” FET, where no current flows until a voltage (relative to the body) allows it.



Field effect transistors (MOSFETs)


Another type of FET uses a metal-oxide-semiconductor based capacitor rather than a junction to control the gate. MOSFET

 Can instead use an n-type bulk with p-type drain and source implants. Again, no current if gate floating.




Field effect transistors (MOSFETs)

 Another type of FET uses a metal-oxide-semiconductor based capacitor rather than a junction to control the gate. MOSFET



Can instead use an n-type bulk with p-type drain and source implants. Again, no current if gate floating.

 
A negative voltage on the gate (wrt the body) induces positive charge carriers to form a conduction channel — a p-channel.



“Enhancement mode” since current normally off.

Field effect transistors (MOSFETs)


We can also make depletion mode MOSFETs

 

If we introduce a channel of charge carriers that allow current to flow with the gate floating, we then need to push them away with a gate voltage to stop the current.

Field effect transistors (MOSFETs)


We can also make depletion mode MOSFETs

 

If we introduce a channel of charge carriers that allow current to flow with the gate floating, we then need to push them away with a gate voltage to stop the current.



Field effect transistors (FETs)

 Electro-static discharge (ESD) is a risk for MOSFETs due to thin oxide.




Field effect transistors (FETs)

  Electro-static discharge (ESD) is a risk for MOSFETs due to thin oxide.




Field effect transistors (FETs)

 Electro-static discharge (ESD) is a risk for MOSFETs due to thin oxide.





Field effect transistors (FETs)

 Note that the MOSFET has large input impedance since little current flows through capacitor; just induces charge to enable I_D current flow.




Field effect transistors (FETs)

  Note that the MOSFET has large input impedance since little current flows through capacitor; just induces charge to enable I_D current flow.




MOSFET switches





MOSFETs are useful as switches

 

On with gate high

 


On with gate low

    

MOSFET switches



MOSFETs are useful as switches

 

MOSFETs are useful for logic

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.




MOSFET inverter

  

MOSFETs are useful for logic

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.


MOSFET inverter

   

But resistors cost more than transistors in both space, €, and power...


CMOS

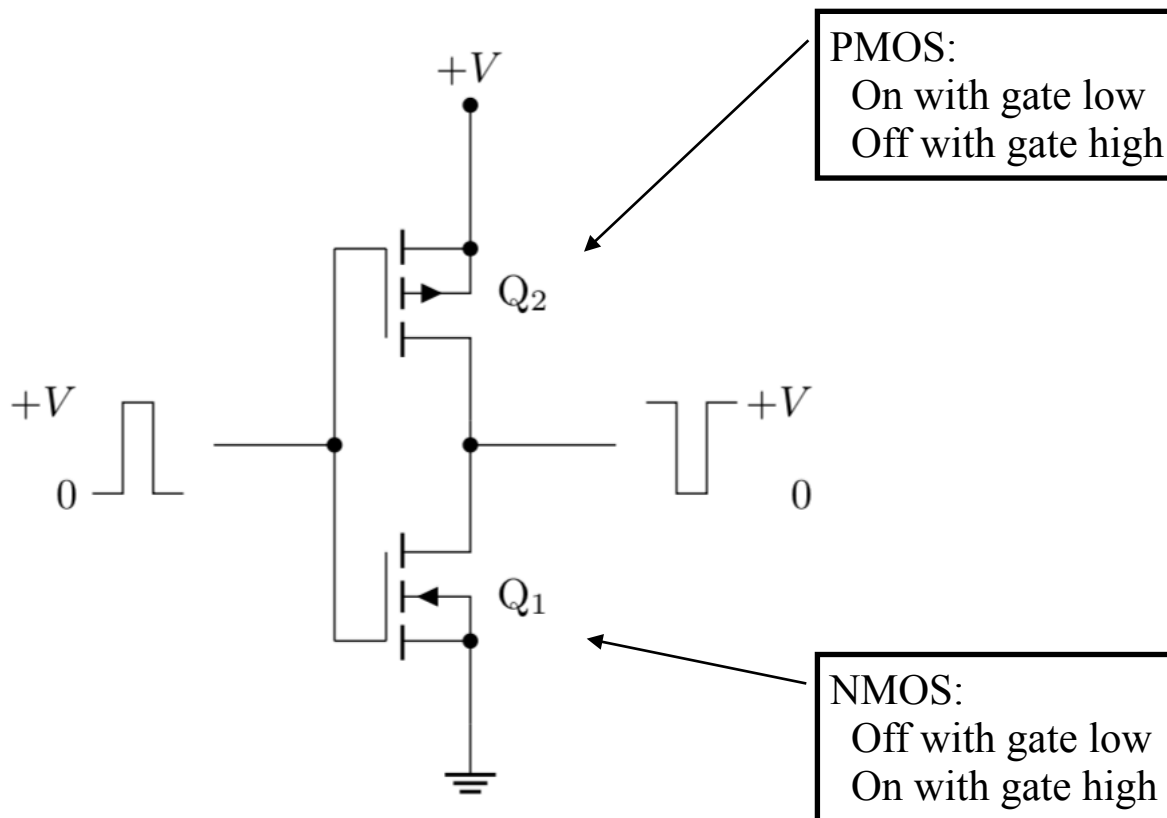Combining n-channel and p-channel MOSFETs together gives a balance of switching. Called, Complementary Metal-Oxide-Semiconductor Field Effect Transistors, or CMOS



CMOS

 
For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.
This is a logic NOT.



CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.


What is this?

 

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.


What is this?

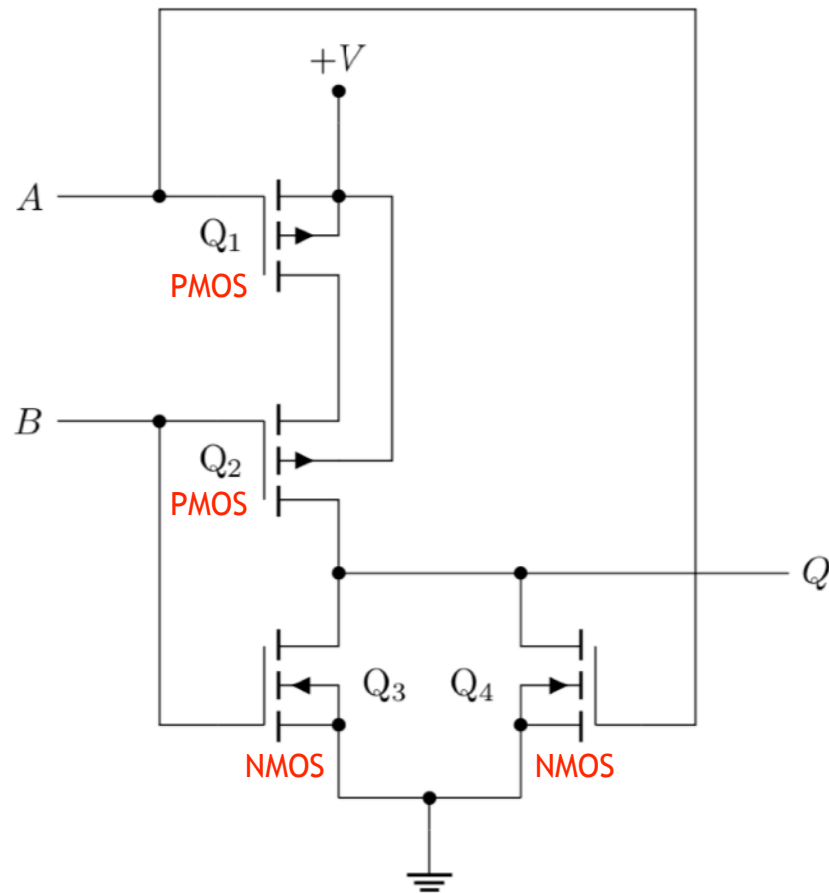

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.

What is this?

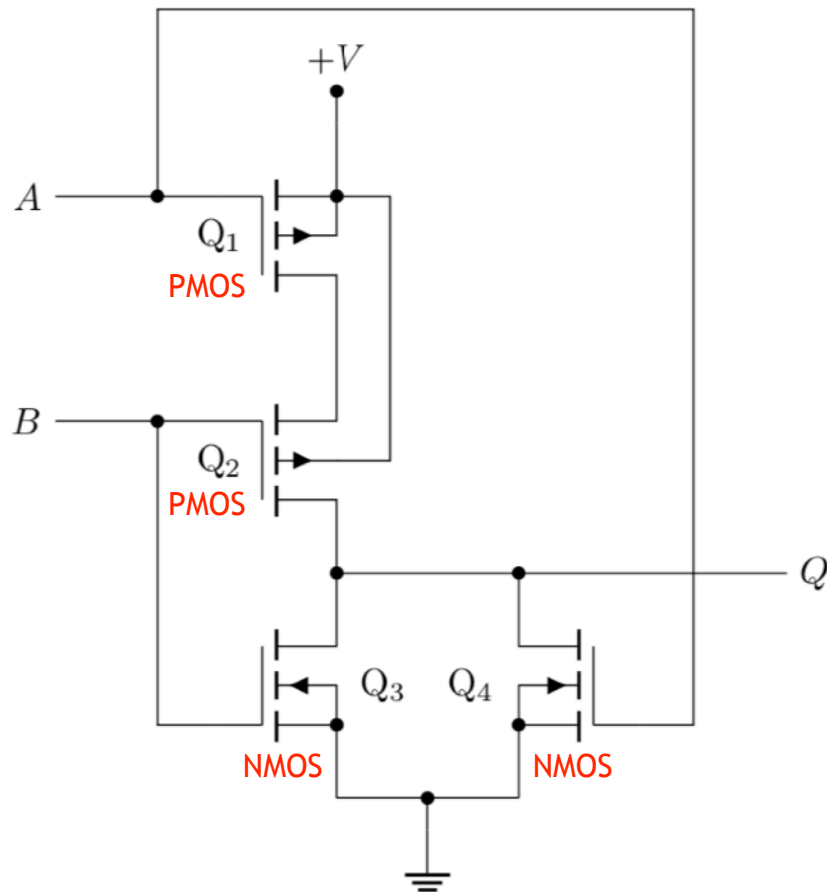

PMOS:
On with gate low
Off with gate high

NMOS:
Off with gate low
On with gate high


Truth table:

A	B	Q
0	0	1
1	0	0
0	1	0
1	1	1

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.

What is this?

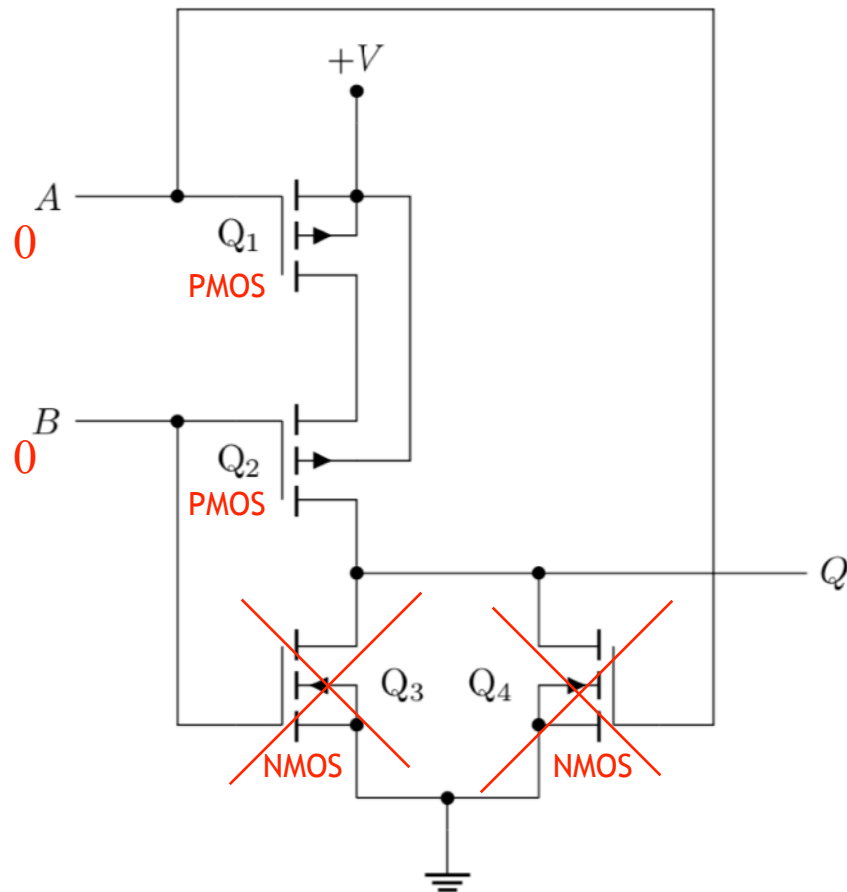

PMOS:
On with gate low
Off with gate high

NMOS:
Off with gate low
On with gate high


Truth table:

A	B	Q
0	0	1
1	0	0
0	1	0
1	1	1

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.

What is this?

 

PMOS:
On with gate low
Off with gate high

NMOS:
Off with gate low
On with gate high


Truth table:

A	B	Q
0	0	1
1	0	0
0	1	0
1	1	1

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.

This is a NOR = NOT OR logic gate

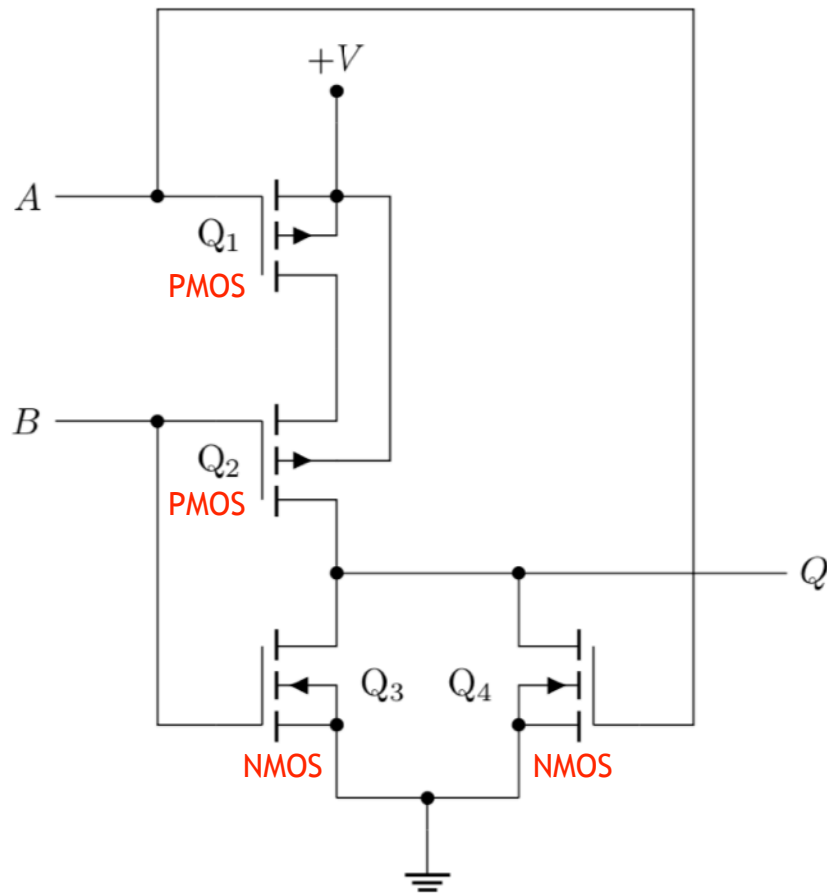

PMOS:
On with gate low
Off with gate high

NMOS:
Off with gate low
On with gate high

Truth table:

A	B	Q
0	0	1
1	0	0
0	1	0
1	1	0

CMOS

For inputs and outputs that are at V_{DD} or V_{SS} only, we can represent logic high and logic low signals and perform logic operations.


What is this?

PMOS:
On with gate low
Off with gate high

NMOS:
Off with gate low
On with gate high

Truth table:

A	B	Q
0	0	
1	0	
0	1	
1	1	

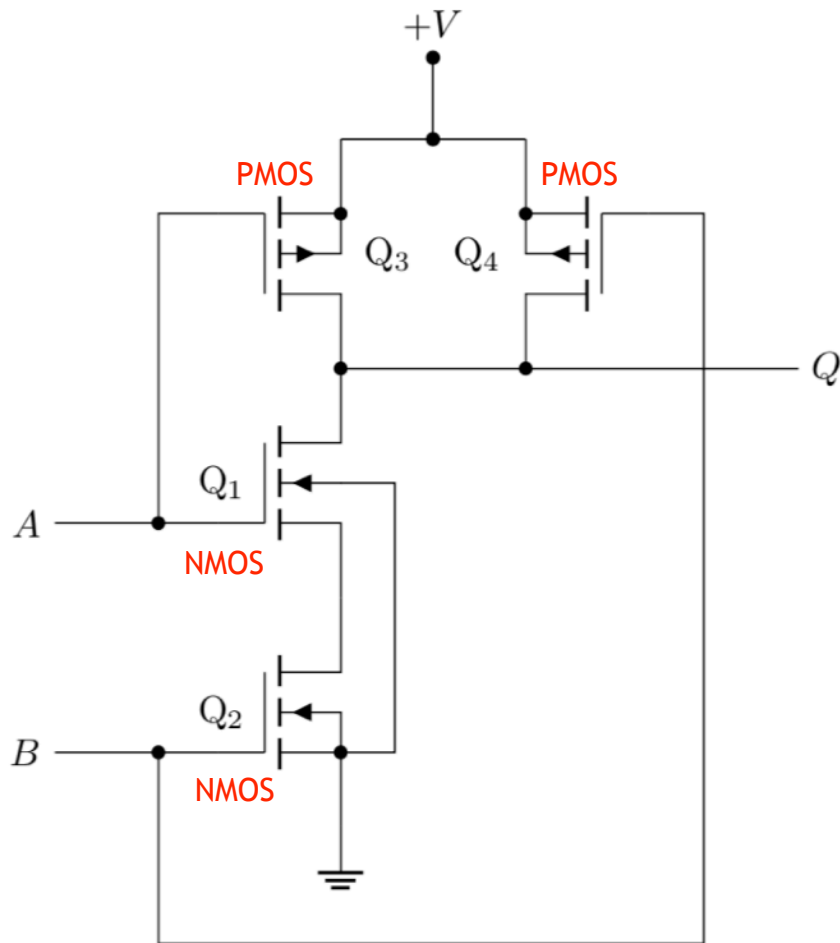

CMOS Logic

CMOS is the workhorse of modern logic circuits

